

(REVISED COURSE)

(3 Hours)

[Total Marks : 100

N.B. (1) Question No. 1 is compulsory.

(2) Attempt any **four** questions out of remaining **six** questions.

1. Answer the following questions (any four) :— 20
 - (a) Describe LM 380 as phono-amplifier.
 - (b) With a neat diagram, explain the operation of direct frequency synthesizer.
 - (c) Explain the method of impedance matching using reactive networks over a narrow frequency range.
 - (d) Explain FET-Mixer with neat diagram.
 - (e) Which are the general features of audio amplifiers ?
2. (a) With a neat block diagram, explain the basic operation of PLL and derive the expression for transfer function of Second Order PLL. 10
 - (b) Explain the following PLL applications : 10
 - (i) Amplitude demodulation
 - (ii) Signal synchronizers and carrier recovery.
3. (a) Explain in detail the analysis of the series RLC circuit and suggest any one application of it. 10
 - (b) Explain different methods of neutralization and feedback techniques used in wideband amplifiers. 10
4. (a) Derive the expressions for resistance and capacitance of a capacitive transformer and show that the turns ratio is $\left(1 + \frac{C_1}{C_2}\right)$. 10
 - (b) Explain the characteristics of RCA 3040 Video-amplifier with a neat circuit diagram. 10
5. (a) What is DDS ? With a neat block diagram explain its operation. 10
 - (b) Explain frequency synthesizer by phase lock method and bring out its advantages as compared with direct frequency synthesizer. 10
6. (a) Design a lossless coupling network that matches a load of $(12 + j5) \Omega$ to a 40Ω source impedance at 20 MHz. 10
 - (b) What is hybrid transformer ? Explain the power transfer in such transformer. 10
7. (a) Design a direct digital frequency synthesizer to generate 15.8×10^6 Hz from a 1×10^6 Hz reference oscillator. 10
 - (b) Drive an expression for output voltage of a double balanced mixer. 10