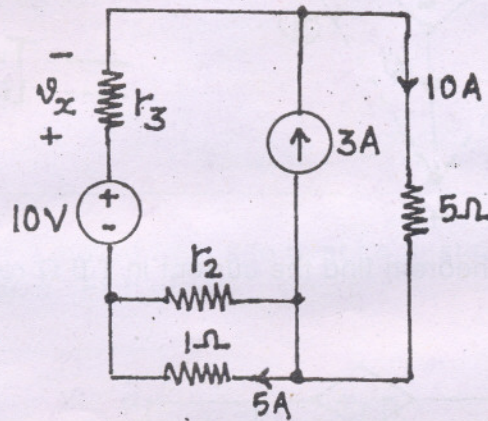


- N.B. (1) Question No. 1 is **compulsory**.
 (2) Attempt any **four** questions out of remaining **six** questions.
 (3) In **all** solve **five** questions.


1. Solve all :

20

- (a) For the network shown determine v_x , r_2 and r_3 .



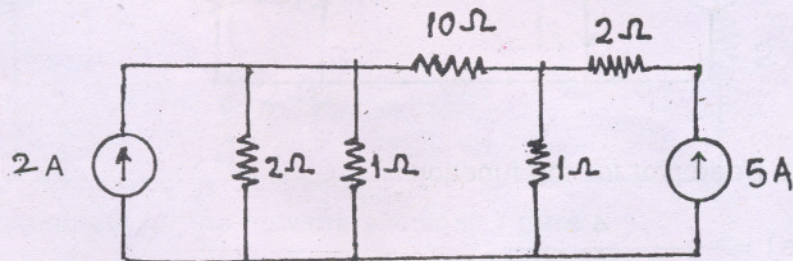
- (b) Using Thevenin's theorem, determine the power loss in the $10\ \Omega$ resistor.




- (c) The reduced incidence matrix $[A]$ of an oriented graph is,

$$A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

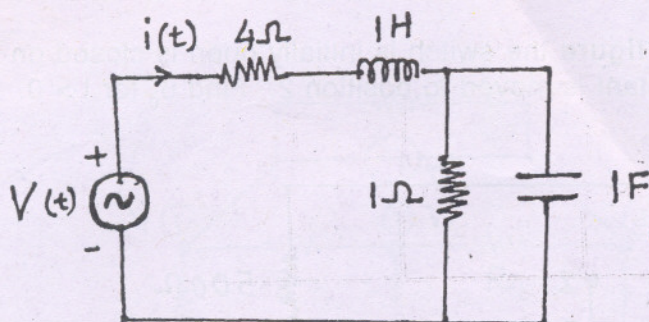
- (i) Draw the graph
 (ii) How many trees are possible for this graph ?
 (d) Obtain the pole zero plot of transfer impedance of the network shown in figure below :



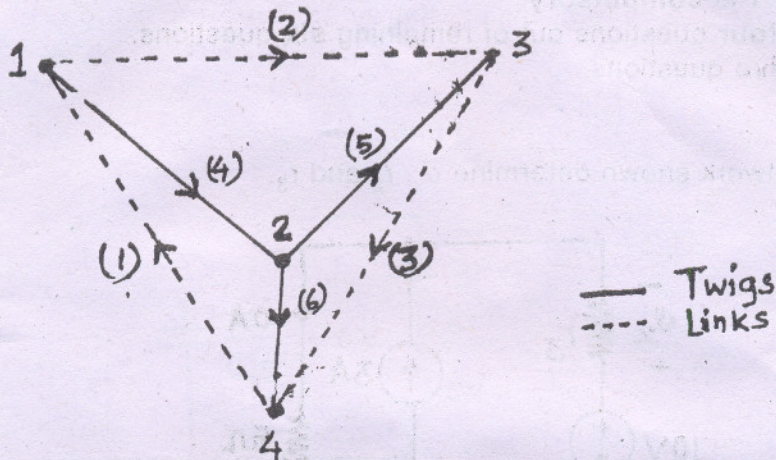2. (a) The oriented graph of a network is shown in figure. Write (i) incidence matrix (ii) f-Cutset matrix and (iii) f-Tieset matrix. 10



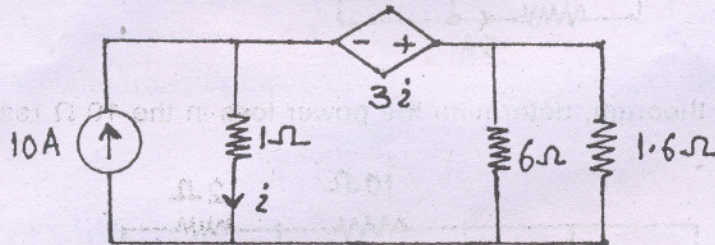
- (b) In the network, by Norton's theorem find the current in 1.6Ω resistor. 10




3. (a) Construct the Bode plot for the function 10

$$F(s) = \frac{4}{(1+s) \left(1 + \frac{s}{3}\right)^2}$$

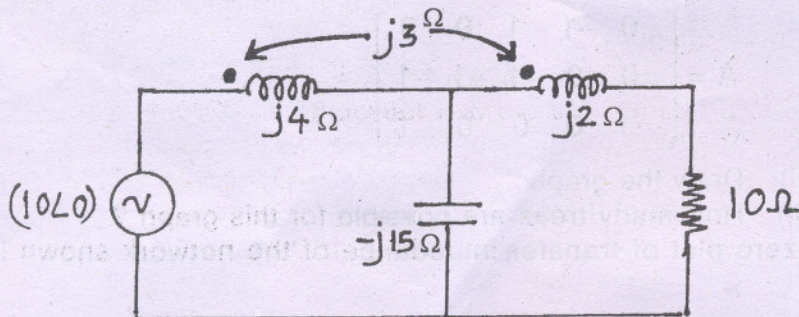- (b) Find the voltage across the 10Ω resistor for the network shown in figure. 10




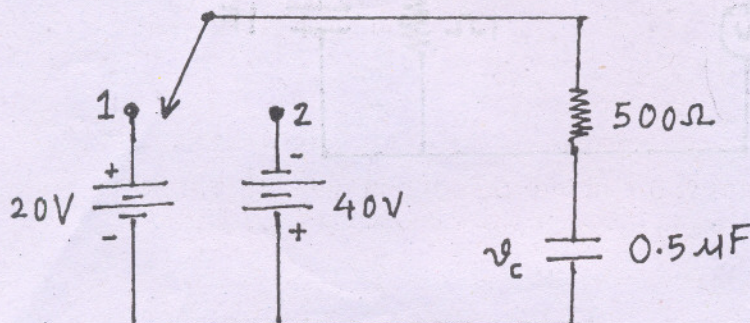4. (a) In the RC circuit shown in figure the switch is initially open is closed on position 1 at $t = 0$ and after 1 time constant is moved to position 2. Find v_c for $t > 0$. 10




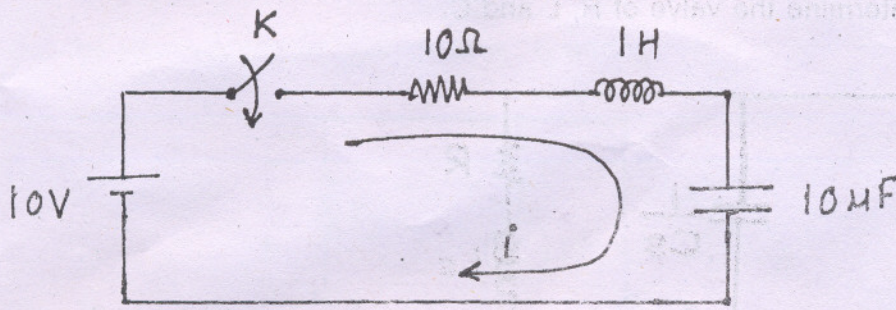(b) In the network shown in figure, switch K is closed. Assuming all initial conditions zero, 10


find i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$



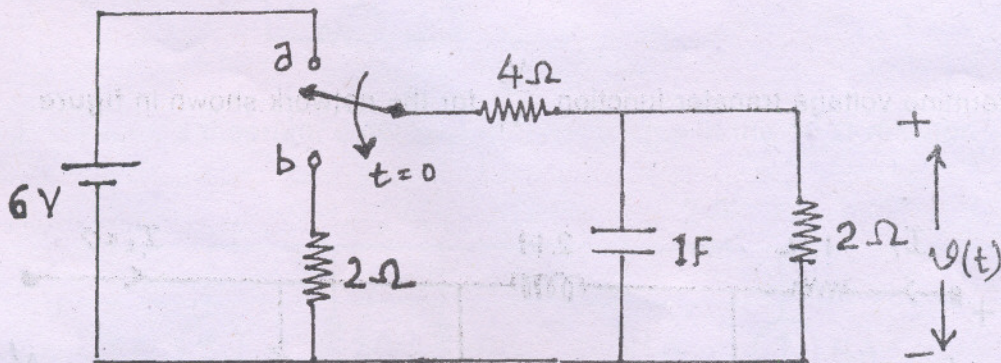
5. (a) In the network switch is moved from a to b, at $t = 0$, steady state conditions having been established in position a. Find $v(t)$. 10



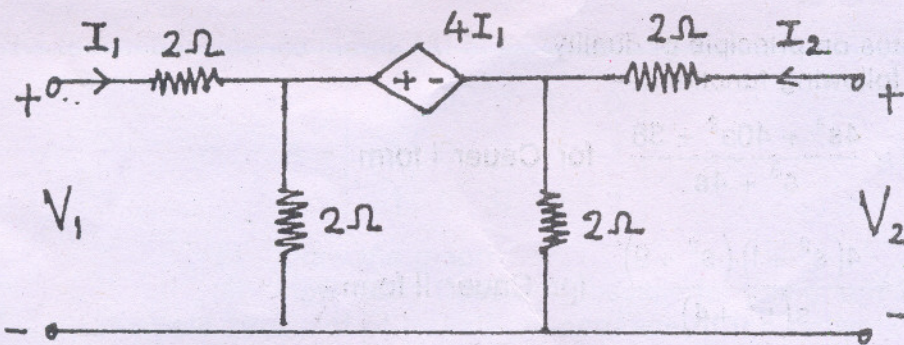(b) Find Z and h-parameters for the network shown in figure. 10



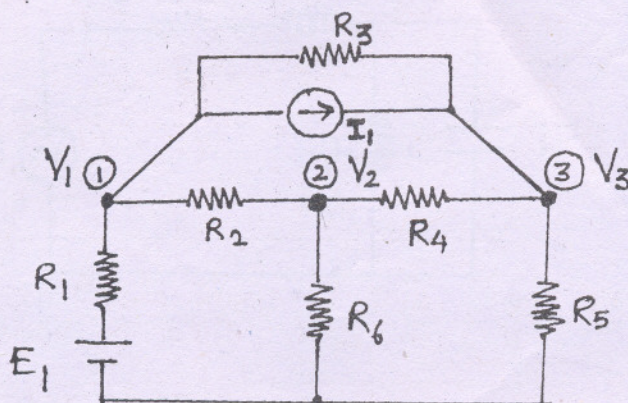6. (a) Develop nodal equations in nodes (1), (2) and (3) in the circuit. 5




- (b) Explain the properties of positive real function (P.R.F.) with proper illustration. 5
 (c) The network is shown in **figure**. The poles and zeros of the driving point function $Z(s)$ of this network are at: 10


Poles at $-\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$

Zeros at -1

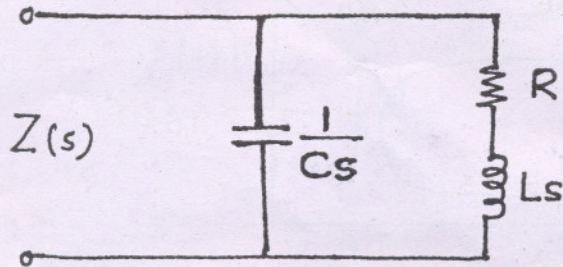If $Z(j0) = 1$, determine the value of R , L and C .



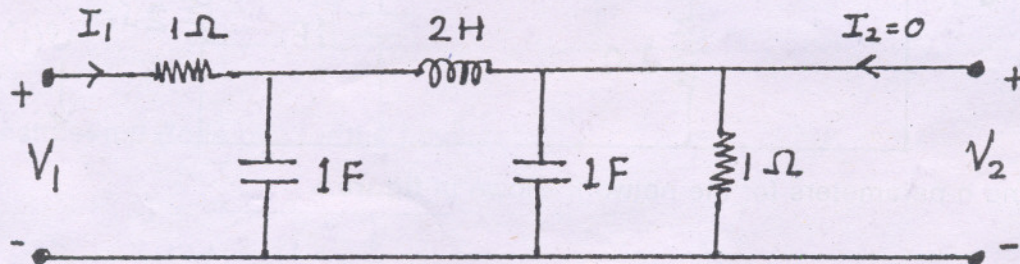7. (a) Determine voltage transfer function $\frac{V_2}{V_1}$ for the network shown in **figure**. 6



- (b) Write short notes on principle of duality.
 (c) Synthesis the following functions—

(i) $Z(s) = \frac{4s^4 + 40s^2 + 36}{s^3 + 4s}$ for Cauer I form

(ii) $Z(s) = \frac{4(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$ for Cauer II form