

Con/5468-07.

(REVISED COURSE)
(3 Hours)

CD-6714

[Total Marks : 100]

N.B (1) Question No. 1 is compulsory

- (2) Attempt any **four** out of the remaining **six** questions.
 (3) Assume **suitable** data if required.
 (4) **Figures** to the right indicate **full** marks.

1. Attempt the following questions

- (a) Draw the graph from given incidence matrix and calculate total number of possible trees.


$$A = \begin{vmatrix} 1 & 0 & 0 & 0 & 1 & 1 \\ -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 & -1 \end{vmatrix}$$

4

- (b) Write a short note on source shifting and source transformation.


4

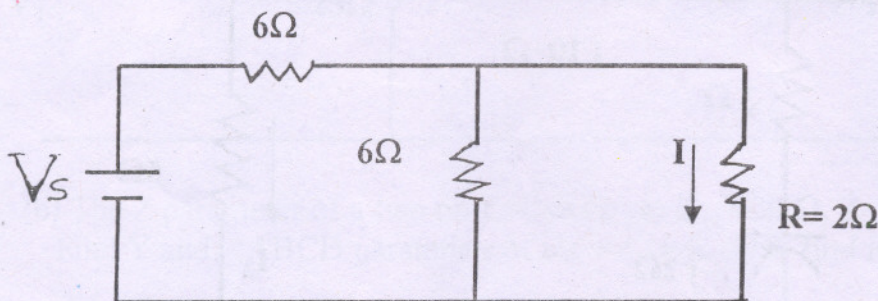- (c) Current in
- 2Ω
- resistor is
- $I = 3A$
- . If
- R
- is changed to
- 3Ω
- , find new value of
- I



4

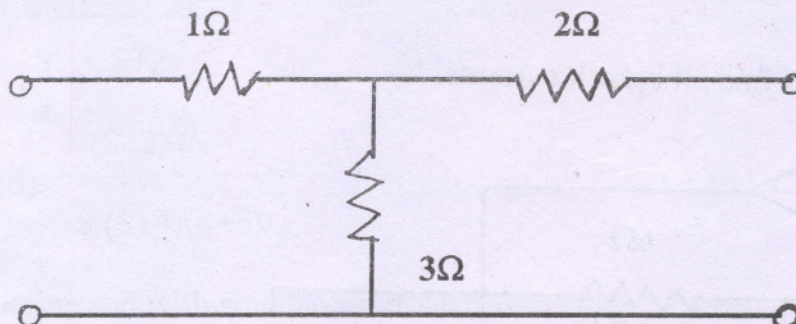- (d) Determine parameter
- Z_{22}
- and
- A
- for the network shown.



4

- (e) Write short note on initial condition and its significance.

4

Con/5468-CD-6714-07.


2

2 (a) Find V_{out} by superposition theorem.


50Ω

200Ω

10

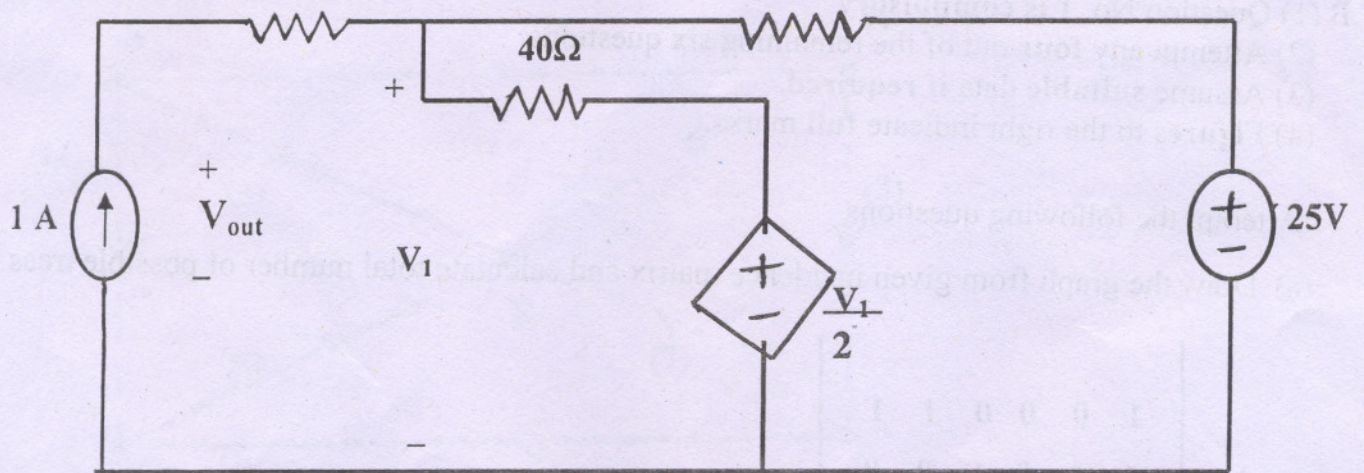


(b) Find I_2 by mesh analysis.

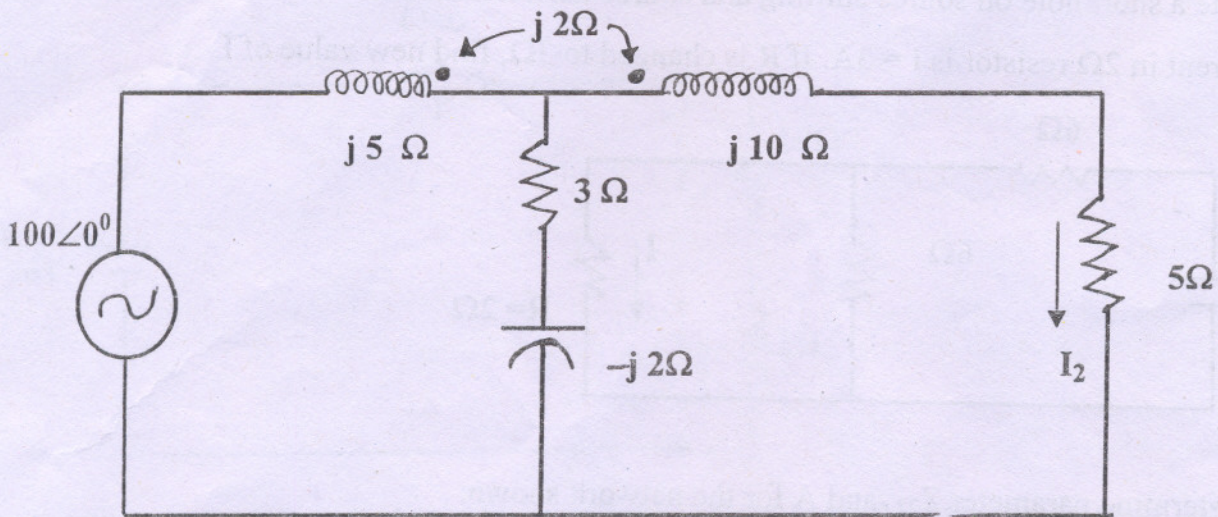

3 (a) Use mesh analysis and find all branch currents.


10

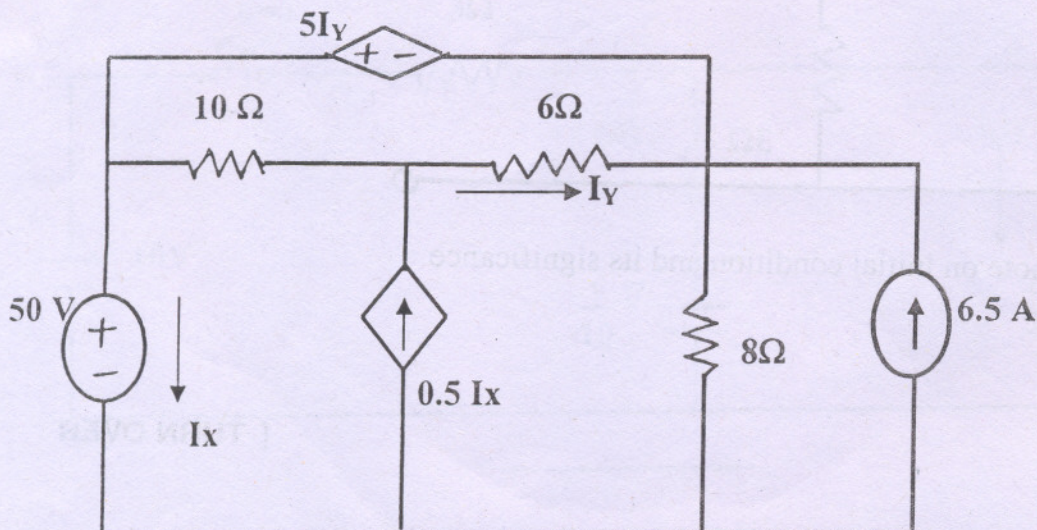


Con/5468-CD-6714-07.

3

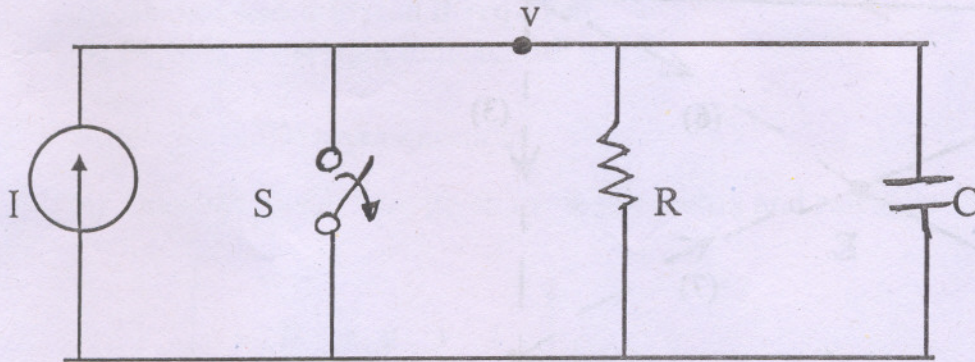(b) Switch is opened at $t=0$. Solve for v , $\frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$ at $t=0^+$ 10



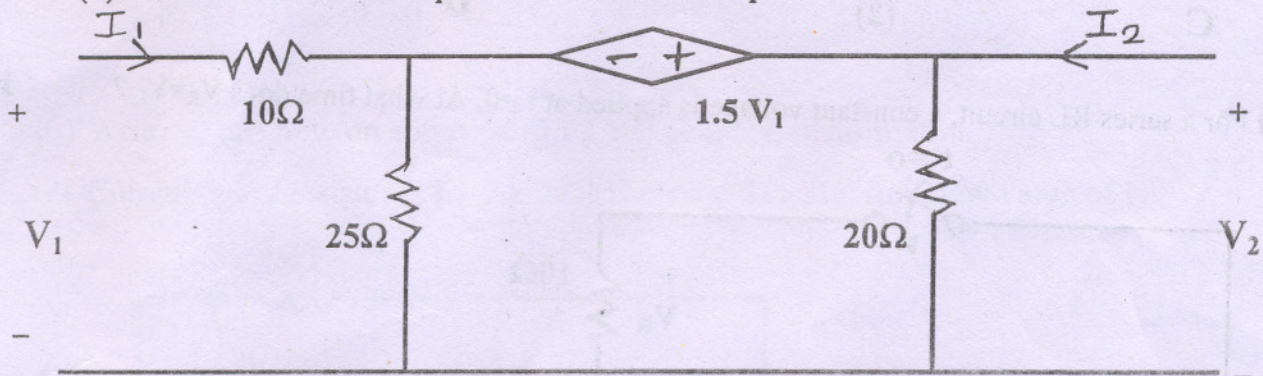4 (a) Find the transmission parameter for the two-port network shown. 10



(b) The Z parameter of a two port network are $Z_{11}=20 \Omega$, $Z_{22}=30 \Omega$, $Z_{21}=Z_{12}=10 \Omega$. Find Y and ABCD parameter of the network. Also find its equivalent T network 10

5 (a) Test whether following functions are positive real or not. 10


(i) $\frac{S+2}{S^2+3S+2}$ (ii) $\frac{S^2+6s+2}{S^2+3S+5}$

(b) $Y(S) = \frac{(S+2)(S+5)}{S(S+4)(S+6)}$ synthesize using Cauer-I and Cauer-II form. 10


6 (a) Define and with suitable example differentiate between 10

- i) Tree and Cotree
- ii) f-cutest matrix and Tieset matrix
- iii) Planer and nonplaner graph.

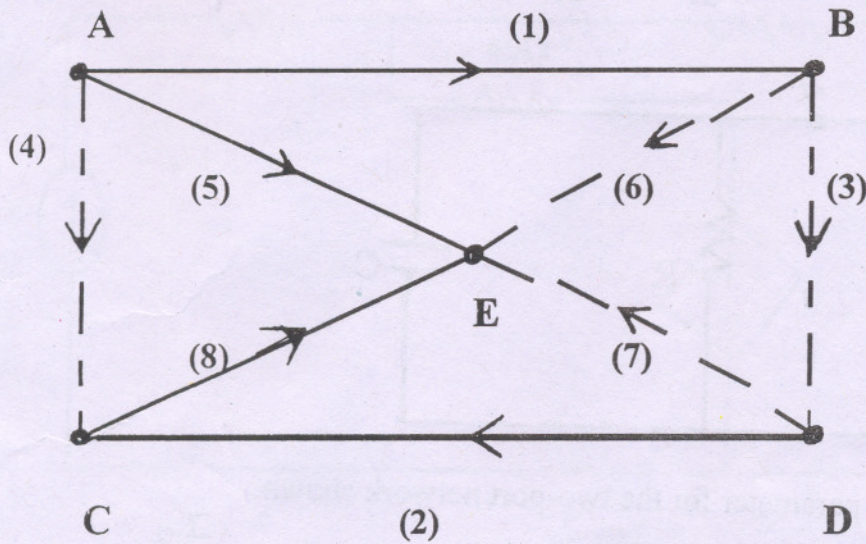(b) Obtain Incidence matrix, Tieset matrix and f-cutest matrix for the graph shown. 10



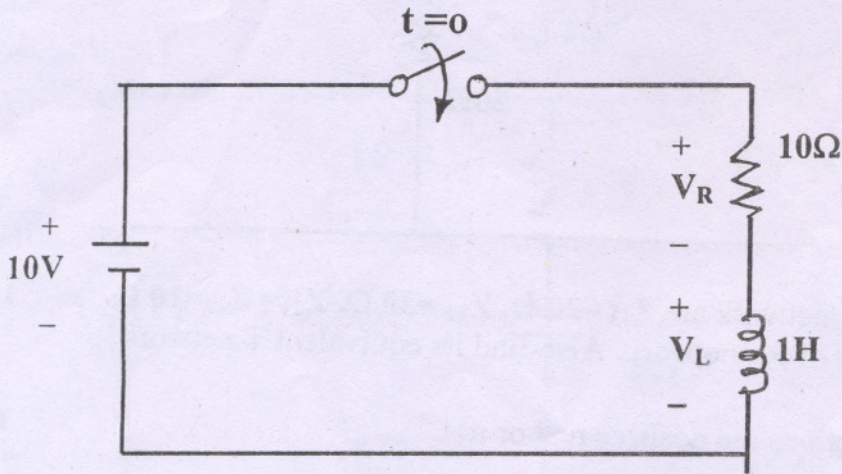7 (a) For a series RL circuit, a constant voltage is applied at $t=0$. At what time does $V_R=V_L$? 10



(b) In the network shown the switch is opened at $t = 0$ when steady state condition has been reached previously. Find $i(t)$ for $t > 0$ for open switch position. Use Laplace method. 10

