


(REVISED COURSE)

(3 Hours)


[Total Marks : 100

- N.B.** (1) Question No. 1 is compulsory.
 (2) Attempt any **four** out of remaining **six** questions.
 (3) Figures to the **right** indicate **full** marks.

 1. (a) Compare synchronous counters and asynchronous counters. 6
 (b) Draw a switch debouncer using NAND gates and explain it. 8
 (c) Develop state diagram for serial binary adder to be designed as Moore machine. 6
2. (a) Design a MOD-100 counter using IC-7493. 10
 (b) Design two bit Bidirectional shift register using JK flip-flop. Follow all the steps in designing of sequential machine. 10
3. (a) Design a synchronous counter with JK flip-flops which runs through a sequence of- 10



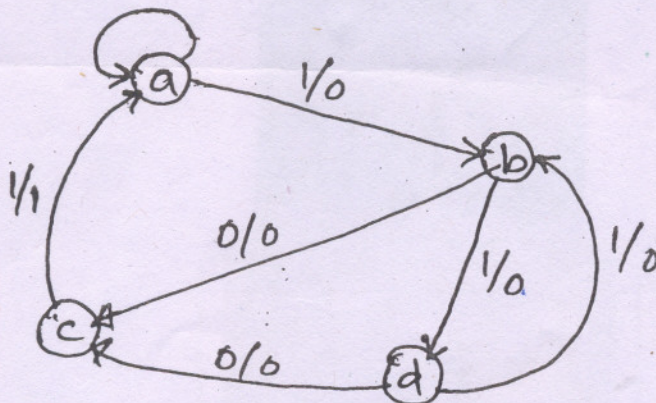- (b) The sequential state diagram may have one or more redundant states. Using state reduction technique obtain the minimised state diagram. 10



4. (a) Write a VHDL code for a left to right shift register with an enable input. 10
 (b) Draw and explain logic diagram for 8 × 4 diode ROM. 10
5. (a) Design a state machine that detects three or more consecutive 1's in a string of bits coming through an input line. Synthesize the circuit using D flip-flops. 10
 (b) Write a VHDL code for a two digit BCD counter. 10
6. (a) Draw the universal state diagram for a 4-bit serial in parallel out right shift register. How twisted ring counter can be designed using this register? 10
 (b) Discuss CPLD Xilinx XC 9500 architecture with neat block diagram. Describe main features. 10
7. Write a short notes on (any two) :- 20
 - (a) XC 4000 FPGA family
 - (b) VHDL features
 - (c) Estimation of digital system reliability.