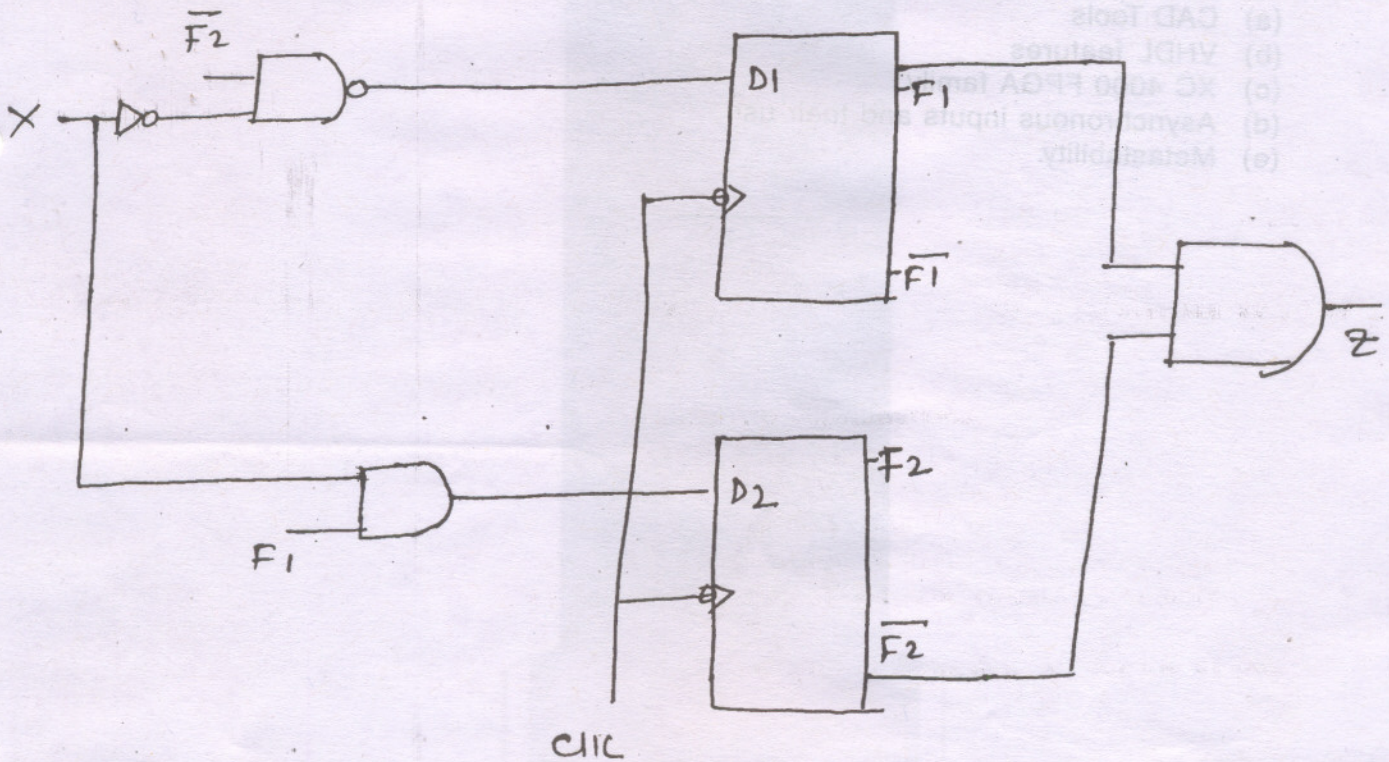


(3 Hours)

[Total Marks : 100

- N.B. (1) Question No. 1 is compulsory.
 (2) Attempt any four questions out of remaining six questions.
 (3) Figures to the right indicate full marks.


1. (a) Compare synchronous counters and asynchronous counters. 6
- (b) Draw a switch debouncer using NAND gates and explain it. 6
- (c) Design sequential m/c serial binary adder using JK F/F and NAND gates only. 8
2. (a) Analyze the sequential machine shown and obtain the state diagram for the same. 10



- (b) Write a VHDL code for a left to right shift register with an enable input. 10
3. (a) Design a coin operated vending m/c that dispenses candy under following condition :— 10
 - (i) The machine accept nickels (= 5 cents) and dimes (= 10 cent)
 - (ii) It takes 15 cents for a piece of candy to be released from the machine.
 - (iii) If the 20 cents is deposited, the machine will credit the buyer with 5 cents and wait for the buyer to make second purchase.

Follow all the steps including state decomposition and state assignment rules in designing of above machine.

 - (b) Design a synchronous counters with JK F/F which runs through a sequence of 10



4. (a) What are different types of shift registers ? Design 4 bit Johnson counter using 74194 universal shift register. 10
- (b) Discuss various modes of operating IC 7490. Also include sequence table for various modes. 10
5. (a) Explain SRAM architecture block diagram with timing diagram for read and write operation. 10
- (b) Design a state machine that detects three or more consecutive 1's in a string of bits coming through an input line synthesis the circuit using D flip-flops. 10
6. (a) Give the main features of Xilinx XC 9500 CPLD family. 10
- (b) Discuss the main issues related to the estimation of Digital System Reliability. 10
7. Write notes on (any three) :— 20
- (a) CAD Tools
 - (b) VHDL features
 - (c) XC 4000 FPGA family
 - (d) Asynchronous inputs and their use
 - (e) Metastability.