

N.B. : (1) Question No. 1 is **compulsory**.

(2) Attempt any **four** questions from remaining **six** questions.

(3) Assume **suitable** data if **required** and state it **clearly**.

1. (a) Draw the circuit diagram of three op-amp instrumentation amplifier. Get 10
an expression for the output.
- (b) Why is an op-amp diode rectifier called as a precision rectifier ? Explain 10
with waveforms.
2. (a) Design a voltage regulator using IC 723 to regulate the output voltage between 10
4V to 20V and output current of 100 mA.
- (b) Draw the circuit diagram and explain multiplication and division of two analog 10
signals using op amps.
3. (a) Explain how a missing pulse can be detected using IC 555. 10
- (b) Design an op-amp based Schmitt trigger with $UTP = +4V$, $LTP = -2V$. 10
Assume op-amp is powered with $\pm 12V$ and $V_{ref.} = -3V$.
4. (a) Design a phase shift oscillator with $f_o = 5 \text{ KHz}$. How is the peak to peak 10
output voltage adjusted ?
- (b) Draw the functional block diagram of PLL IC 565 and explain its working. 10
5. (a) What are the different types of Digital to Analog converters ? Explain 10
one of the techniques in detail.
- (b) Design a Low-pass, second order KRC filter using equal component design 10
using $f_o = 1 \text{ KHz}$ and $Q = 5$. What is its dc gain ?
6. (a) Explain the frequency response of an ideal integrator and that of practical 10
integrator with figures.
- (b) What are the main features of IC 8038 ? 10
7. Write notes on (any two) :- 20
 - (a) Switched Capacitor Filters
 - (b) Three Pin Regulators
 - (c) Dual Slope ADC
 - (d) Antilog Amplifier.