


Lib

Electrical Network Analysis & Synthesis


- N.B. : (1) Question No. 1 is compulsory.
 (2) Solve any four questions from Q. Nos. 2 to 7.
 (3) Assume suitable data if necessary.

2.30 to 5.30

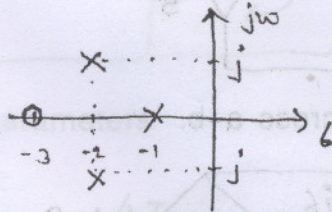
1. (a) Determine the network function if d.c. gain of the system is 10 and p-z diagram is as shown - 4



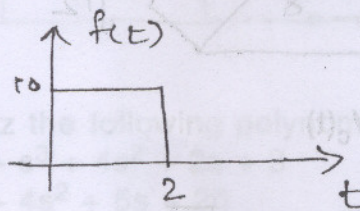
- (b) State the properties of positive real function. 4
 (c) Express transmission parameters in terms of Z-parameters. 4
 (d) Find the Laplace transform of the waveshape shown. 4



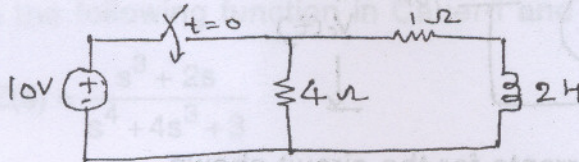
- (e) What is time constant of the circuit? Find the same for the circuit shown. 4



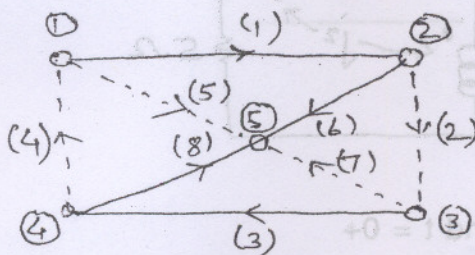2. (a) Write A, B and Q matrices for the graph shown. 10




- (b) At what time does $V_R = V_L$ 10

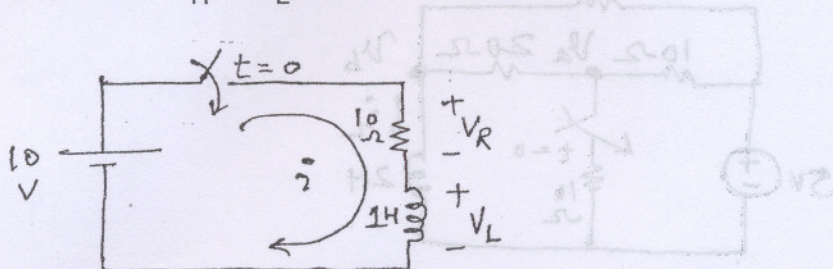


3. (a) Find magnitude of VCCS by Mesh Analysis.

10

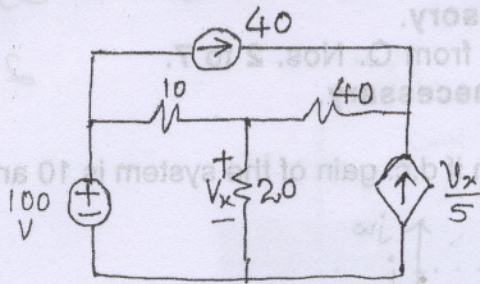


(b) Find Thevenin's equivalent across a-b:

10

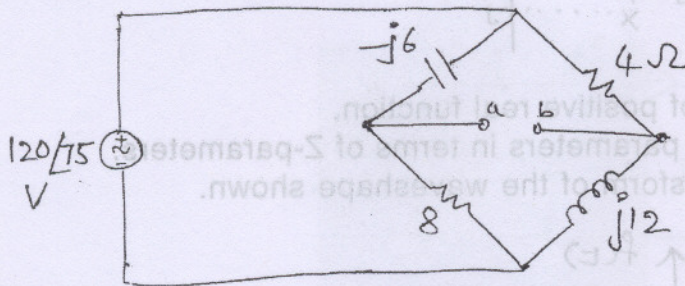


4. (a) For a unit ramp input find $V_c(t)$

10

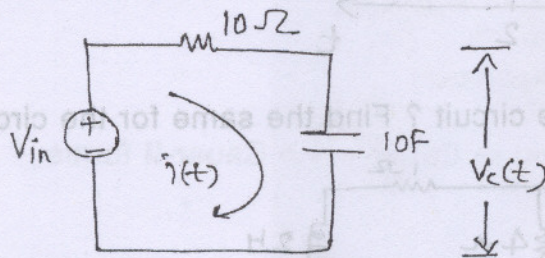


(b) Calculate the Mesh currents for the circuit shown.

10

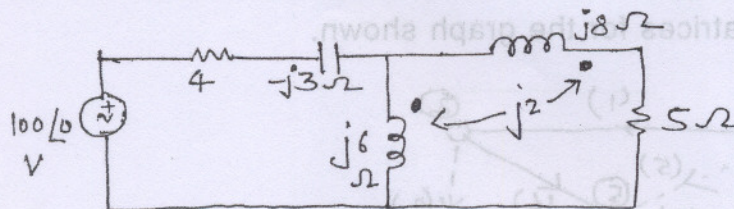


5. (a) Find V_a and V_b at $t = 0^-$ and $t = 0^+$

10

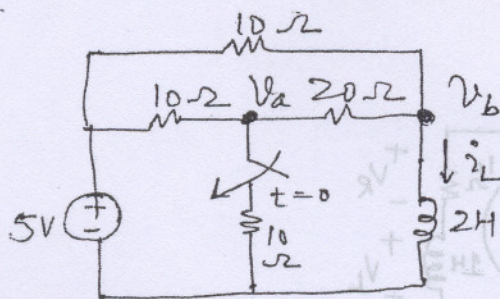


(b) Find $i(t)$ for $t > 0$

10

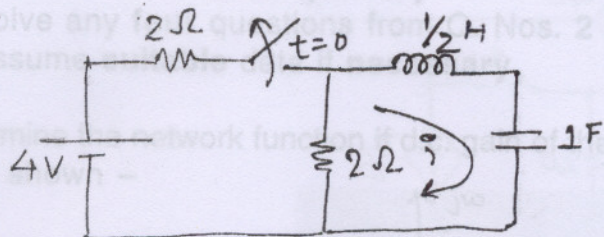

6. (a) Find Z and h - parameters

10

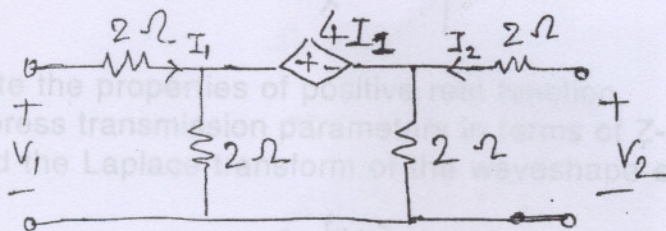

(b) Check for Hurwitz the following polynomials :

10

(i) $P(s) = s^4 + s^3 + 4s^2 + 2s + 3$

(ii) $P(s) = s^3 + 4s^2 + 5s + 20$

Use Continued Fraction Expansion.

7. (a) Realize the following function in Cauer-I and Cauer-II forms.

10

$$Z(s) = \frac{s^3 + 2s}{s^4 + 4s^3 + 3}$$

(b) Define Z and Y parameters. Also derive the condition for RECIPROCITY for Z-parameters.

10

(a) Write A, B and Q matrices for the graph shown.

10