

- N. B. : (1) Question No. 1 is compulsory.
 (2) Attempt any four questions out of remaining six questions.
 (3) Assume suitable data wherever necessary.
 (4) Figures to the right indicate full marks.

1. Answer any five:-

20


- (a) How to find gain margin and phase margin from Bode Plot.
- (b) Compare open and closed loop control systems and give examples.
- (c) Compare the two stability methods:-
 (i) Root Locus (ii) Routh's Criterion.
- (d) Draw the step responses of a standard second order undamped, underdamped and critically damped system. Also show pole locations of these systems.
- (e) Define 'Type' and 'Order' of the system. Hence determine 'Type' and 'Order' of a control system with

$$G(s) = \frac{5(S+1)}{S(S+5)(S+4)} \text{ and } H(s) = 1$$

- (f) Explain Hurwitz Stability Criterion. What are its disadvantages?


2. (a) Find the transfer function $\frac{C(s)}{R(s)}$ using Block diagram Reduction Technique-

10

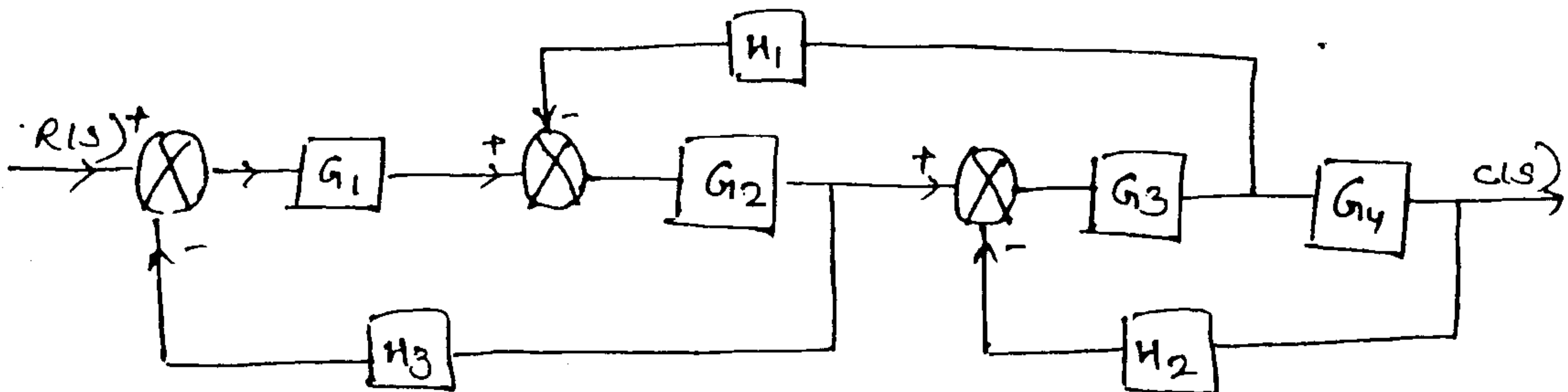

- (b) Derive the expression for output response of standard second order underdamped system. 10

3. (a) Consider the following block diagram shown. Draw its equivalent signal flow graph and find the transfer function $\frac{C(s)}{R(s)}$ using Mason's gain rule. 10

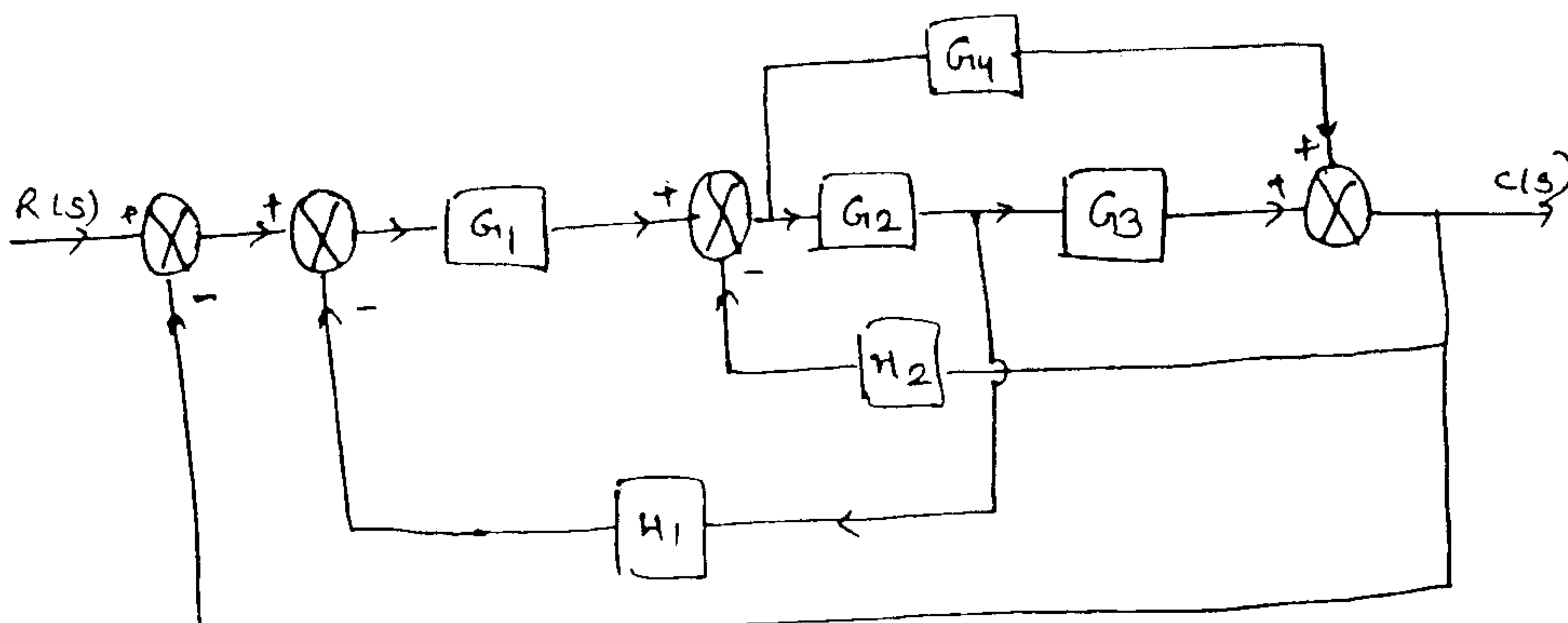

Con. 5580-LJ-10391-13.

- (b) Find all the error coefficients for unity feedback systems having transfer function as **10**

$$(a) G(s) = \frac{14(s+3)}{s(s+5)(s^2+2s+2)} \quad (b) G(s) = \frac{26}{s^2(s-1)(s^2+6s+13)}$$

Calculate the 'Type' of the system in each case.

4. (a) Using Routh's Stability Criterion, determine the number of roots on imaginary axis for the system $S^6 + 4S^5 + 3S^4 - 16S^2 - 64S - 48 = 0$ and comment on stability of given system. **10**

- (b) Sketch the root locus for the system having **10**

$$G(s).H(s) = \frac{K(s+0.5)}{s(s^2+2s+2)}$$

Also determine 'k' for damping ratio of 0.5 from the root locus.

5. (a) Sketch the Bode plot for system **10**

$$G(s).H(s) = \frac{242(s+5)}{s(s+1)(s^2+5s+121)}$$

Comment on system stability.

- (b) Sketch the polar plot for the system having transfer function $G(s) = \frac{1}{s(1+s)^2}$ **10**

6. (a) Sketch the Nyquist plot for $G(s).H(s) = \frac{50}{(s+1)(s+2)}$ **10**

and comment on the closed loop stability of the system.

- (b) Derive the transfer function of a armature controlled DC servomotor and obtain the resulting block diagram. **10**

7. Write short notes on following:-- **20**


- (a) Synchros
 (b) Co-relation between time domain and frequency Domain specifications.
 (c) PI and PD controllers.

- N.B. : (1) Question No. 1 is compulsory.
 (2) Attempt any **four** questions from the remaining **six** questions.
 (3) Assume suitable **data** wherever required but **justify** the same.


1. (a) State properties of Hurwitz polynomial. 5
 (b) Express transmission parameters in terms of admittance parameters. 5
 (c) Given the incidence matrix obtain the linear graph. :- 5

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & -1 \\ 0 & 0 & -1 & 1 & 1 \end{bmatrix}$$

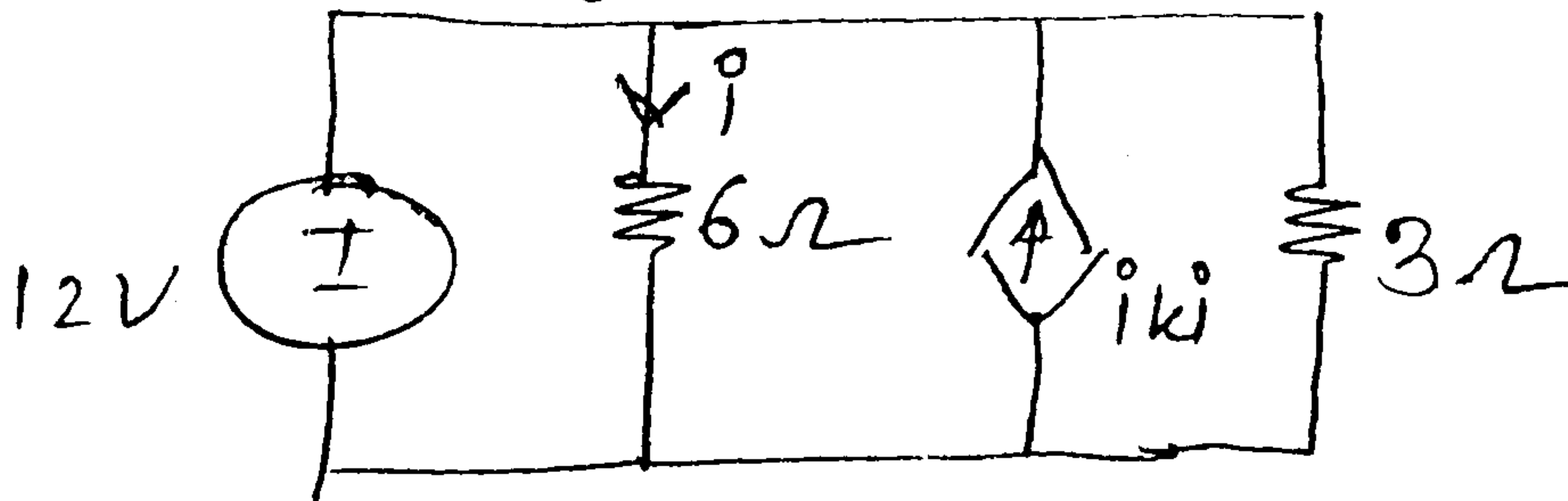
- (d) Determine 'Ki' for the given network :- 5



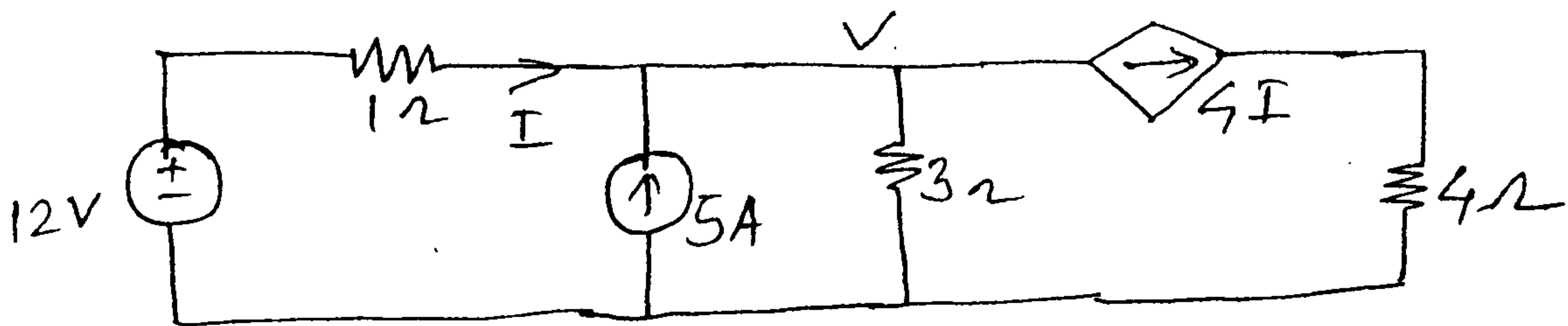
2. (a) Find current in the 4 ohm resistor of the circuit using superposition theorem :- 10



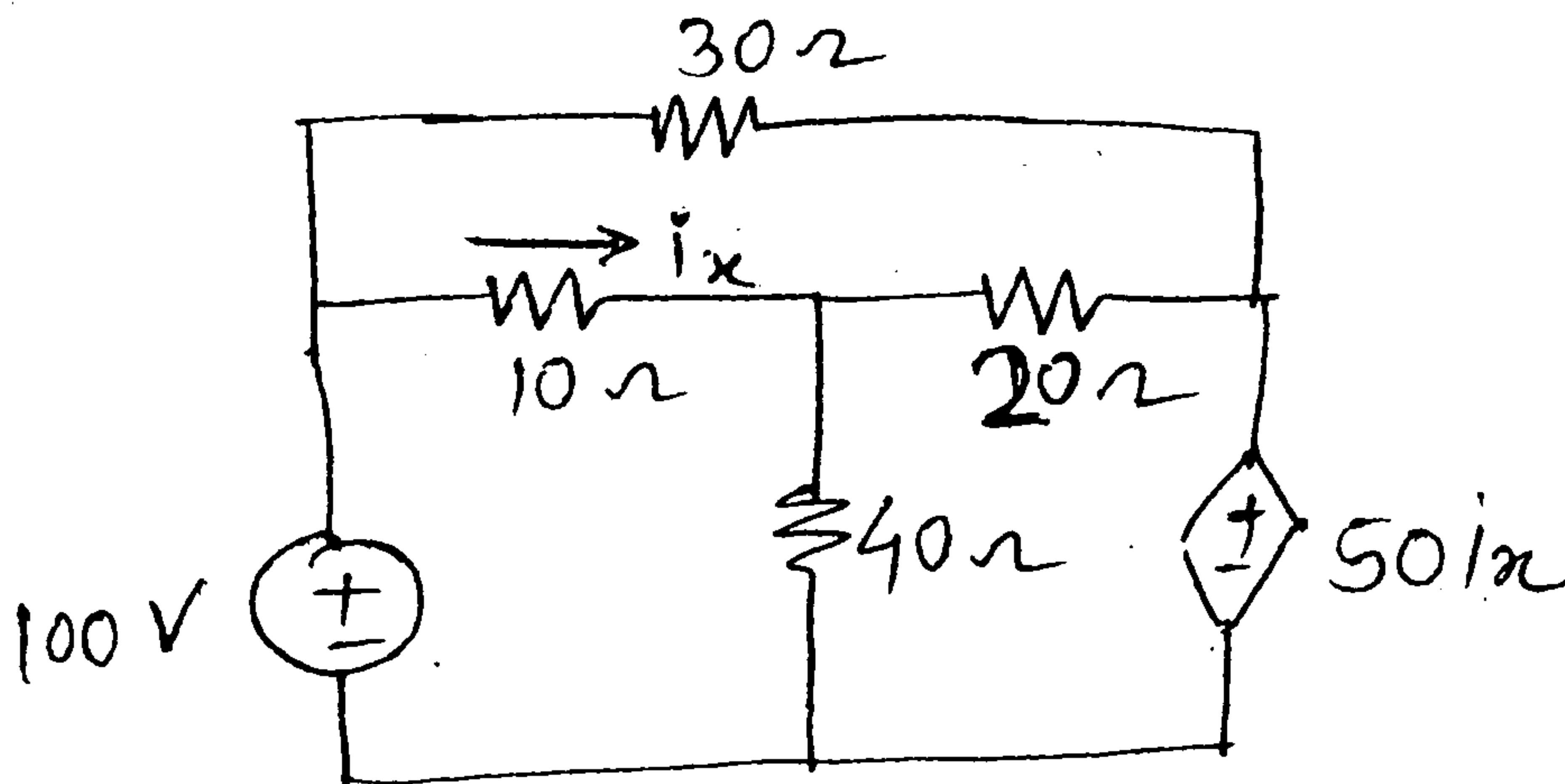
- (b) Find power associated with CCVS :- 10



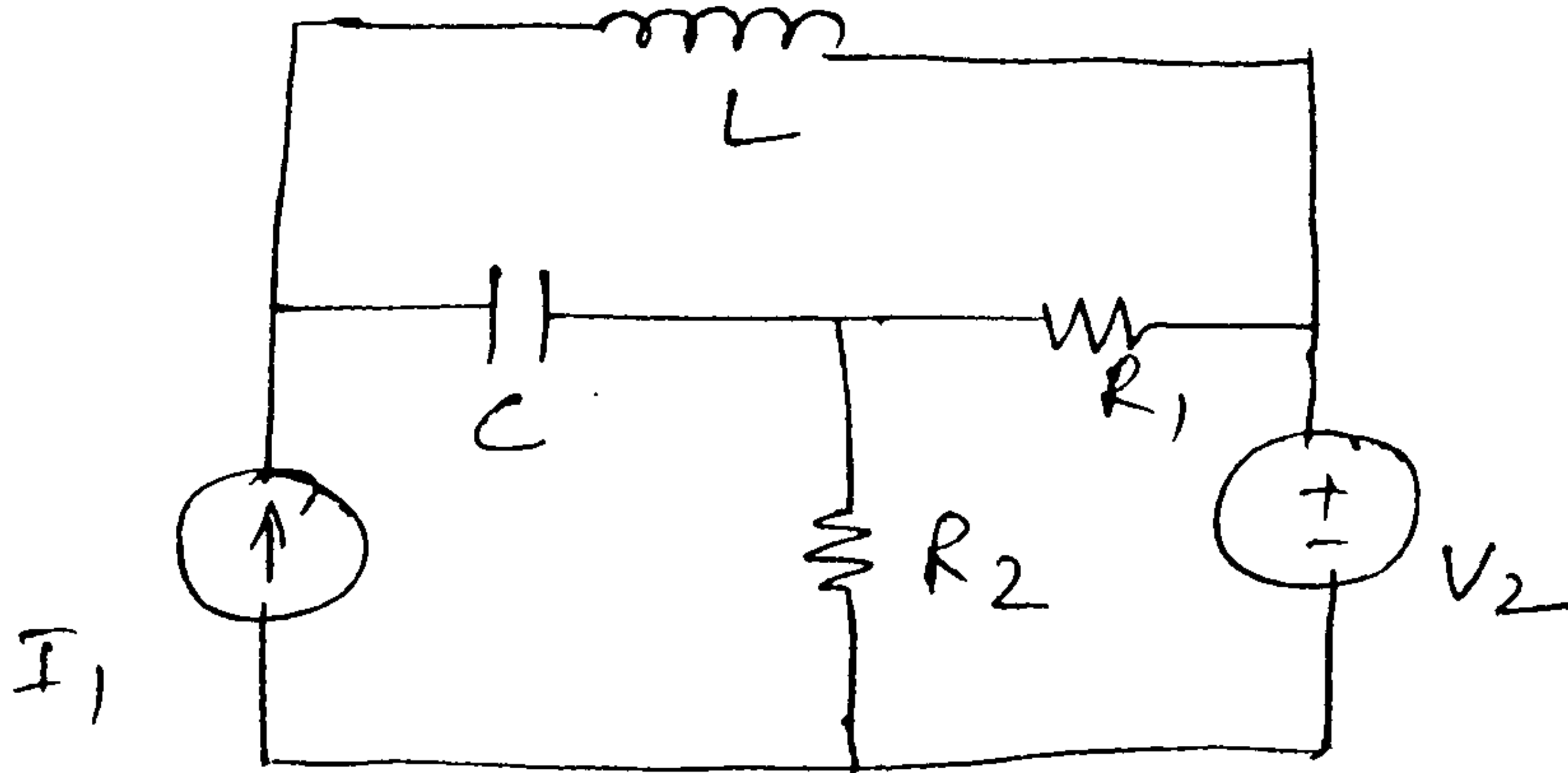
3. (a) Find Incidence matrix, cutset matrix, tieset matrix, for the network shown below. 10



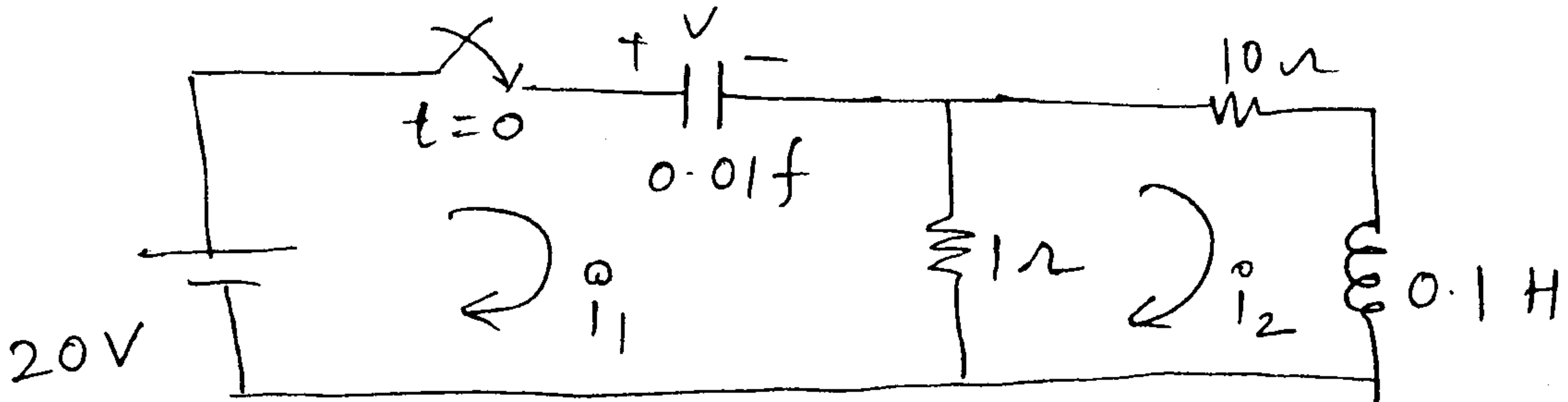
(b) Determine $i_1, i_2, \frac{di_1}{dt}, \frac{d^2i_1}{dt^2}, \frac{d^2i_2}{dt^2}$ at $t=0^+$ in the circuit shown :- 10



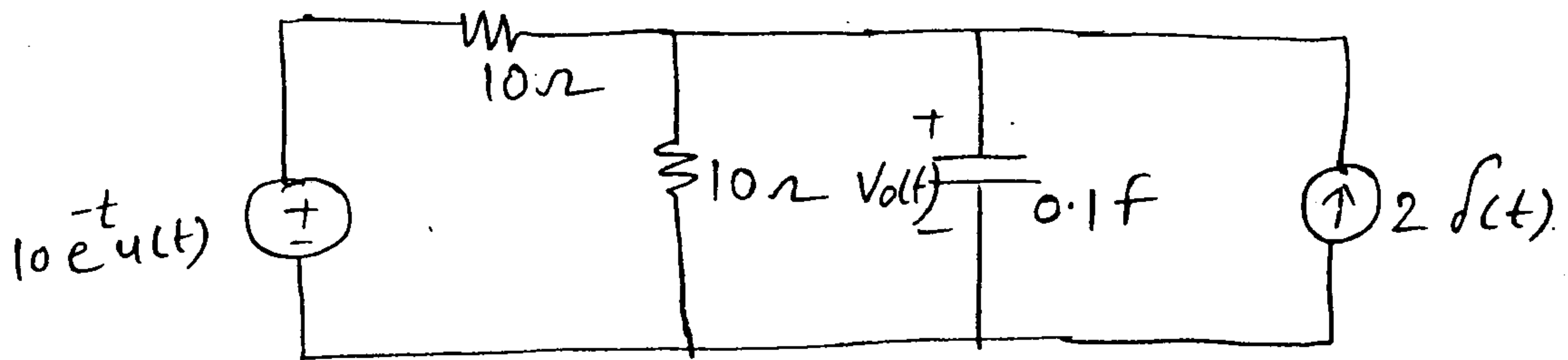4. (a) Find $V_o(t)$; Assume $V_o(0) = 0V$:- 10




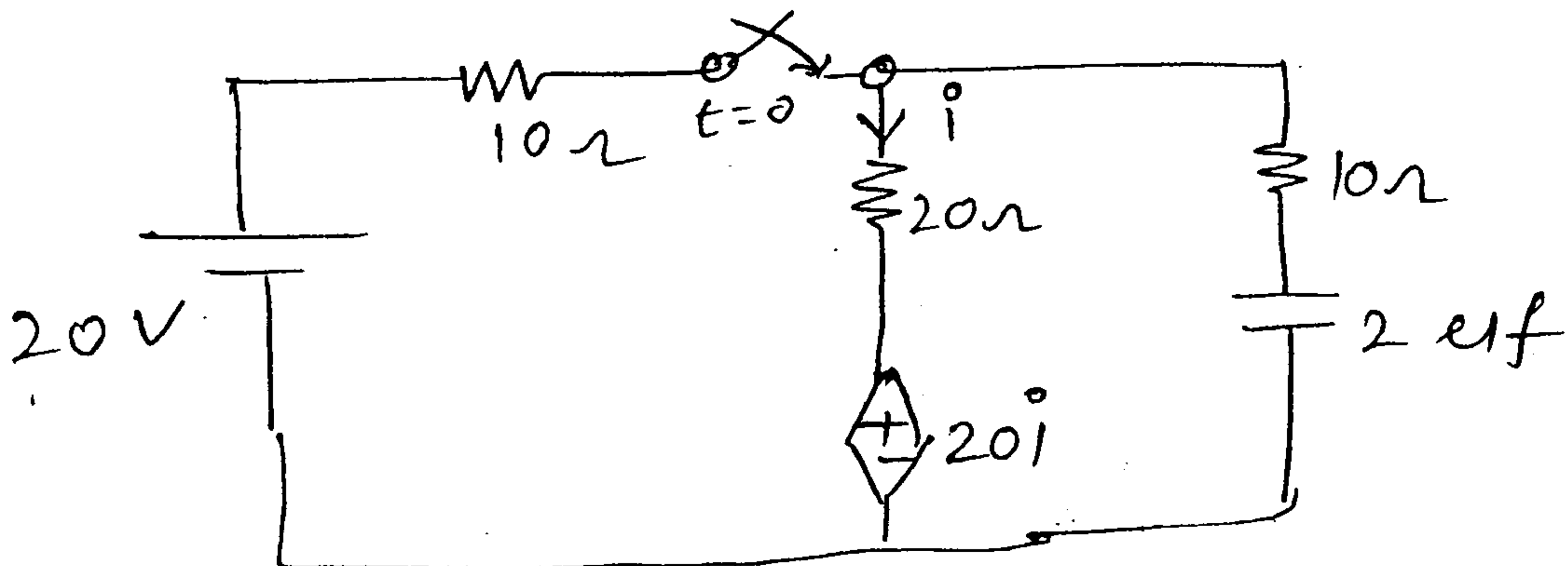(b) For the circuit shown find current equation when switch is opened at $t=0$. 10




5. (a) Find three loop currents at $t=0^+$:-

10

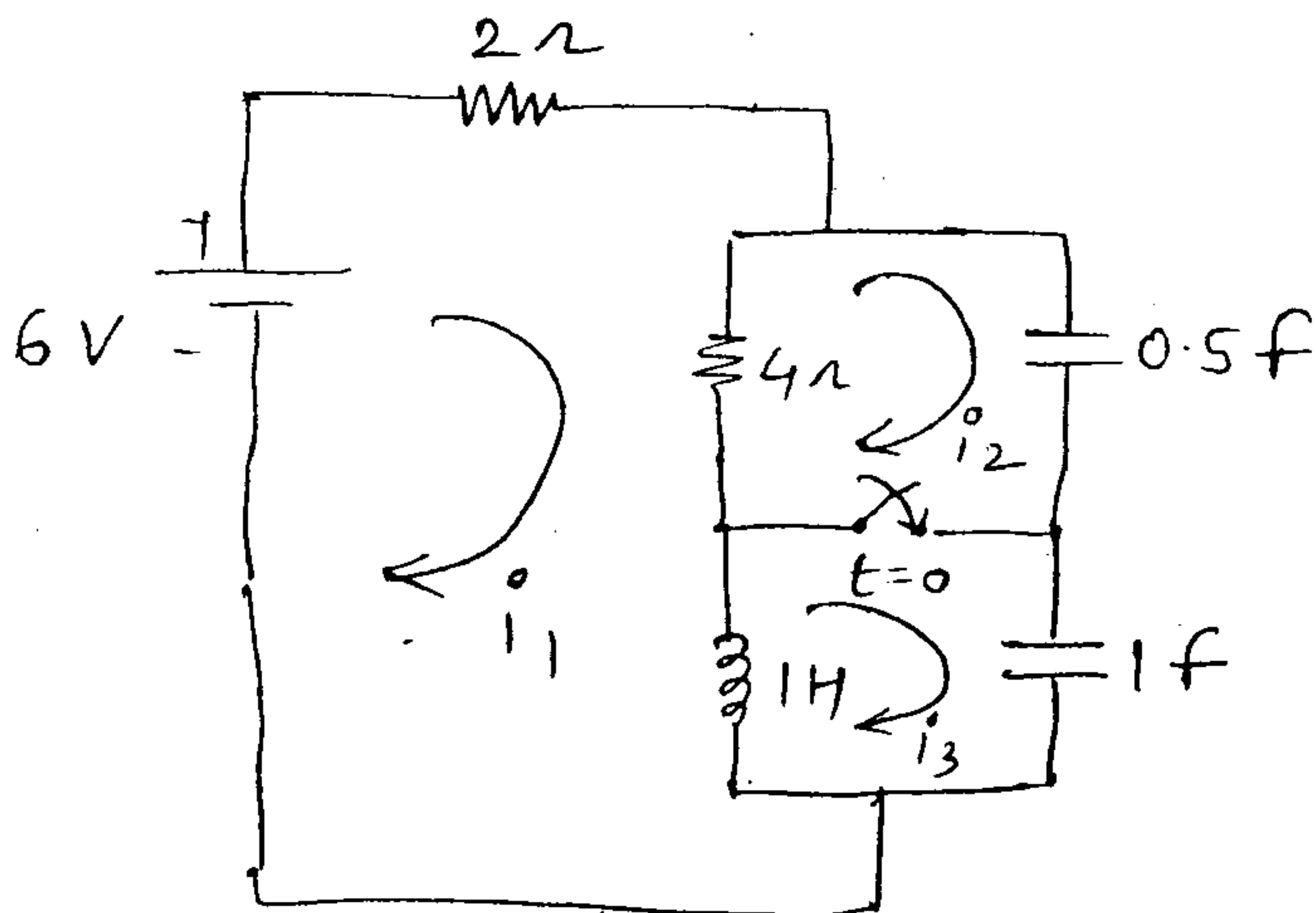


(b) Find $i(t)$ for the circuit given using Classical method :-

10

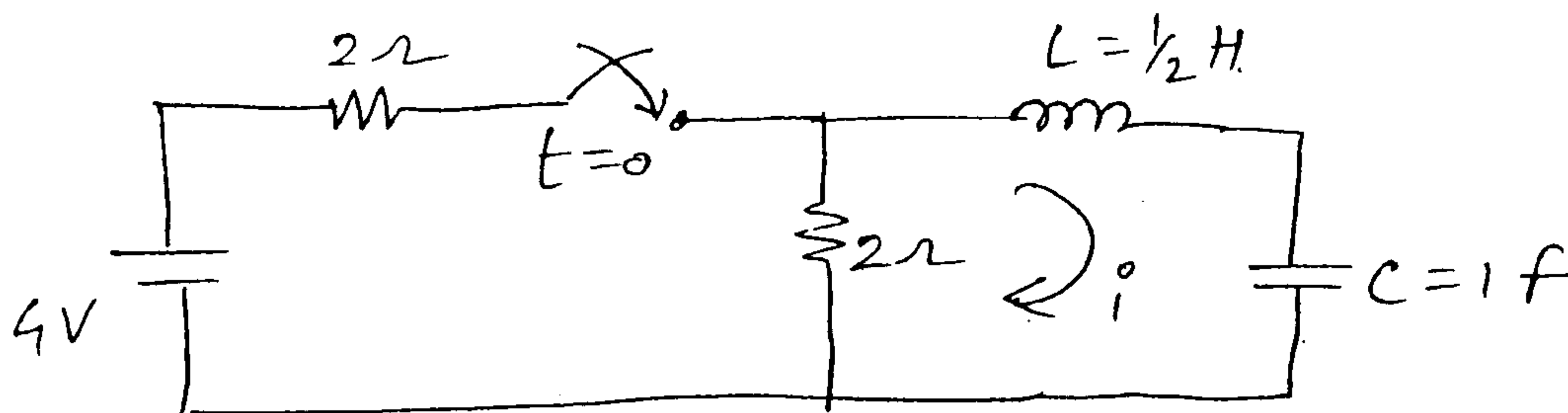


6. (a) Find Z and Y parameters :-

10

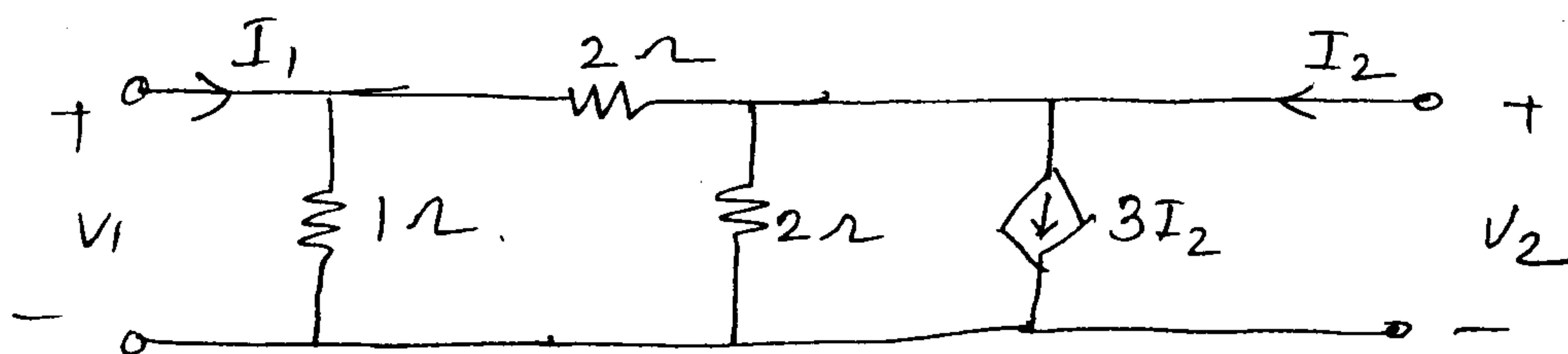

(b) Find ABCD parameter for the network shown :-

10

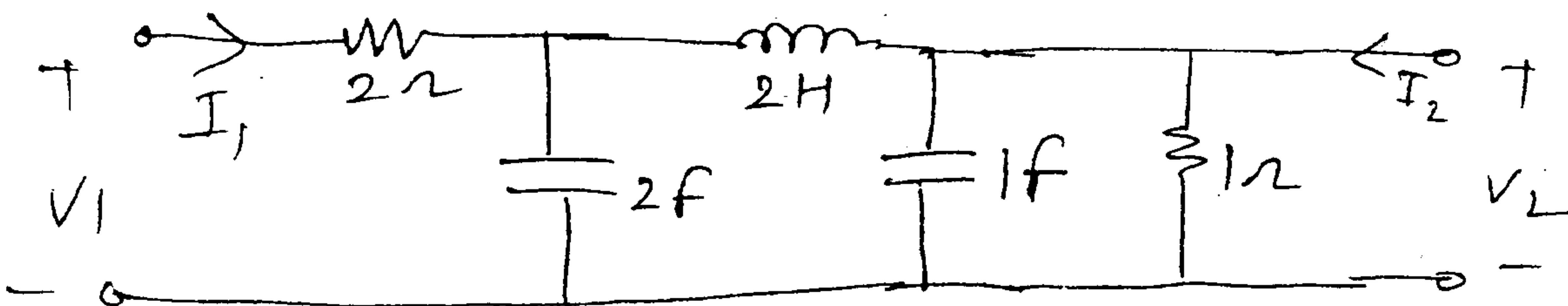

Con. 5592-LJ-10421-13.

4

7. (a) Realise the function in Foster-I and Foster-II forms :-

10

$$Y(S) = \frac{S(S+2)(S+6)}{(S+1)(S+4)(S+8)}$$

(b) Synthesize the function in Cauer-I and Cauer-II forms :-

10

$$Z(S) = \frac{S^3 + 2S}{S^4 + 2S^2 + 3}$$

Con. 6556-13.

LJ-10252

(3 Hours)

[Total Marks : 100]

- N.B. :** (1) Question No. 1 is compulsory.
 (2) Attempt any four questions out of remaining six questions.
 (3) Figure to the right indicate full marks.

1. (a) Prove that following matrix is orthogonal and hence find A^{-1} where :— 5

$$A = \begin{bmatrix} -2/3 & 1/3 & 2/3 \\ 2/3 & 2/3 & 1/3 \\ 1/3 & -2/3 & 2/3 \end{bmatrix}$$

- (b) Find $L[\sin\sqrt{t}]$ 5

- (c) Find the constants a, b, c, d if $f(z) = x^2 + 2axy + by^2 + i(x^2 + 2dxy + y^2)$ 5

- (d) Obtain Half range cosine series for $f(x) = x(0, 2)$ Using parsevis identity deduce that : 5

$$\frac{\pi^4}{96} = \frac{1}{1^4} + \frac{1}{3^4} + \frac{1}{5^4} \dots$$

2. (a) Find $L\left\{\int_0^t u^{-1} e^{-u} \sin u du\right\}$ 6

- (b) Find the Fourier expansion of $f(x) = 4 - x^2$ in the interval $(0, 2)$. 6

- (c) Find two matrices P and Q such that PAQ is in normal form where $A = \begin{bmatrix} 1 & 2 & 3 \\ 2 & 3 & 0 \\ 0 & 1 & 2 \end{bmatrix}$ 8

Hence find A^{-1} if it exist.

3. (a) Prove that the matrix $A = \frac{1}{2} \begin{bmatrix} 1+i & -1+i \\ 1+i & 1-i \end{bmatrix}$ is unitary. 6

- (b) Use Green's Theorem to evaluate $\int_0^{\pi/2} (e^{-x} \sin y dx + e^{-x} \cos y dy)$ where C is the rectangel 6

whose vertices are $(0, 0), (\pi, 0), (\pi, \pi/2), (0, \pi/2)$.

- (c) Use Laplace Transform to solve $(D^2 - D - 2)y = 1$ Where $y(0) = 1, y'(0) = 0$ 8

[TURN OVER]

Con. 6556-LJ-10252-13.

2

4. (a) If $\{f(k)\} = \{2^0, 2^1, 2^2, \dots\}$ find $z \{f(k)\}$. 6
- (b) Find an analytic function whose Real part is $u = x^3 - 3xy^2 - 3x^2 - 3y^2 + 1$ 6
- (c) Find the Fourier expansion of $f(x) = x + n^2$ When $-\pi \leq x \leq \pi$ and hence deduce that 8
- $$\frac{\pi^2}{6} = \frac{1}{1^2} + \frac{1}{2^2} + \frac{1}{3^2} + \dots$$
5. (a) If $V = e^x \sin y$ prove that V is a harmonic function. Also find the corresponding analytic 6
function and harmonic conjugate.
- (b) Find the finite Fourier sine transform of $\sin kx$ if k is not an integers and $0 < x < \pi$. 6
- (c) Find: (i) $L^{-1} \{\tan^{-1}(a/s)\}$ (ii) $L^{-1} \frac{s^2 + 2s + 3}{(s^2 + 2s + 5)(s^2 + 2s + 2)}$. 8
6. (a) Solve the equations $x + y + z = 3$, $x + 2y + 3z = 4$, $x + 4y + 9z = 6$ 6
- (b) Obtain complex form of Fourier series for $f(x) = e^{ax}$ in $(-1, 1)$ 6
- (c) Prove that $\bar{F} = (y^2 \cos x + z^3) i + (2y \sin x - 4) j + (3xz^2 + 2) k$ is conservative field. 8
Find (i) Scalar potential (ii) the work done in moving an object in this field from $(0, 1, -1)$
to $(\pi/2, -1, 2)$
7. (a) If $S = \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$ and $A = \frac{1}{2} \begin{bmatrix} 5 & 2 & 1 \\ 1 & 4 & -1 \\ -1 & -2 & 3 \end{bmatrix}$. Find SAS^{-1} . 6
- (b) Evaluate using LT $\int_0^\infty \int_0^t \frac{e^{-t} \sin y}{u} du dt$. 6
- (c) Find the bilinear transformation, which maps $z = -1, 1, \infty$, on to the Points $w = -i, -1, i$. 8

Basic Electronic Circuits.

shilpa-2nd half-(b)13-46

Con. 5411-13.

(OLD COURSE)


LJ-10283

(3 Hours)

[Total Marks : 100]

N. B. : (1) Question No. 1 is **compulsory**.(2) Solve any **four** questions from remaining **six** questions.(3) Assume any **suitable** data wherever **required**.

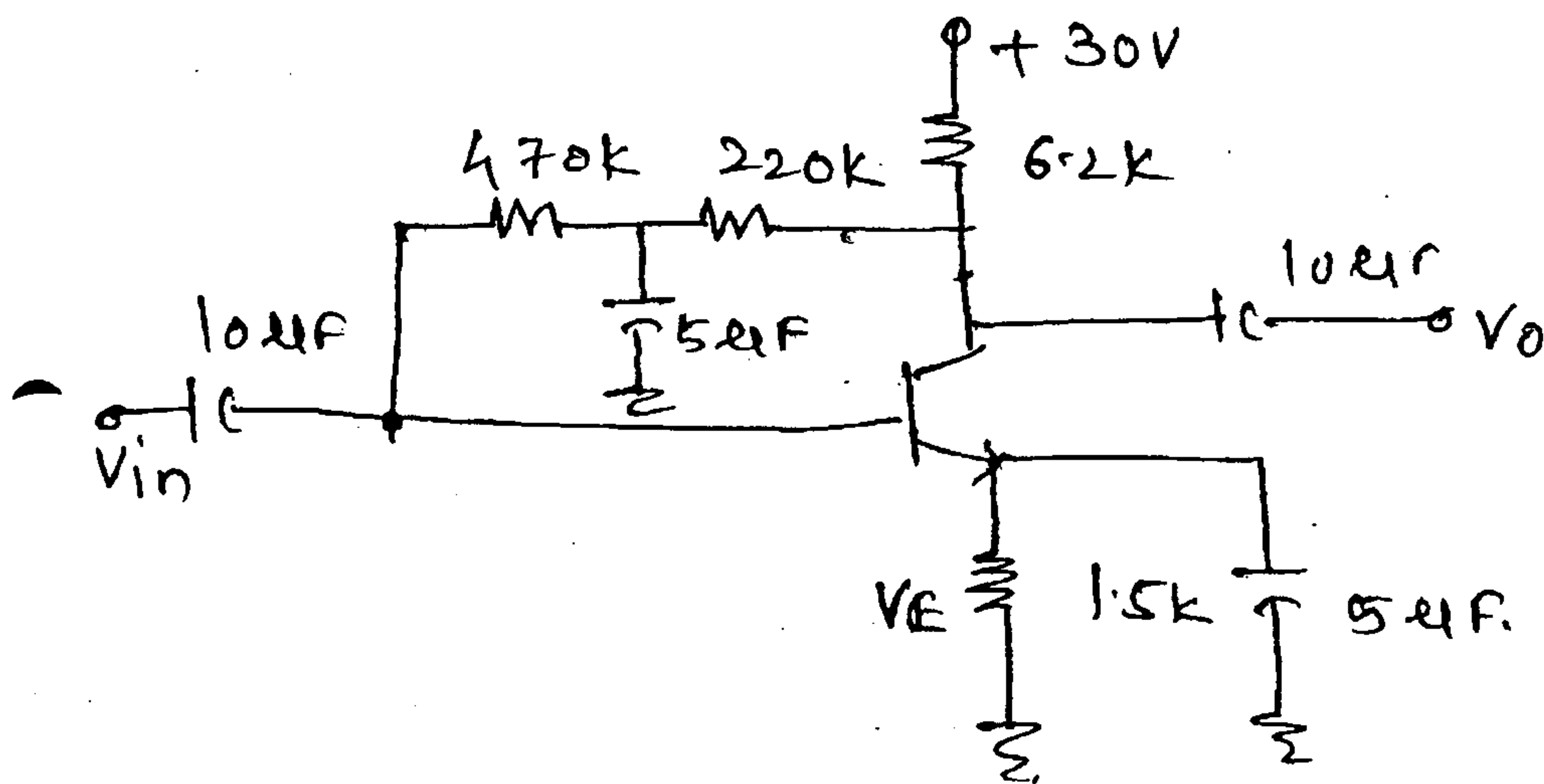1. (a) Explain the Phenomenon of thermal runaway of BJT. 5
 (b) Derive the condition for zero temperature drift biasing of FET. 5
 (c) Derive the relationship between α and β . 5
 (d) Draw a circuit diagram of voltage multiplier and explain its operation. 5
2. (a) Draw and explain fullwave rectifier with capacitive filter. Derive expression for ripple factor. 10
 (b) For the circuit shown in **figure**. Determine – 10
- (i) I_c (iii) V_E
 (ii) V_c (iv) V_{CE}




$$\beta_{dc} = 100$$

3. (a) Design single stage CE amplifier for the following specifications – 15
 $A_v \geq 100$, $S = 8$ $V_o = 2.5$ V
 $F_L = 20$ Hz, $Z_i = 2.7$ k Ω
- (b) Determine A_v , Z_i and Z_o for the designed circuit. 5


[TURN OVER

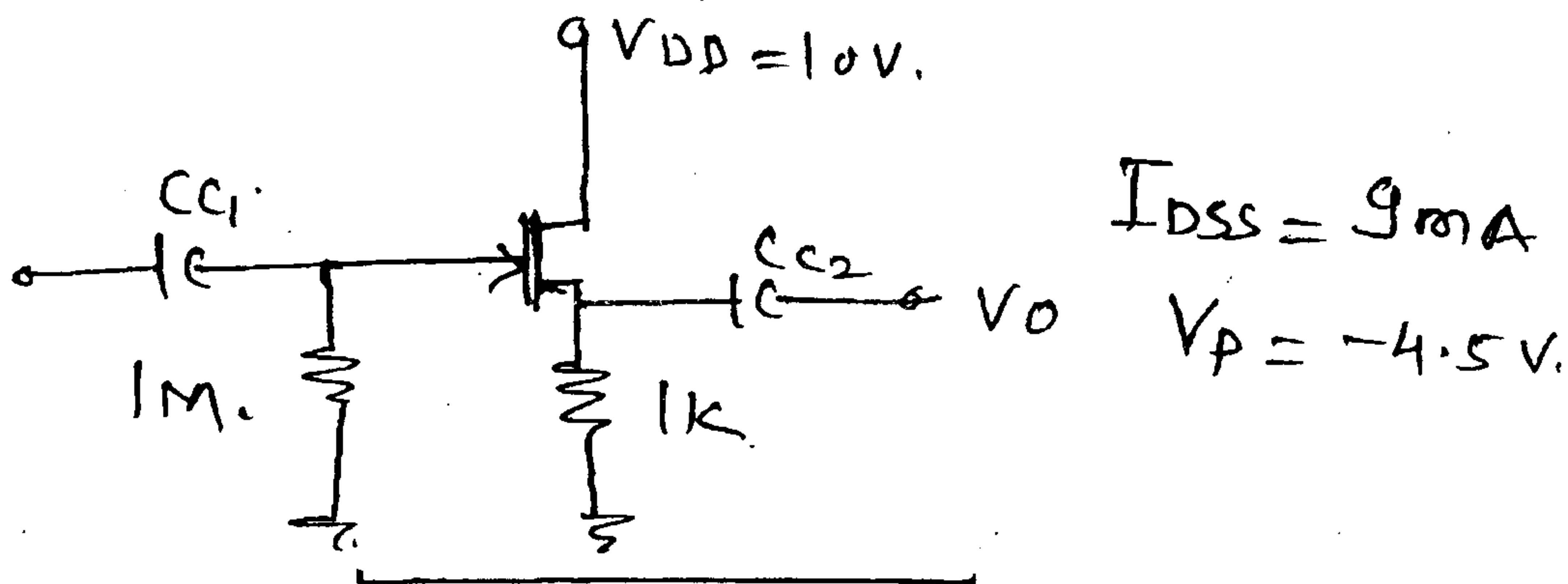4. (a) For the circuit shown in figure find A_v , R_i and R_o . 10




(b) Explain different biasing techniques of D and E MOSFET. 10

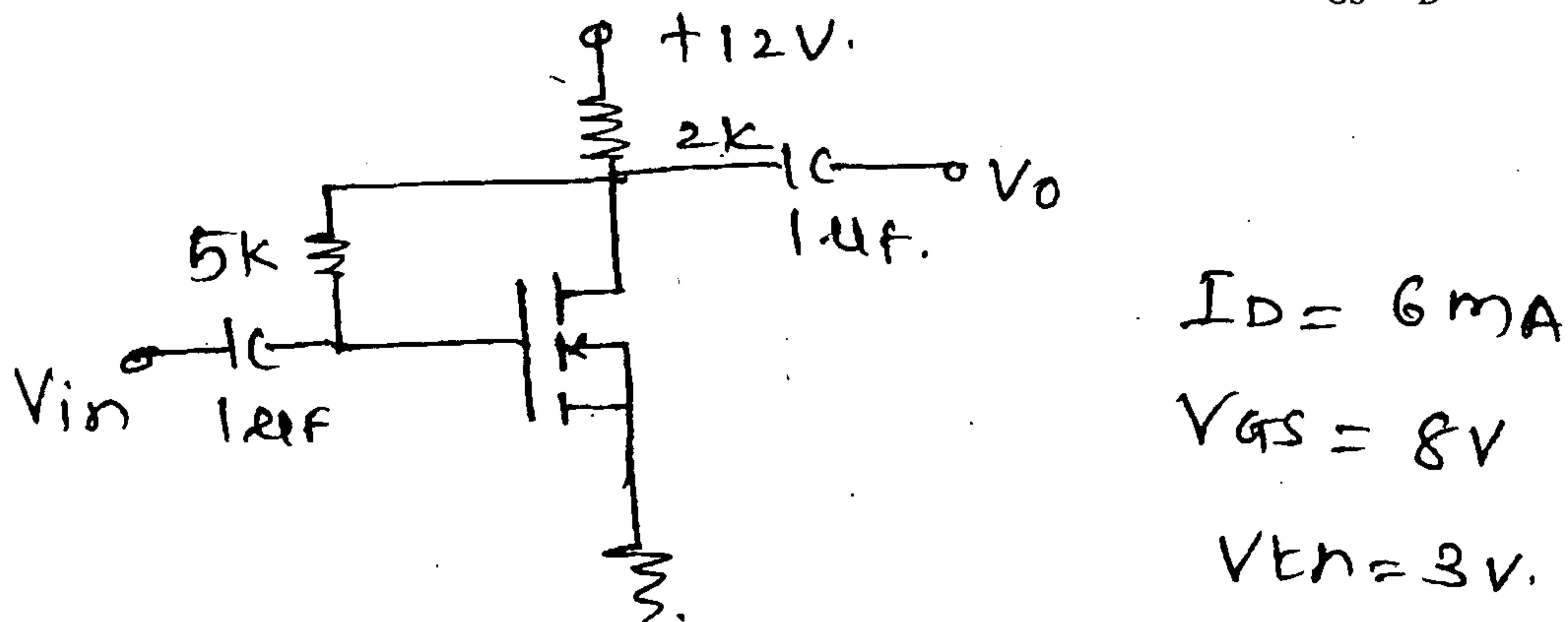5. (a) For drain Feedback circuit shown in figure determine V_{GS} , I_D and V_{DS} . 10



(b) Explain the construction, working principle and characteristics of DMOSFET. 10

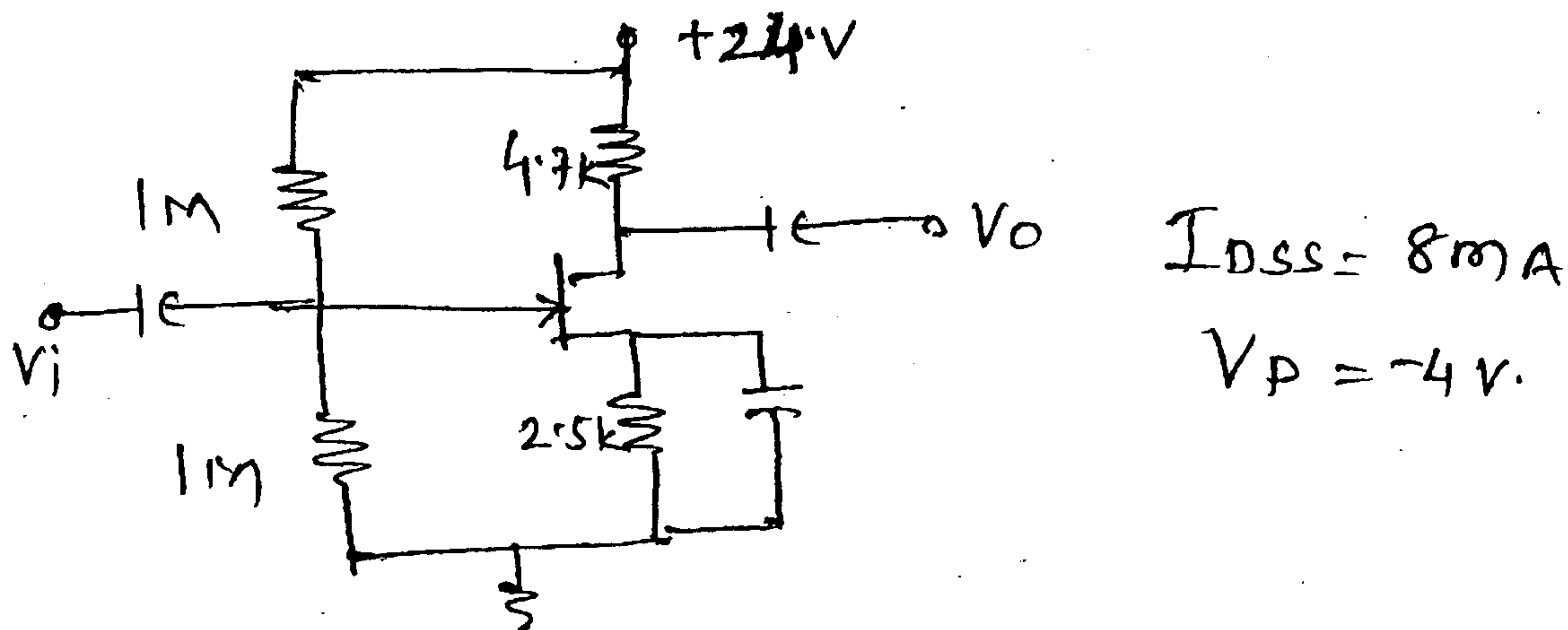6. (a) For the circuit shown in figure determine A_v , R_i and R_o . 10



(b) Explain thermal stability in BJT. How to active it? 10

shilpa-2nd half-(b)13-48

Con. 5411-LJ-10283-13.

3

7. Write a short notes (any **three**) :-

20

- (a) LED
- (b) Photodiodes and Photovoltaic cells
- (c) Zener as a voltage regulator
- (d) Diode clamping circuits.
