


(REVISED COURSE)

(3 Hours)

[Total Marks : 100


- N.B. (1) Question No. 1 is compulsory.
 (2) Attempt any four questions out of remaining six questions.
 (3) Assumption made should be clearly stated.

- | | | |
|----|---|----|
| 1. | (a) Compare Active and Passive filter. | 5 |
| | (b) Compare Butterworth, Chebyshev and Elliptic magnitude approximations. | 6 |
| | (c) Explain the principle of realization of a resistor in a switched capacitor filter. | 5 |
| | (d) Explain with an example, how higher order (more than two) active filters are realized. | 4 |
| 2. | (a) Derive voltage transfer function for a general single amplifier active filter. | 10 |
| | (b) For the n/w, find the normalised voltage transfer function and the frequency denormalized voltage transfer function, when the centre frequency changed to 10 ⁴ Hz, find the corresponding element values and draw the circuit. | 10 |

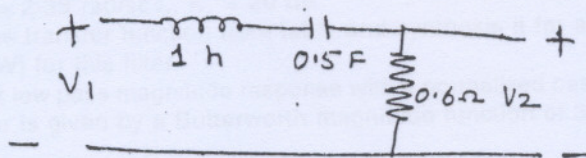

- | | | |
|----|---|----|
| 3. | (a) Show that driving point admittance at port 1 has the poles that are same as that of the voltage transfer function | 10 |
|----|---|----|

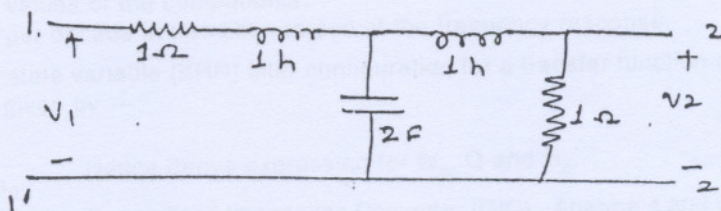transfer function $\frac{V_2(s)}{V_1(s)}$



- | | | |
|-----|--|----|
| (b) | Determine the order of Butterworth response that realise the following specification and also find the Butterworth function.
$w_p = 1 \text{ rad/sec}$ $k_p = 3\text{dB}$
$w_s = 2 \text{ rad/sec}$ $k_s = 15\text{dB}$. | 10 |
| 4. | (a) By using method of constraint derive the expression for voltage transfer function of a finite gain high pass Sallen-Key filter. | 10 |
| | (b) Design equal resistance, equal capacitance high pass filter with $Q = 0.707$ and cutoff frequency of 5 KHz. Draw the circuit | 10 |
| 5. | (a) Derive transfer function for a second order infinite gain low pass single amplifier filter. Hence realize an infinite gain single amplifier filter for following specification.
$f_n = 1 \text{ KHz}$, $Q = 0.707$, $ H_0 = 5$ Choose $C = 0.01 \mu\text{F}$ | 12 |
| | (b) Explain how a leap-frog structure is developed. | 8 |
| 6. | (a) Derive the expression for a state variable configuration using three amplifier. Specify the expression for L_p , H_p and B_p output. | 10 |
| | (b) Explain and draw neat circuit digram of inverting, non inverting and lossy integrators using parasitic insensitive switched capacitors. | 10 |
| 7. | (a) What is Biquadratic function. | 8 |
| | (b) Draw and explain 'Tow Thomas Biquadratic filter'. Derive relation for voltage transfer function, if it is used as a high pass filter. | 12 |