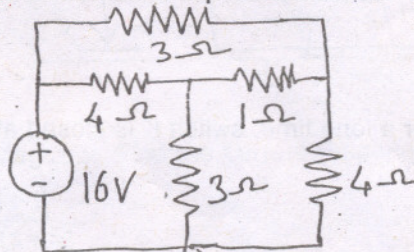


- N.B.** (1) Question No. 1 is **compulsory**.
 (2) Attempt any **four** questions out of remaining **six** questions.
 (3) In all solve **five** questions.

1. Solve all :—


- (a) Find Thevenin's resistance equivalent across 1 ohm resistance :—

3




- (b) For the circuit shown in figure, find I_1 , I_2 and I_3 :—

3

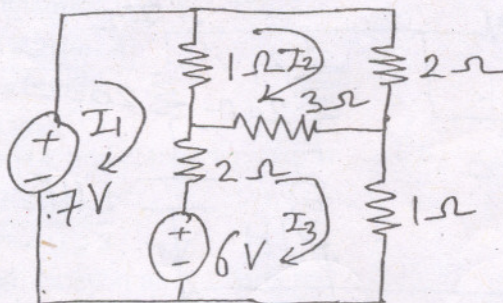


- (c) Draw the dual circuit for the network shown below :—

4

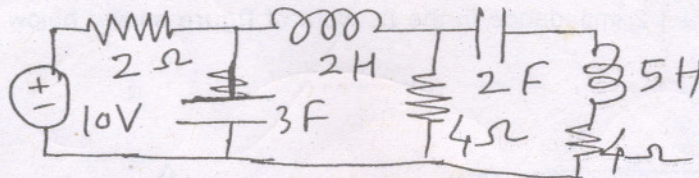

- (d) What is the time constant of the circuit ?

4

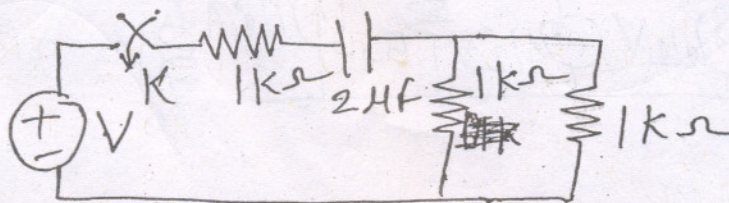


- (e) Find the Laplace transform of decaying exponential function.
 (f) Explain initial condition for inductor and capacitor.

3

3


2. (a) Find current I_3 in the **figure** shown below by Loop Analysis.

10

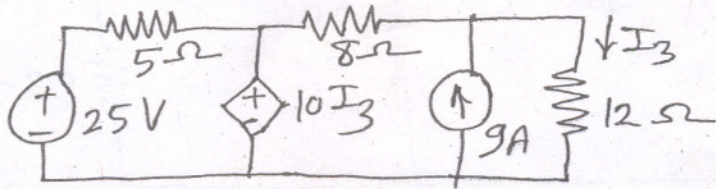

(b) Using Superposition Theorem determine V_a and V_b for the network shown below :—


10

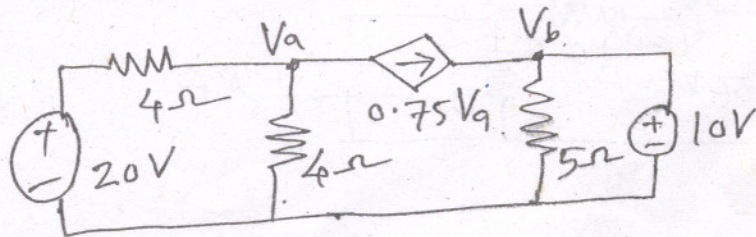

[TURN OVER


3. (a) Find the value of R_L to get the maximum power. Also find that power :—

10

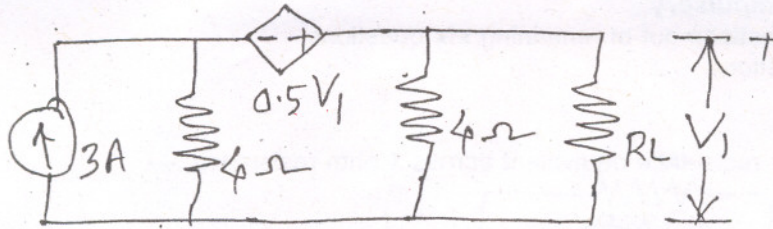


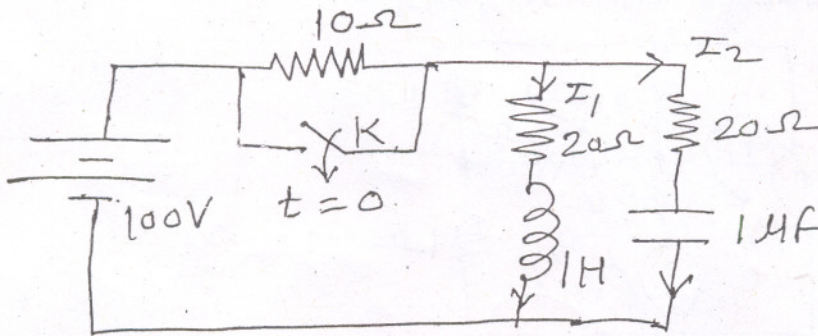(b) In the network given the switch (K) is open for a long time, switch K is closed at $t = 0$. Determine I_1 , I_2 , $\frac{dI_1}{dt}$, $\frac{dI_2}{dt}$ at $t = 0^+$. 10

$I_2, \frac{dI_1}{dt}, \frac{dI_2}{dt}$ at $t = 0^+$.




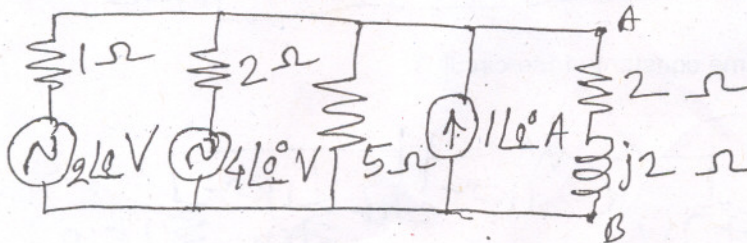4. (a) Find the current in the $2 + j 2$ impedance in the network of figure shown below. Use Thevenin's Theorem :— 8




(b) For the circuit shown below. Draw the oriented graph and write :— 12

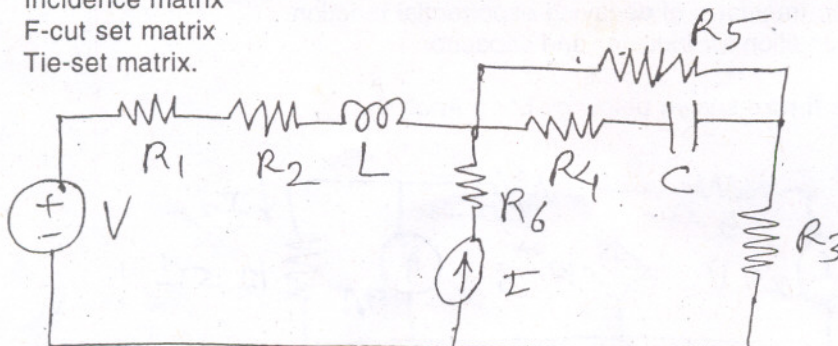- (i) Incidence matrix
- (ii) F-cut set matrix
- (iii) Tie-set matrix.



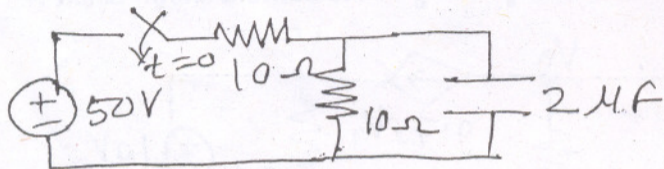
5. (a) In the circuit of **figure** below. Determine V_C (Voltage across capacitor). 10



- (b) Draw Bode plot for — 10

$$\frac{50(1+0.02s)}{s(1+0.05s)}$$

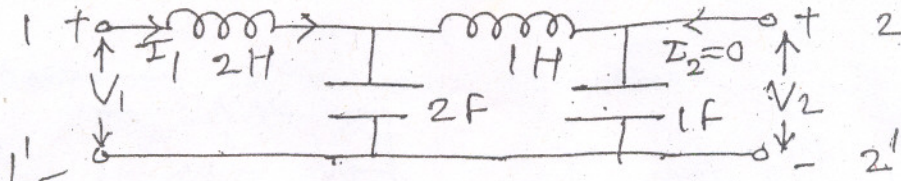6. (a) Find the open circuit transfer impedance V_2/I_1 and open circuit voltage ratio V_1/V_2 for the following Ladder network :— 10



- (b) Using pole, zero diagram. Find the current response in time domain if :— 10

$$I(s) = \frac{4s(s+1)}{(s+2)(s+5)}$$

7. (a) Synthesize the following function :— 8

$$Z(s) = \frac{6(s+2)(s+4)}{s(s+3)}$$

Use Foster-II Method.

- (b) A deriving point R-L admittance function is given by — 6

$$Y_{RL}(s) = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$$

Realize the given function as R-L form using Cauer-I

- (c) Synthesize the following $Y_{RL}(s)$ using Cauer-II term — 6

$$Y_{RL}(s) = \frac{(s+1)(s+4)}{s(3s+4)}$$