 


- N.B. (1) Question No. 1 is compulsory.
(2) Attempt any four out of remaining six questions.

1. (a) Analyze the clocked synchronous machine given below. Write excitation equations, excitation/transition tables and state/output table. 10




- (b) Design a MOD-100 counter using IC 7493. 10

2. (a) Design a coin operated vending machine that dispenses chocolates under the following condition :- 12
(i) The machine accept Re. 1 and Rs. 2 as coins.
(ii) It takes Rs. for a chocolate to be released from machine.
(iii) If Rs. 4 is deposited, the machine will credit the buyer with Re. 1 and wait for the buyer to make a second purchase.


Follow all the steps including state decomposition and state assignment in designing a MOORE machine.

- (b) Draw a switch debouncer using NAND gates and explain. 8

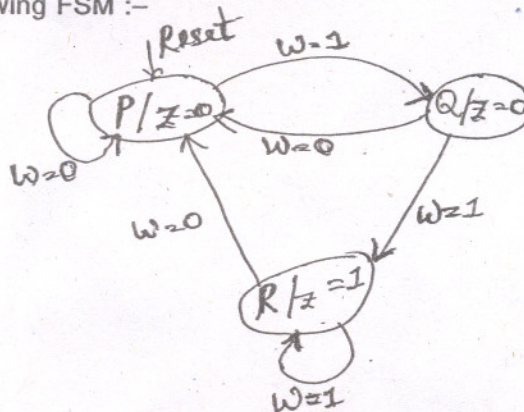3. (a) Draw and Explain the logic diagram for 8×4 diode ROM. 10
(b) Write the VHDL code for the following FSM :- 10



 4. (a) Design a asynchronous counter using JK flip-flops which goes through a sequence of :- 10



Flipflop responds to the negative edge of a clock pulse. The counter should reset to zero state whenever it encounters an unused state.

- (b) Draw the universal state diagram for a 4 bit serial in parallel out right shift register. Using it to design a twisted ring counter. 10

5. (a) Write a VHDL program for a 8 bit bidirectional shift register. 10
(b) Examine the working of a SRAM cell. Also show how an array of the cells form a SRAM block and so a memory unit. 10

6. (a) Give the main features of Xilinx XC 9500 CPLD family. **10**
- (b) Discuss the main issues related to the estimation of Digital System Reliability. **10**
7. Write notes on (any **two**) :- **20**
- (a) CAD Tools
 - (b) VHDL
 - (c) XC 4000 FPGA family.
-