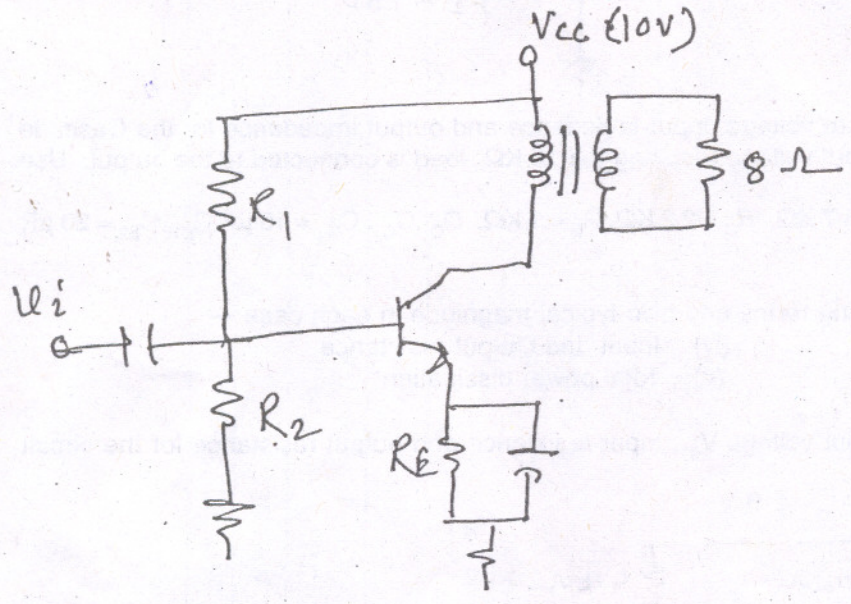


S. e. s. e. m. f.


- N.B.** (1) Question No. 1 is compulsory.
(2) Answer any four questions from remaining.
(3) Assume suitable data whenever necessary.

1. (a) Derive the expression of transformer coupled class A amplifier? What is the maximum efficiency at class A and class B transformer coupled amplifier? **6**
(b) Calculate the ac power delivered to the 8 Ω speaker, dc input power, power dissipated by the transistor and efficiency of the circuit shown in figure. **8**



$V_{CEQ} = 10 \text{ V}$
 $I_{CEQ} = 140 \text{ mA}$
 $V_{CE \text{ min}} = 1.7 \text{ V}$
 $V_{CE \text{ max}} = 18.3 \text{ V}$
 $I_C \text{ min} = 25 \text{ mA}$
 $I_C \text{ max} = 255 \text{ mA}$

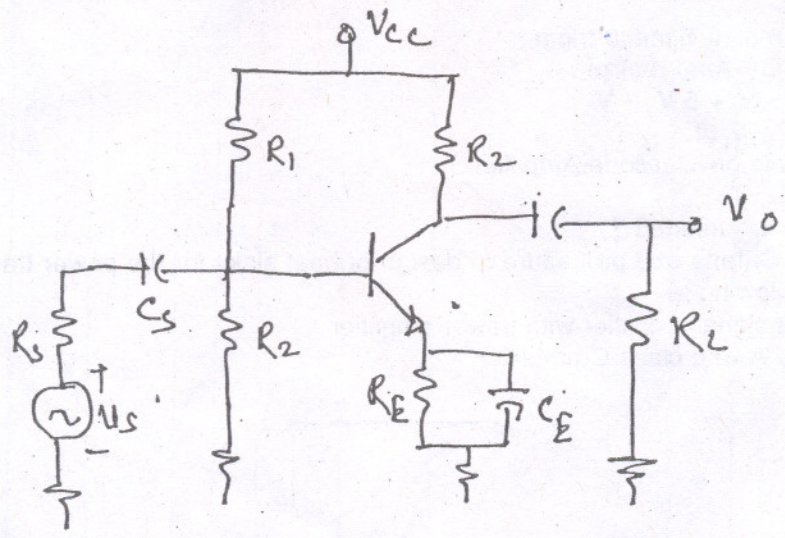- (c) Determine the input power, output power and circuit efficiency for a class B amplifier providing a 20 V peak signal to a 16 Ω load and power supply at $V_{CC} = 30 \text{ V}$. **6**
 2. (a) Determine the lower cutoff frequency for the network of figure :- **15**



$C_S = 10 \mu\text{f}$, $C_E = 20 \mu\text{f}$, $C_C = 1 \mu\text{f}$
 $R_S = 1 \text{ K}\Omega$, $R_1 = 40 \text{ K}\Omega$, $R_2 = 10 \text{ K}\Omega$, $R_E = 2 \text{ K}\Omega$
 $R_C = 4 \text{ K}\Omega$, $R_L = 2.2 \text{ K}\Omega$
 $\beta = 100$, $\xi_0 = \infty \Omega$, $V_{CC} = 20 \text{ V}$


Sketch the frequency response using Bode plot.

- (b) State and explain Miller Theorem. How it is useful to determine the frequency response of amplifier? **5**


3. (a) Draw the circuit diagram of Wien Bridge Oscillator and explain its working. Derive the equation for frequency of oscillation ? 10
- (b) Design a phase-shift oscillator using FET (BFW 11) and feedback circuit value of $R = 10 \text{ K}\Omega$ for 1 KHz frequency. 6
- (c) What are the advantages of negative feedback on performance of amplifier ? 4

[TURN OVER

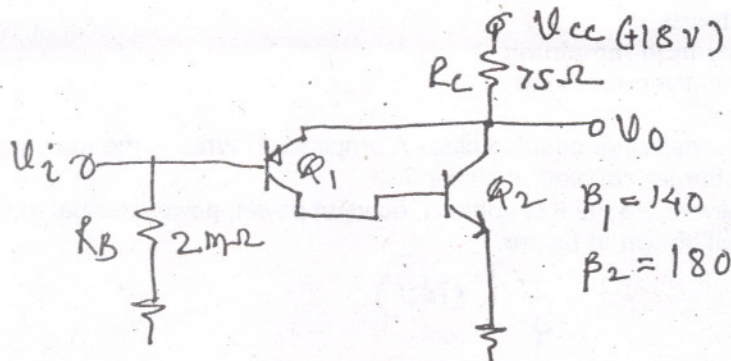4. (a) Calculate the D.C. bias currents and voltages for the figure to provide V_0 at one half the supply voltage. 5



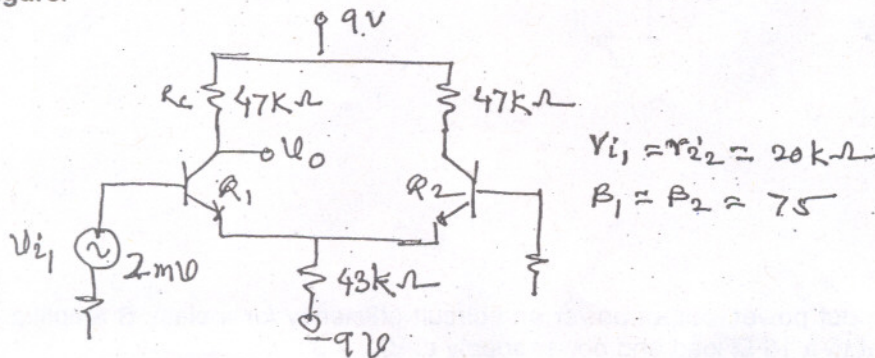- (b) Calculate the voltage gain, output voltage, input impedance and output impedance for the Cascade BJT amplifier, calculate the output voltage resulting if a $10\text{ K}\Omega$ load is connected to the output. Use following parameters :—
 $(V_i = 25\ \mu\text{V}, R_1 = 15\text{ K}\Omega, R_2 = 4.7\text{ K}\Omega, R_C = 2.2\text{ K}\Omega, R_E = 1\text{ K}\Omega, C_{C1}, C_{C2}, C_{C3} = 10\ \mu\text{F}, C_{E1}, C_{E2} = 20\ \mu\text{F}, \beta = 200, V_{CC} = +20\text{ V}).$ 15
5. (a) For OP Amp 741 explain following terms and give typical magnitude in each case — 10
- Input offset voltage
 - Slew rate
 - CMRR
 - Input and Output resistance
 - Total power dissipation.
- (b) Calculate the single ended output voltage V_{01} , input resistance and output resistance for the circuit shown in figure. 5



- (c) Explain the need of compensating networking in OP-Amp. 5
6. (a) Explain OP-Amp as a Schmitt' trigger. 6
- (b) Using practical OP-Amp realize :— 10
- $V_0 = > V_1 + 5 V_2 - V_3$
 - $V_0 = \int V_1 dt.$
- (c) Write a short note on 'Cascode Amplifier'. 4
7. (a) Why heat sinks are needed ? 10
- Explain Design Criteria and procedure of design of heat sinks for the power transistors.
- (b) Compare the following :— 10
- Small signal amplifier with power amplifier
 - Class A with class C amplifier.

DATA SHEET

Transistor type	P _{dmax} @ 25°C Watts	I _{cmax} @ 25°C Amps	V _{CE} ^(sat) volts d.c.	V _{CBO} volts d.c.	V _{CEO} (SUS) volts d.c.	V _{CER} (SUS) volts d.c.	V _{CEX} volts d.c.	V _{BE0} volts d.c.	T _j max °C	D.C. current gain			Small Signal			h _{fe} max.	V _{BE} max.	θ _{jc} °C/W	Derate above 25°C W/°C
										min	typ.	max.	min.	typ.	max.				
2N 3055	115.5	15.0	1.1	100	60	70	90	7	200	20	50	70	15	50	120	1.8	1.5	0.7	
ECN 055	50.0	5.0	1.0	60	50	55	60	5	200	25	50	100	25	75	125	1.5	3.5	0.4	
ECN 149	30.0	4.0	1.0	50	40	—	—	8	150	30	50	110	33	60	115	1.2	4.0	0.3	
ECN 100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	280	50	90	280	0.9	35	0.05	
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	220	125	220	260	0.9	—	—	
2N 525(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	65	—	45	—	—	—	—	
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	450	240	330	500	0.9	—	—	

Transistor type	h _{ie}	h _{oe}	h _{re}	θ _{ja}
BC 147A	2.7 K Ω	18 μ Ω	1.5 × 10 ⁻⁴	0.4°C/mw
2N 525 (PNP)	1.4 K Ω	25 μ Ω	3.2 × 10 ⁻⁴	—
BC 147B	4.5 K Ω	30 μ Ω	2 × 10 ⁻⁴	0.4°C/mw
ECN 100	50 Ω	—	—	—
ECN 149	15 Ω	—	—	—
ECN 055	12 Ω	—	—	—
2N 3055	6 Ω	—	—	—

BFW 11—JFET MUTUAL CHARACTERISTICS

-V _{GS} volts	0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4	2.5	3.0	3.5	4.0
I _{DS} max. mA	10	9.0	8.3	7.6	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1	0.5	0.0
I _{DS} typ. mA	7.0	6.0	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0	0.0	0.0
I _{DS} min. mA	4.0	3.0	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0

N-Channel JFET

Type	V _{DS} max. Volts	V _{DC} max. Volts	V _{GS} max. Volts	P _d max. @25°C	T _j max.	I _{DSS}	g _{mo} (typical)	-V _p Volts	r _d	Derate above 25°C	θ _{ja}
2N3822	50	50	50	300 mW	175°C	2 mA	3000 μ Ω	6	50 KΩ	2 mW/°C	0.59°C/mW
BFW 11 (typical)	30	30	30	300 mW	200°C	7 mA	5600 μ Ω	2.5	50 KΩ	—	0.59°C/mW