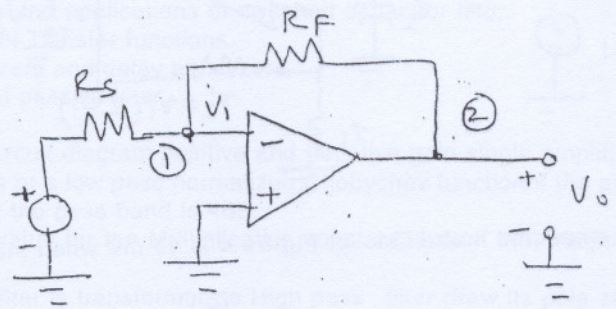


(REVISED COURSE)  
3 Hours

[ Total Marks : 100

- N.B. (1) Attempt any five questions.  
(2) Assume suitable data if necessary.  
(3) Figures to the right indicate full marks.

1. (a) Find the function  $V_o/V_{IN}$  for the operational amplifier circuit shown in Figure 1. 10



(b) Sketch the gain versus frequency for the voltage transfer function : 10

$$T(s) = 10 \frac{s^2 + 16}{s^2 + 2s + 100}$$

2. (a) Find the Butterworth approximation for a Low-pass filter whose requirements are characterized by- 10

$$A_{max} = 0.5 \text{ dB}, \quad A_{min} = 12, \quad \omega_p = 100, \quad \omega_s = 400$$

(b) An active RC network is known to have the following transfer function- 10

$$T(s) = \frac{s^2 + \frac{1}{R_1 C_1 R_2 C_2}}{s^2 + \frac{1}{R_3 C_3} s + \frac{1}{R_1 C_1 R_4 C_4}}$$


The network is used to realize the band-reject filter function :

$$T'(s) = \frac{s^2 + 144}{s^2 + 0.8s + 16}$$

If every resistor and capacitor increases by one percent, find-

- (i) The biquadratic parameter sensitivities at  $\omega = 3.6 \text{ rad/sec}$ .
- (ii) The component sensitivities.
- (iii) The gain deviation at  $\omega = 3.6 \text{ rad/sec}$ .

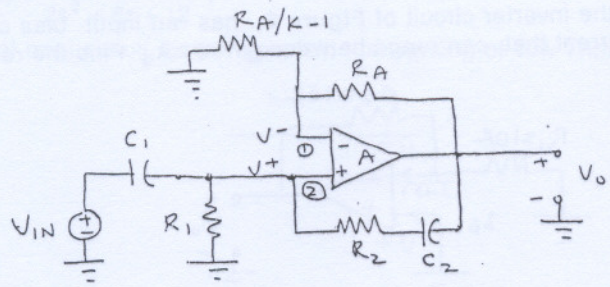3. (a) The active RC circuit shown in Figure 2 realizes a second-order high-pass function. Find it transfer function  $V_o/V_{IN}$  and derive expressions for the sensitivity of  $\omega_p$  and  $Q_p$  to elements  $R_1$ ,  $R_2$ ,  $C_1$ ,  $C_2$  and the amplifier gain A. 10



(b) Synthesize the following  $d_p$  function : 10

$$Z(s) = \frac{s^3 + 2s}{s^2 + 1}$$


4. (a) Realize the following voltage transfer function using an LC Ladder terminated in a  $1 \Omega$  resistor : 10

$$T(s) = \frac{s}{s^4 + 3s^3 + 3s^2 + 3s + 1}$$


(b) Synthesize the following Low-pass function using the positive feedback circuit shown in Figure 3 :

$$T(s) = \frac{2b}{s^2 + as + b}$$


where a and b are positive constants.

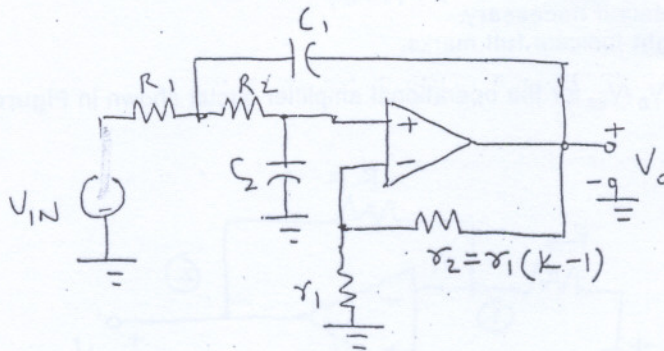

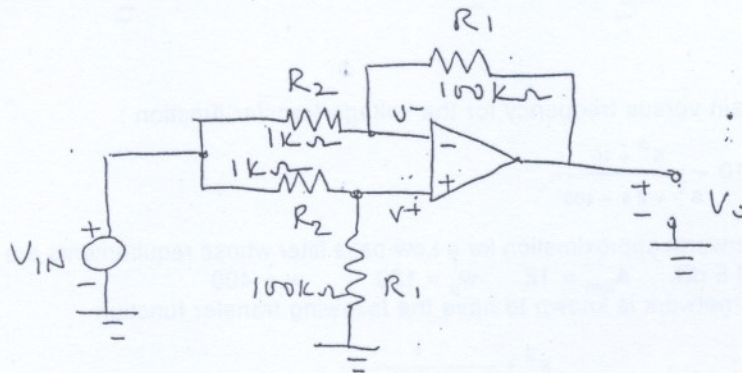
5. (a) The output voltage measured in the Ckt. of Figure 4 is 10 mV when the input voltage is 1 volt. Find the CMRR. 10



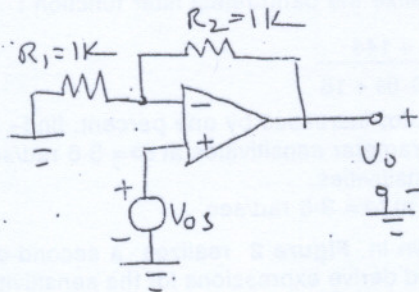(b) (i) The output offset voltage measured in the Ckt. of Figure 5 is 10 mV. What is the input-offset voltage,  $V_{OS}$ , if  $R_1 = R_2 = 10\text{ K}$ . 5



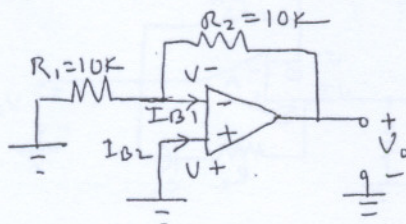(ii) The op amp used in the inverter circuit of Figure 6, has an input bias current of 500 nA and an input-offset current that can range between  $\pm 100\text{ nA}$ . Find the resulting maximum output offset voltage. 5



6. (a) By using method of constraint derive the expression for voltage transfer function of a finite gain high pass Sallen-Key filter. 10
- (b) Draw a neat circuit diagram of Akerberg-Mossberg filter and derive the expression for its voltage transfer function having low pass characteristics. 10
7. Write short notes on the following :- 20
- (a) Gain equalizers and delay equalizers.
  - (b) Generalized Impedance Converter (GIC).
  - (c) Phase approximation and Ideal transmission
  - (d) Switched capacitor filters.