

Library

- N.B. :** (1) Question No. 1 is **compulsory**.
 (2) Attempt any **four** questions from **Q. Nos. 2 to 7**.
 (3) Assume **suitable** data wherever **necessary**.
 (4) Draw **neat** sketches/circuits to support your answers.
 (5) **Figures** to the **right** indicate **full** marks.

1. (a) Explain constant current sweep generator using BJT in CB configuration. Derive the sweep speed (ss) and sweep amplitude (Vs). 10
 (b) Draw and explain the working of practical transistorised boot strap Time-base generator with its voltage and current waveform. 10
2. (a) Draw the circuit of a schmitt trigger using 555 timer and explain its operation with the input output waveforms. 8
 (b) In astable multivibrator using 555, for $R_A = 6.8 \text{ k}\Omega$; $R_B = 3.3 \text{ k}\Omega$ and $C = 0.1 \mu\text{f}$ Calculate – (i) t_{High} (ii) t_{Low} (iii) free running frequency and (iv) Duty cycle 'D'. 4
 (c) Derive the expression of time delay of a monostable multivibrator. 8
 Discuss any one application of timer in monostable mode.
3. (a) Draw the block diagram of IC 566 VCO and explain it's operation. What is the range of modulating input voltage applied to VCO. 10
 (b) Solve the following differential equation by analog computer simulation – 10

$$\frac{d^2 y}{dt^2} + 5.4 \frac{dy}{dt} + 0.58y = u(t)$$

with initial conditions :

$$y(0) = -4.8 \text{ and}$$

$$\left. \frac{dy}{dt} \right|_{t=0} = \dot{y} = 2.3$$

4. (a) What are the limitations of three terminal regulator. How those can be overcome by IC 723? Explain the remedies with functional diagram of IC 723. 10
 (b) How fixed three terminal regulator can be used as adjustable regulator? Specify suitable component values to get $V_o = 7.5\text{V}$ in adjustable regulator circuit using IC 7805; where $I_Q = 4.2 \text{ mA}$ and $I_{R_1} = 25 \text{ mA}$. 10
5. (a) Explain with circuit diagram, working of OP- Amp as monostable multivibrator with the waveforms of triggering signal, capacitor waveform and output waveform. 10
 (b) State the types of DACs depends on resistive techniques. Explain the working of one of them in details. 10
6. (a) Draw the functional diagram of IC 8038. Explain and give it's frequency of oscillation at output. 10
 (b) Explain the operation of Dual-slope ADC. Give the conversion time for the Dual-slope ADC. 10
7. Short notes on any **four** : 20
 (a) Analog MUX and D EMUX
 (b) XR - 2206
 (c) UJT sweep generator circuit
 (d) SMPS
 (e) Sample and Hold circuit
 (f) Frequency Divider using 555.