

(REVISED COURSE)

(3 Hours)


[Total Marks : 100

- N.B. : (1) Question No. 1 is compulsory.
 (2) Attempt any four questions out of the remaining six questions.
 (3) Assume any suitable data if required.
 (4) Figures to the right indicate full marks.

1. Attempt the following questions :—

(a) Construct the dual circuit for the circuit shown—

5

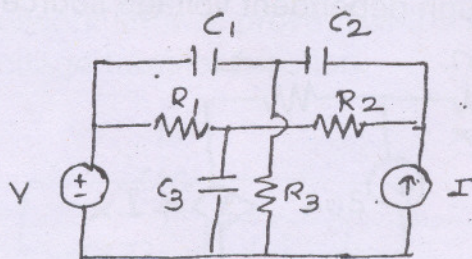

(b) Given—


5

$$A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

Draw oriented graph and show one tree.


(c) Find Thevenin's equivalent circuit of following network across A – B.

5

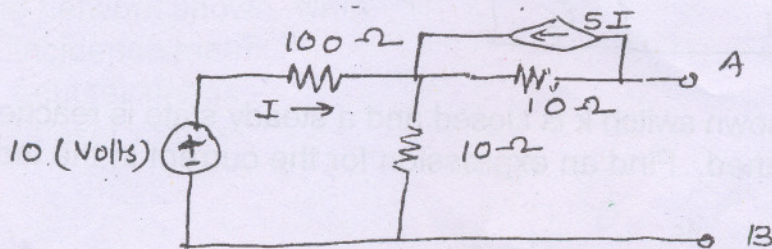


(d) For the network shown, find transfer function which relates current $i(t)$ with source current $f(t)$. Also find poles and zeros of this transfer function.


5

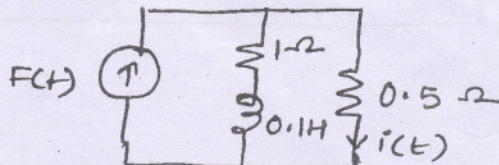

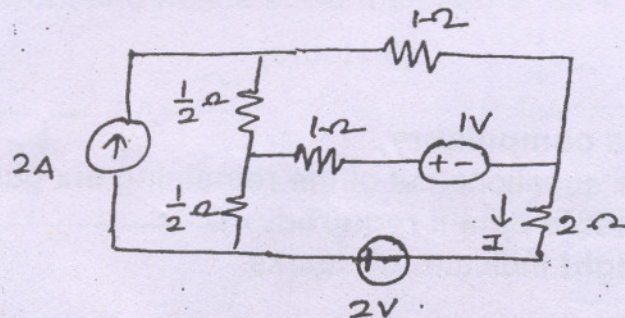
2. (a) Using source shifting and source transformation, find current I in the circuit. 10



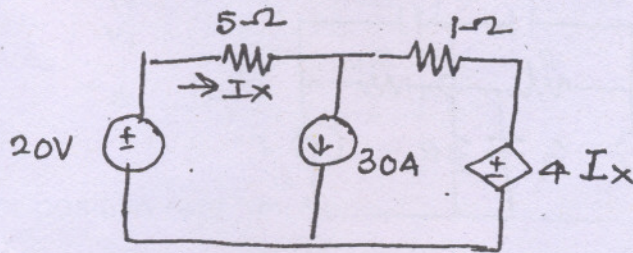
- (b) Find current I_x by superposition principle. Hence find the voltage of independent 10 voltage source and current through dependent voltage source. 10



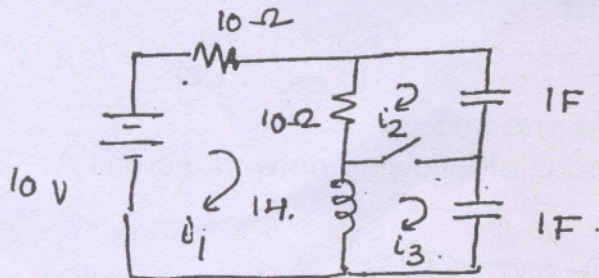
3. (a) The network shown attains steady state with the switch k open. At $t = 0$, switch 10 is closed. Determine $i_1(0+)$, $i_2(0+)$, $i_3(0+)$.



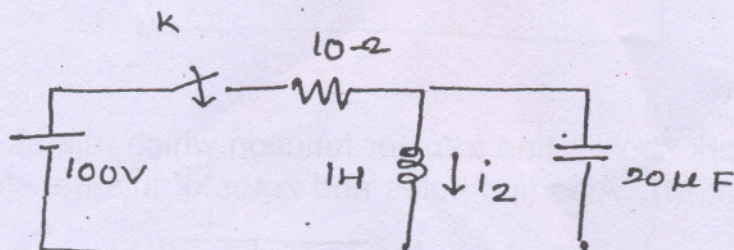
- (b) In the network shown switch k is closed and a steady state is reached. At $t = 0$, 10 the switch is opened. Find an expression for the current in the inductor, $i_2(t)$.



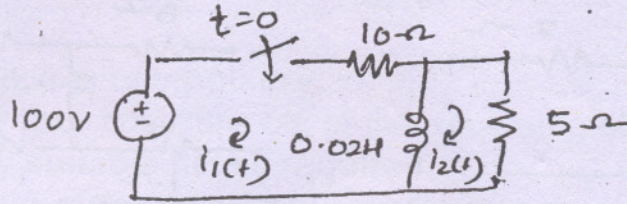
4. (a) Use a laplace transformation to find the current $i_1(t)$, $i_2(t)$ which results when the switch is closed at $t = 0$. 16




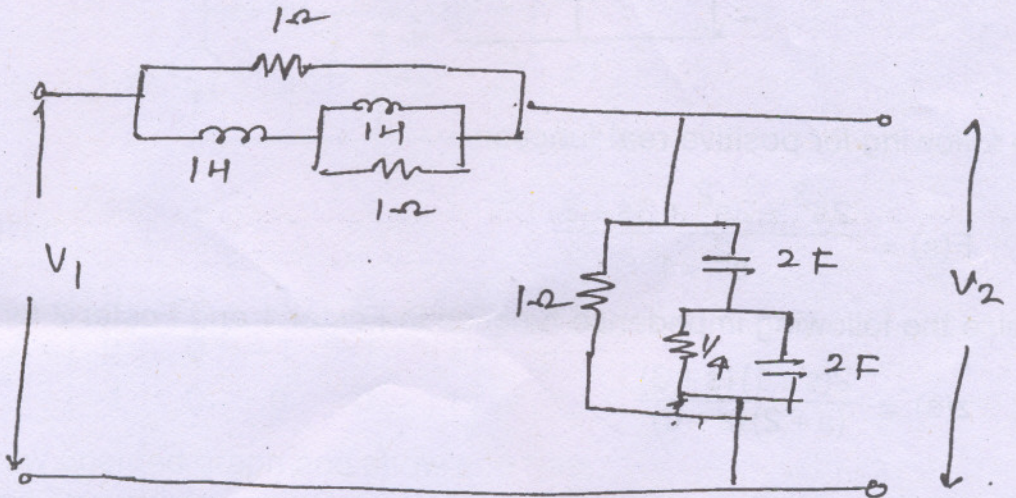
- (b) Write short note on initial condition and its significance. 4
5. (a) For the network shown, prove that the input impedance at port 1 is 1Ω . Also find the voltage transfer function. 10



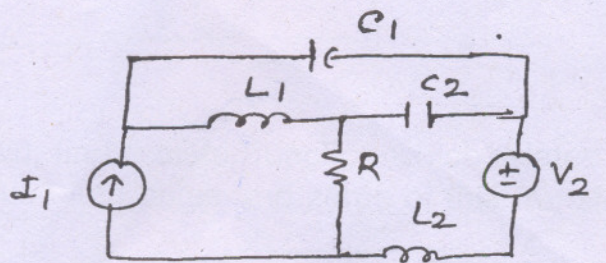- (b) For the network shown write— 10
- (i) Incidence matrix
 - (ii) f-cutset matrix
 - (iii) f-tieset matrix.




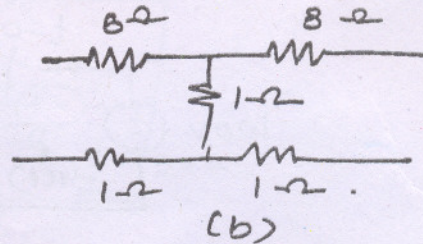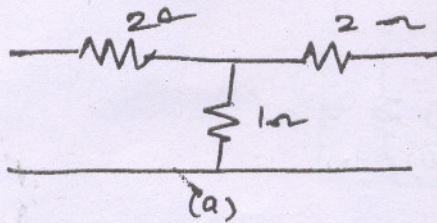6. (a) Two network 'a' and 'b' shown in figure are connected in series. find z-parameter of equivalent network and hence show that $z_{eq} \neq z_a + z_b$ why?



- (b) For the network, determine transmission parameters.

8

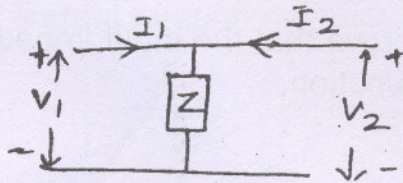

7. (a) Test the following for positive real function—

10

$$F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$$

- (b) Synthesize the following impedance function in Foster 1 and Foster 2 form—

10

$$z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$