

Electrical Network Analysis & Synthesis

Con. 2742-09.

VR-3309

(REVISED COURSE)

3 p.m. to 6 p.m.

(3 Hours)

[ Total Marks : 100

Lib

N.B.: (1) Question No. 1 is compulsory.


(2) Attempt any four questions from the remaining questions.

(3) Assume suitable data wherever required but justify the same.


1. (a) State the properties of Hurwitz polynomial. 4

(b) Express transmission parameters in terms of admittance parameter. 4

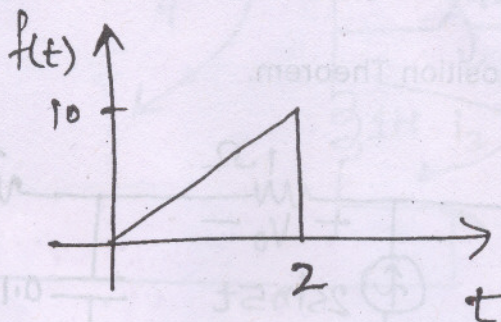(c) Find Laplace Transform of the following waveshape. 4



(d) Find  $Z(s)$  if  $Z(\infty) = 1$  4

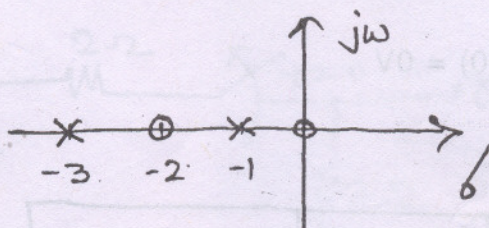

(e) For the network given determine the number of possible Trees. 4

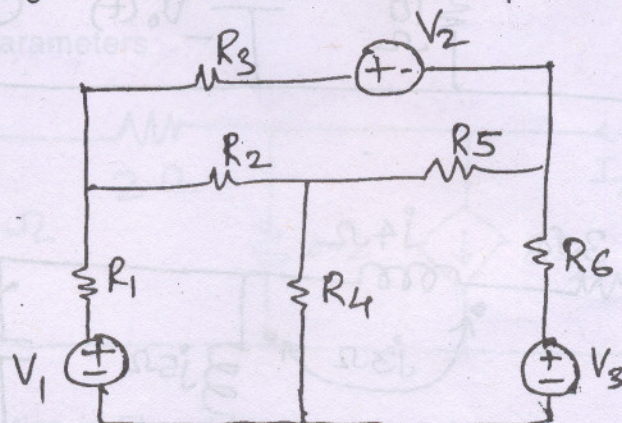


FIG. 1

2. (a) In the **Figure 1** above,

$$R_1 = R_6 = R_3 = 2 \Omega$$


$$R_2 = R_4 = R_5 = 4 \Omega$$

$$V_1 = 4V, V_2 = 6V; V_3 = 10 V$$

Write TIESET and CUTSET. Also obtain matrix KVL equation and hence determine the values of link currents.


(b) Derive the expression for  $i(t)$ .

6

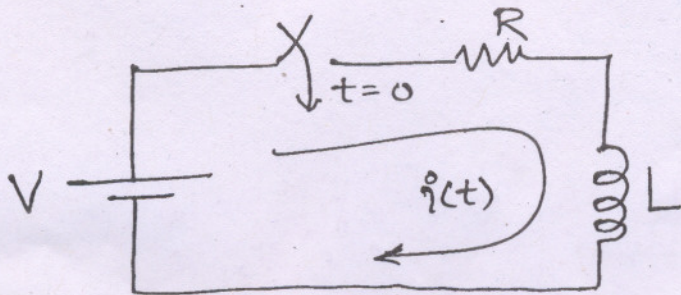


[ TURN OVER


3. (a) Find power associated with CCVS.

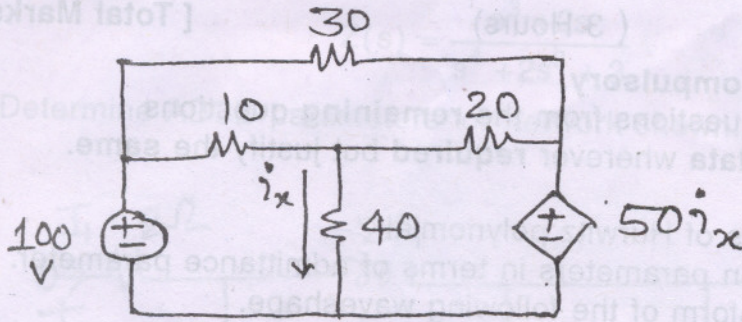

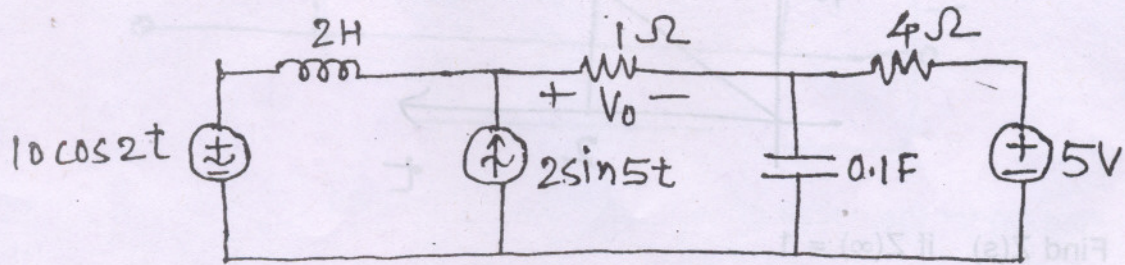
(b) Find  $V_o$  using Superposition Theorem.



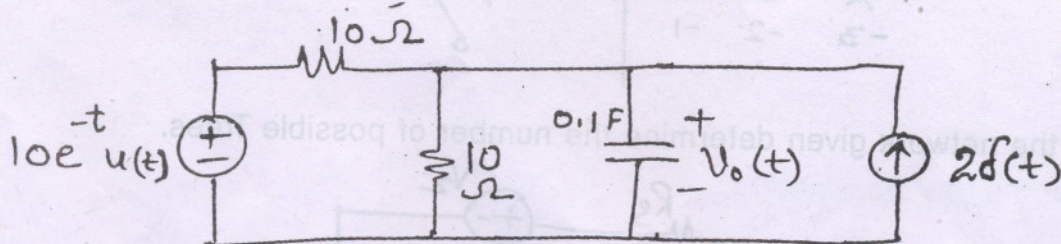4. (a) Find  $V_o(t)$ ; Assume  $V_o(0) = 0V$




(b)

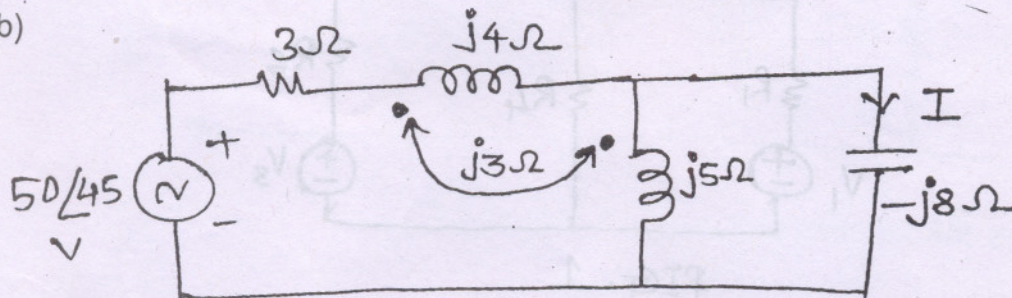

In the above circuit find I.


5. (a) Find three loop currents at  $t = 0^+$

10

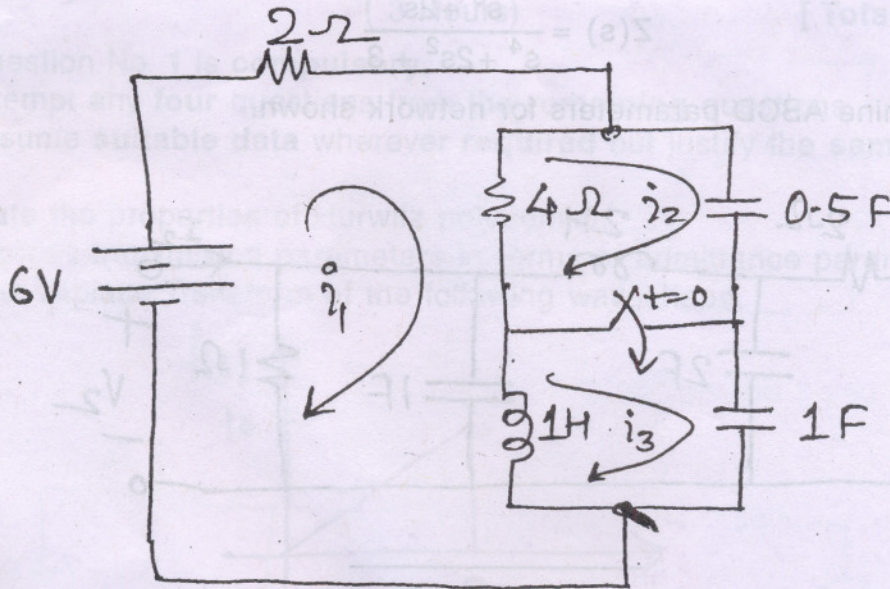


(b) Find  $i(t)$  for the circuit given using classical method.

10

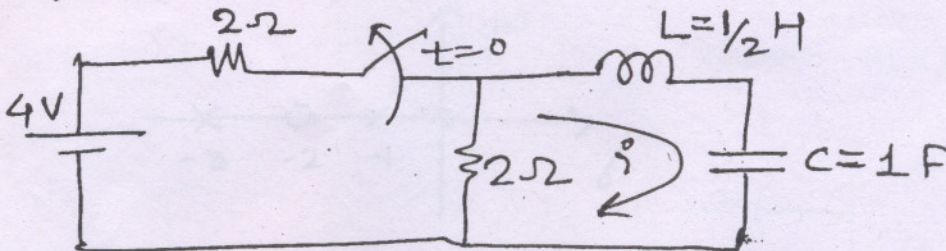

6. (a) Find Z and Y parameters

10

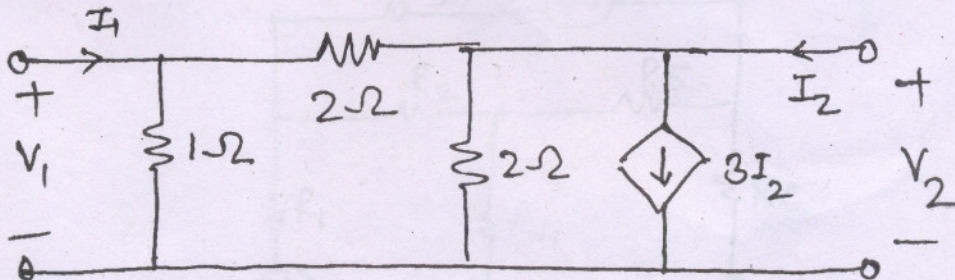

(b) Realise the function in FI and FII forms

10

$$Y(s) = \frac{s(s+2)(s+6)}{(s+1)(s+4)(s+8)}$$

7. (a) Synthesize the function for CI and CII forms

10

$$Z(s) = \frac{s^3 + 2s}{s^4 + 2s^2 + 3}$$

(b) Determine ABCD parameters for network shown.

10

