


(REVISED COURSE)

(3 Hours)

[Total Marks : 100]

- N.B.:** (1) Question Nos. 1 and 4 are compulsory.
 (2) Attempt any **three** from remaining.
 (3) Assume **suitable** additional data whenever **necessary**.
 (4) Use of **Data Sheet** given in **Last Page**.

1. Design a small signal CE amplifier to meet the following specifications : 20
 $V_o = 3.5 \text{ V(peak)}$
 $I_o = 2.47 \text{ mA}$
 $|Av| \geq 35$
 $S \leq 10$
 Lower cutoff frequency = 20 Hz.
 Find Av Z_i Z_o for designed Transistor.
2. (a) Compare series and shunt regulator circuits using BJT. 10
 (b) Explain various biasing methods of JFET and compare them for their stability. 10
3. (a) Design full wave rectifier to supply load current of $100 \text{ mA} \pm 25 \text{ mA}$ at 250 V 15
 with ripple voltage less than 10 V
 Use LC filter.
 (b) Draw and Explain UJT as relaxation oscillator also give the frequency of oscillation. 5
4. Design a single stage CS Amplifier using JFET with biasing circuit to provide stability 20
 of operating point against device variation so that $2.2 \text{ mA} \leq I_{OS} \leq 4.4 \text{ mA}$ and $|Av| = 10$.
 From the designed amplifier determine what will be the maximum output voltage that can be obtained without distortion and corresponding input voltage and input resistance.
5. (a) Find Z_o Z_i Av A_i for the network given 15

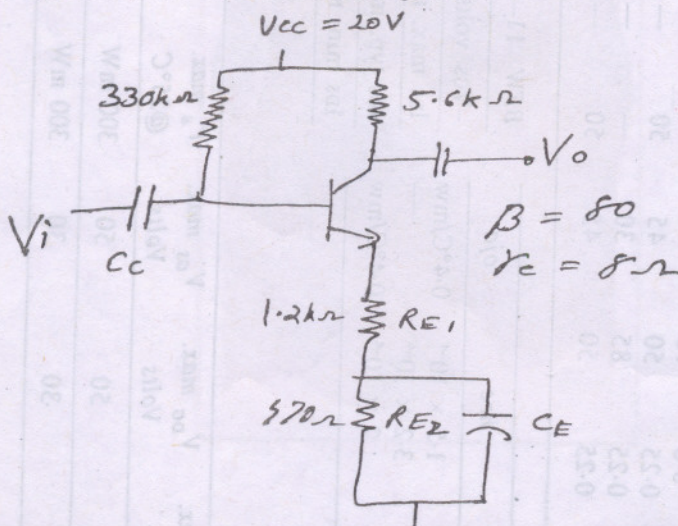

- (b) Explain the concept of Zero Temperature drift in JFET.

6. (a) For a shunt Zener regulator, giving output voltage is 10 V and load resistance 10 varying from $5\text{k}\Omega$ to $10\text{k}\Omega$. V_{in} is varying between 18 to 22V. Find :

(i) R series resistance

(ii) P_2 (max)

(iii) S_V

(iv) R_o

Take $R_2 = 4\ \Omega$ $I_{2(\min)} = 50\ \mu\text{A}$.

(b) Explain the concept of Thermal runaway in BJT. 5

(c) Explain Latching current and holding current in SCR. 5

[TURN OVER

DBEC DATA SHEET

Transistor type	P_{dmax}	I_{cmax}	$V_{CE}^{(sat)}$	V_{CBO}	V_{CEO}	V_{CER}	V_{CEX}	V_{BEO}	T_j max	D.C. current	gain	Small Signal	h_{fe}	V_{BE} max.	θ_{jc}		
	@ 25°C Watts	@ 25°C Amps	volts d.c.	volts d.c.	(Sus) volts d.c.	(Sus) volts d.c.	volts d.c.	volts d.c.	°C							min	typ.
2N3055	115.5	15.0	1.1	100	60	70	90	7	200	20	50	70	15	50	120	1.8	1.5
ECN055	50.0	5.0	1.0	60	50	55	60	5	200	25	50	100	25	75	125	1.5	3.5
ECN149	30.0	4.0	1.0	50	40	—	—	8	150	30	50	110	33	60	115	1.2	4.0
ECN100	5.0	0.7	0.6	70	60	65	—	6	200	50	90	280	50	90	280	0.9	35
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	220	125	220	260	0.9	—
2N525(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	65	—	45	—	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	450	240	330	500	0.9	—

Transistor type	h_{ie}	h_{oe}	h_{re}	ρ_{ja}
BC 147A	2.7 K Ω	18 μ Ω	1.5×10^{-4}	0.4°C/mw
2N 525 (PNP)	1.4 K Ω	25 μ Ω	3.2×10^{-4}	—
BC 147B	4.5 K Ω	30 μ Ω	2×10^{-4}	0.4°C/mw

BFW 11—JFET MUTUAL CHARACTERISTICS

-V _{GS} volts	0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4	2.5	3.0	3.5
I _{DS} max. mA	10	9.0	8.3	7.6	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1	0.5
I _{DS} typ. mA	7.0	6.0	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0	0.0
I _{DS} min. mA	4.0	3.0	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0	0.0

N-Channel JFET

Type	V_{DS} max. Volts	V_{DG} max. Volts	V_{GS} max. Volts	P_d max. @25°C	T_j max.	I_{DSS}	g_{m0}	-V _P Volts	r_d	Derate above 25°C	
2N3822	50	50	50	300 mW	175°C	2 mA	3000 $\mu\Omega$	6	50 K Ω	2 mW/°C	0.5
BFW 11 (typical)	30	30	30	300 mW	200°C	7 mA	5000 $\mu\Omega$	2.5	50 K Ω	—	0.59

UJT type	P_d max. @25°C	I_E max. @25°C	I_P peak pulse current max.	V_{B2E} Volts max.	V_{B2B1} Volts	T_j max	η	R_{BB} K Ω	I_P	I_V					
							min.	max.	min.	typ.	Max.	max.	μ A	min.	max.
2N2646	300mW	50mA	2Amp.	30	35	125°C	0.56	0.75	4.7	7.0	9.1	5.0	—	—	—