

N.B.: (1) Question No. 1 is compulsory.

(2) Attempt any four questions from remaining six questions.

(3) Assume suitable data if necessary and state it clearly.


1. (i) The reduce incidence matrix is given below. Obtain incidence matrix. 2

$$A = \begin{bmatrix} 1 & 0 & 0 & -1 & -1 & 0 & 0 & 0 \\ -1 & 1 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

(ii) For the complete incidence matrix of Q. 1(i) draw network graph. 2

(iii) Draw pole-zero plot for following network function 2

$$Z(s) = \frac{10(s+2)}{s(s+3)(s+5)}$$

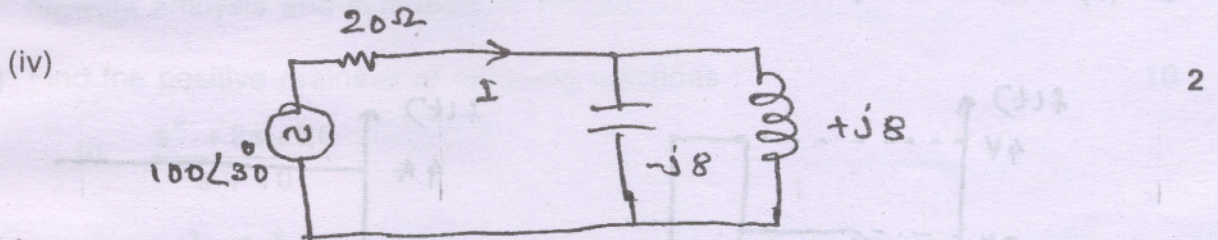


For the network shown in the figure determine I.

(v) For the Q. 1(iv) network, determine power factor angle. (Determine angle between total voltage and current) 2

(vi)


For the network shown in figure determine V (total voltage applied)

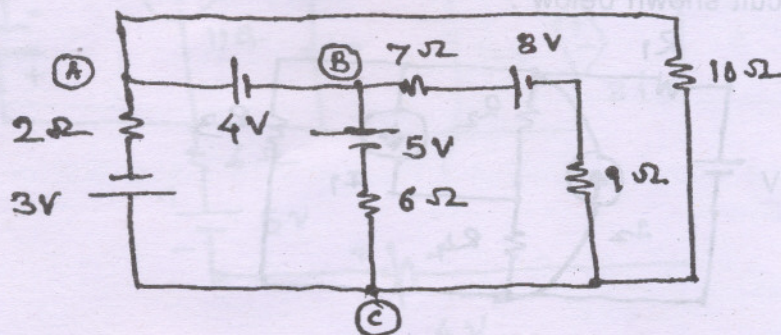(vii) For the network shown in figure below write nodal equation (KCL) at node B. 2



(viii) For the network shown below write nodal equation (KCL) at node B

2

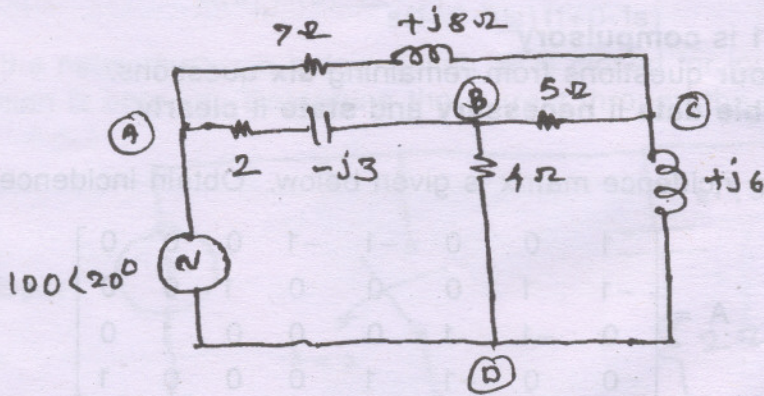

(ix) Under what condition, the transient current in R-L-C circuit is oscillatory ?


2

(x) Define driving point and transfer impedance.


2

2. (a) Determine Laplace transform of the waveforms shown in figure below :

10

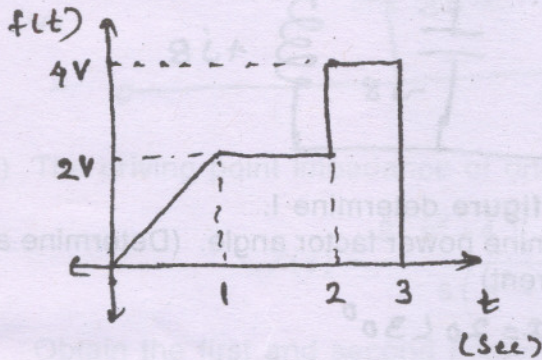

(i)

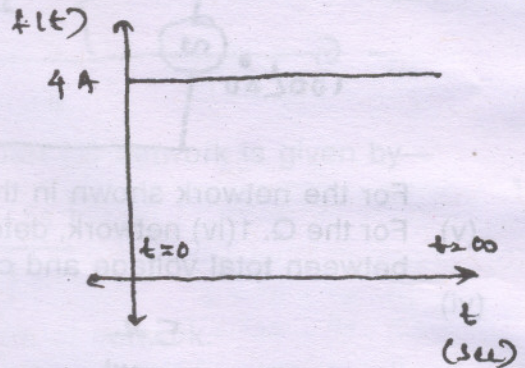

(ii)

(b) For a two port network prove that $AD - BC = 1$, where A, B, C and D are parameters of the network.


5

(c) Write a short note on equivalent circuit of given R-L-C series circuit at $t = 0^-$, $t = 0^+$ and $t = \infty$, when the circuit is excited at $t = 0$ by closing switch with non-zero initial conditions.



5

3. (a) Using principles of network topology write loop equations in the matrix form for the circuit shown below :

10

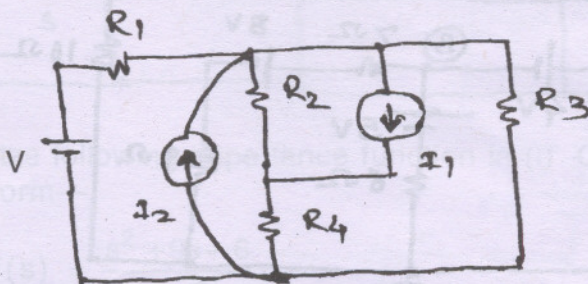

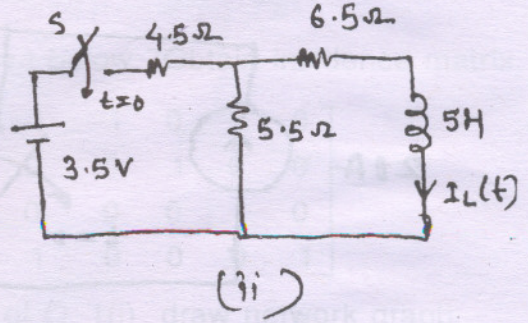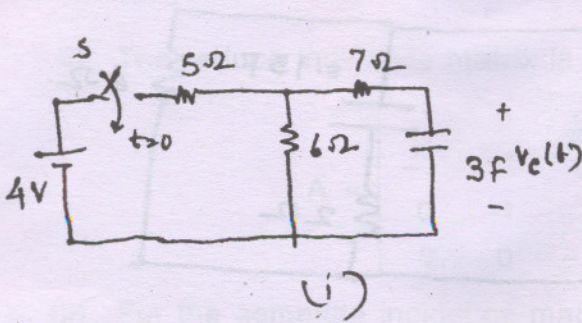- (b) For the networks shown in **figure** below determine $V_C(t)$ and $I_L(t)$ respectively. 5
 When switch 'S' is closed at $t = 0$ with zero initial conditions. (Note : Do not derive the equations used)



- (c) Explain the terms causality and stability in relation to realisability theory of network analysis and synthesis. 5

4. (a) Find the positive realness of following functions : 10

(i)
$$\frac{s^2 + 2s + 20}{s + 10}$$


(ii)
$$\frac{s^3 + 5s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$$

- (b) Check whether following Polynomials are Hurwitz or not. 5

(i) $s^5 + s^3 + s$

(ii) $s^3 + 4s^2 + 2s + 8$

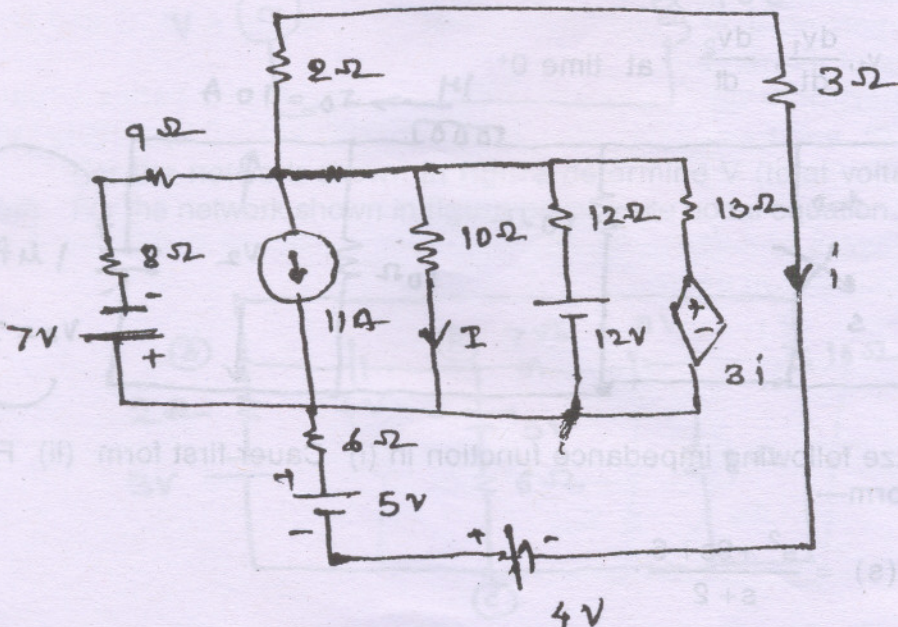
- (c) For the network shown in **figure** below determine current in $10\ \Omega$ resistance (I) using Thevenin's theorem. 5




5. (a) Sketch the Bode plot for the transfer function given below : 10

$$G(s) H(s) = \frac{10(s+1)}{s(1+0.01s)(1+0.1s)}$$

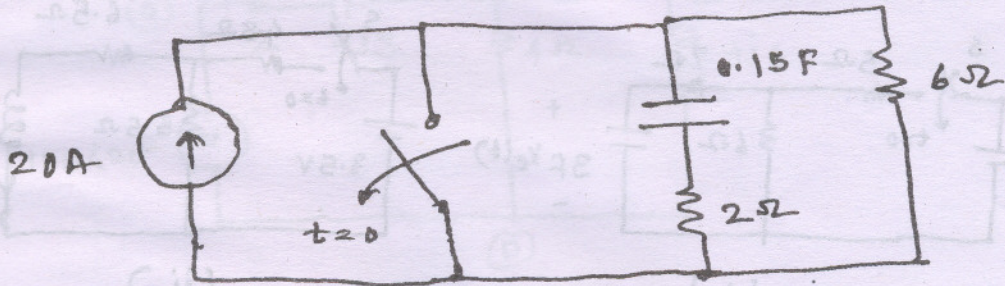- (b) In the network shown below switch 'S' is closed for long time and at $t = 0$. Switch is opened. Determine the current through the capacitor. 10



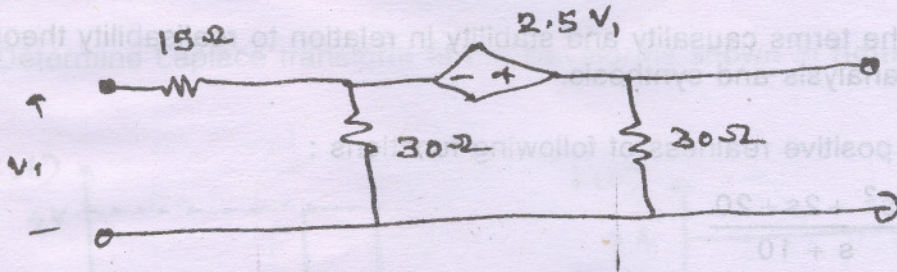6. (a) Find transmission parameters for the two port network shown in figure 10 below : 10




- (b) The driving point impedance of one part LC network is given by— 10

$$Z(s) = \frac{8(s^2+4)(s^2+5s)}{s(s^2+16)}$$

Obtain the first and second Foster form of network.

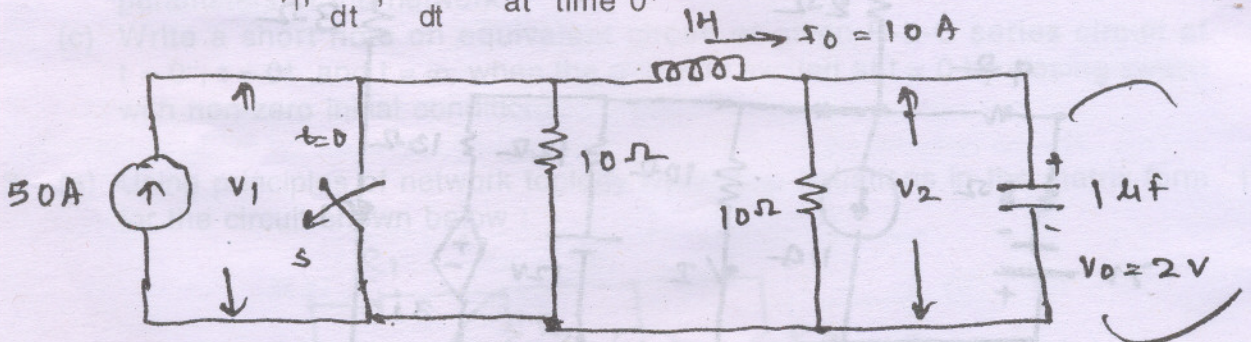7. (a) For the network given below, switch S is opened at $t = 0$ with initial conditions shown. Find the values of 10

$$v_1, \frac{dv_1}{dt}, \frac{dv_2}{dt} \text{ at time } 0^+$$



- (b) Synthesize following impedance function in (i) Cauer first form (ii) Foster second form— 10

$$F(s) = \frac{s^2 + 9s + 6}{s + 2}$$