

Con. 2837-09.

(REVISED COURSE)

Electronic Measuring Instruments
(3 Hours)

[Total Marks : 100

N.B. : (1) Question No.1 is **compulsory**.(2) Attempt any **four** questions out of remaining **six** questions.(3) **Figures** to the **right** indicate **full** marks.(4) Draw **neat** diagram.

1. (a) Why is a delay line used in the vertical section of an oscilloscope ? 5
 (b) Give standard specifications of a signal generator. 5
 (c) Explain factors involved in selection of voltmeter. 5
 (d) Describe the intensity modulation and velocity modulation in a CRO. 5
2. (a) Draw the functional block diagram of a general purpose C.R.O. Explain **10**
 the working of each block in detail.
 (b) What are Lissajous patterns ? How are they used for measurement of **10**
 frequency and phase ?
3. (a) Explain in detail the construction and working of storage oscilloscope. 10
 (b) Explain factors involved in selection of Electronic Voltmeter. Explain the **10**
 working of Electronic Voltmeter using FET bridge.
4. (a) Explain with the help of block diagram working of digital phase meter and **10**
 states its merits and demerits.
 (b) Explain with the help of neat diagram Fastest A/D Analog to Digital Converter. **10**
 Its merits and demerits.
5. (a) With the help of neat diagram, explain the working of function generator **10**
 with proper waveforms at various points.
 (b) Discuss the principle of operation of Q-meter and Impedance measurement **10**
 using Q-meter.
6. (a) Explain with block diagram AF sine and square wave generator. Also state **10**
 the front panel of signal generator.
 (b) Draw the functional block diagram of op-amp and state the ideal characteristics **10**
 of op-amp.
7. Write short notes on (any **three**) :- 20
 - (a) Beat frequency oscillators
 - (b) CRT tube
 - (c) Any one method of Digital-to-Analog converter
 - (d) Requirements of pulse generator.