

- N. B. :** (1) Q. No. 1 is **compulsory**.
(2) Attempt any **four** out of remaining **six** questions.
(3) Assume any **suitable** data wherever required but justify the **same**.

- 1 a Define Inverter Ratio. and state its significance. 20
b What is buried contact? When we use this in MOS technology
c Compare between Silicon and Germanium Technology..
d Define Sheet Resistance, What is the significance of it?
e Draw the Exclusive OR using minimum devices in CMOS Technology?
- 2 a Implement following function also draw the stick diagram 10
- $$F = X + (Y \cdot Z)$$
- Draw Layout for the same.
- b Using nMOS devices design 4:1 MUX also draw the stick diagram. 10
- 3 a Explain the effect of scaling on interconnect with respect to power dissipation and delay 10
b Describe with neat diagram various steps involved in fabrication and sketch each mask steps in cross-sectional view of wafer for nMOS device. 10
- 4 a Derive expression for nMOS transistor current in both regions of operations. 10
b Find the expression for Threshold voltage of pMOS device also explain the effect of substrate potential(Body Effect)on Threshold & overall performance of the device 10
- 5 a Explain following short channel effects: 10
- Threshold voltage roll off
 - Drain Punch-through
 - Velocity saturation
 - Hot carrier effect.
- b Prepare a chart of CMOS Inverter characteristics in five different regions. Specify for the devices the region of operation and justify. 10

- 6 a Derive Noise margin for Resistive load type of an Inverter 10
- b What is total power dissipation in case of CMOS Inverter? Discuss 10
how to approximate the estimation of total power dissipation? What
is power budget ? how to minimize the Power Dissipation?
- 7 Write short notes on: (any four): 20
- a CMOS Domino Logic
- b Explain MOS Capacitor and Band Bending in P-type of Semiconductor .
- c Need & Effect of scaling.
- d Latch-up problem in CMOS device
- e Electron beam lithography
- f Super buffer and its importance in IC design
-