

Circuit & Transmission Lines


QP Code : 545602

(3 Hours)


[Total Marks : 80

- N. B. :** (1) Question No. 1 is compulsory.
 (2) Attempt any **three** questions from the remaining five.
 (3) **Figures** to the **right** indicate **full marks**.
 (4) Use Smith chart for transmission line problem.
 (5) Assume suitable data if required.

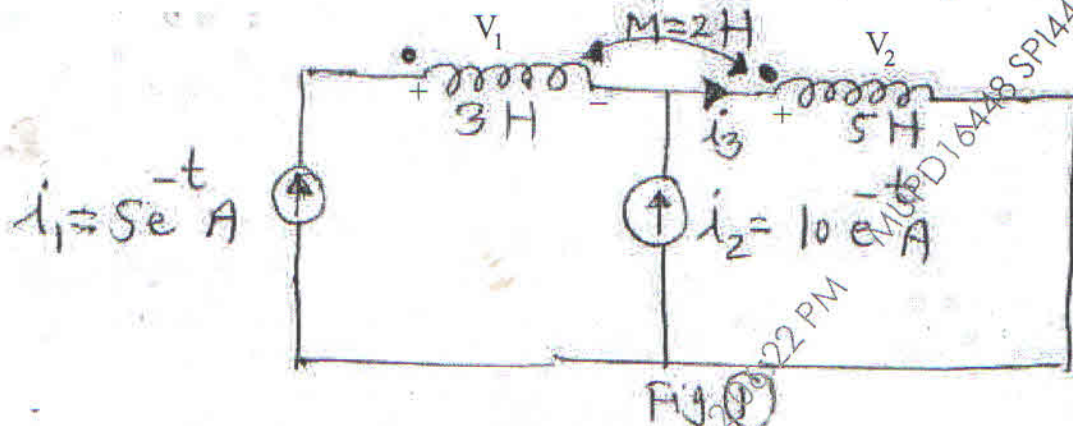
1. (a) In the network shown in fig. (1), find the voltages V_1 and V_2 . 5



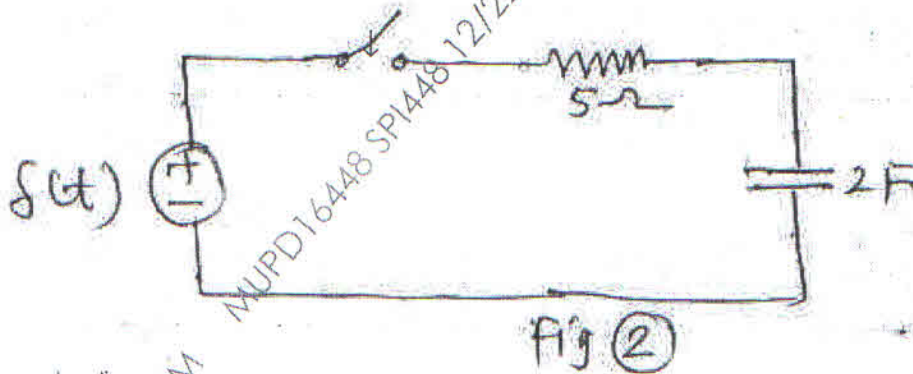- (b) For the network shown in fig (2), determine the current $i(t)$ when the switch is closed at $t = 0$ with zero initial conditions. 5



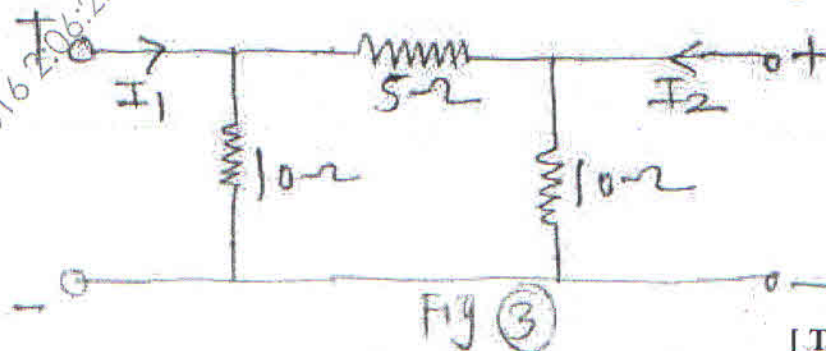- (c) Find the lattice equivalent of symmetric π -network shown in figure (3). 5



[TURN OVER

(d) Define the following parameters of transmission line.

- (i) Input impedance
- (ii) Characteristics impedance
- (iii) VSWR
- (iv) Reflection coefficient
- (v) Transmission coefficient

2. (a) In the network shown in fig. (4) the switch closes at $t = 0$. The capacitor has no initial charge. Find $V_C(t)$ and $i_C(t)$.

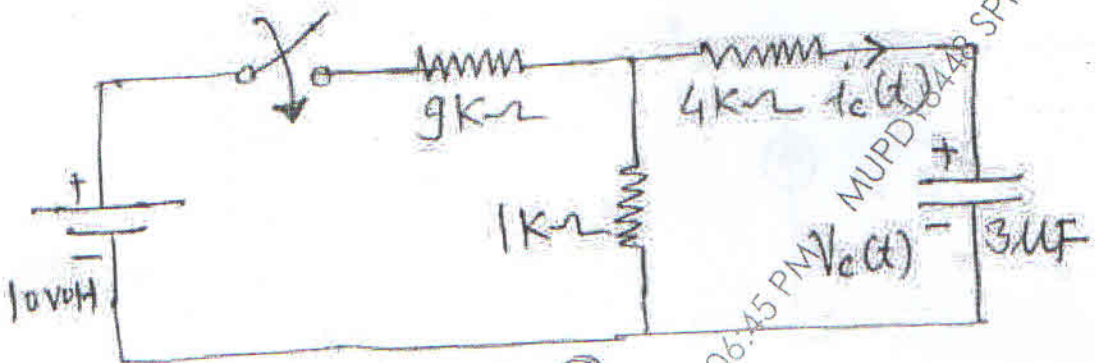


Fig (4)

- (b) Determine the transmission parameters of the network shown in fig (5) using the concept of inter connection of two port network.


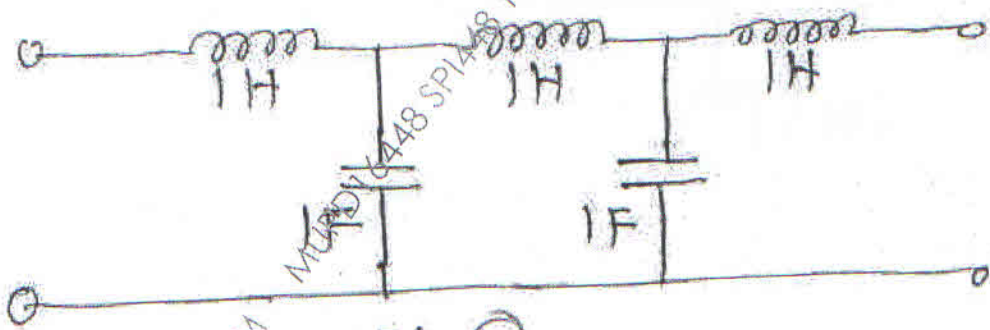


Fig. (5)

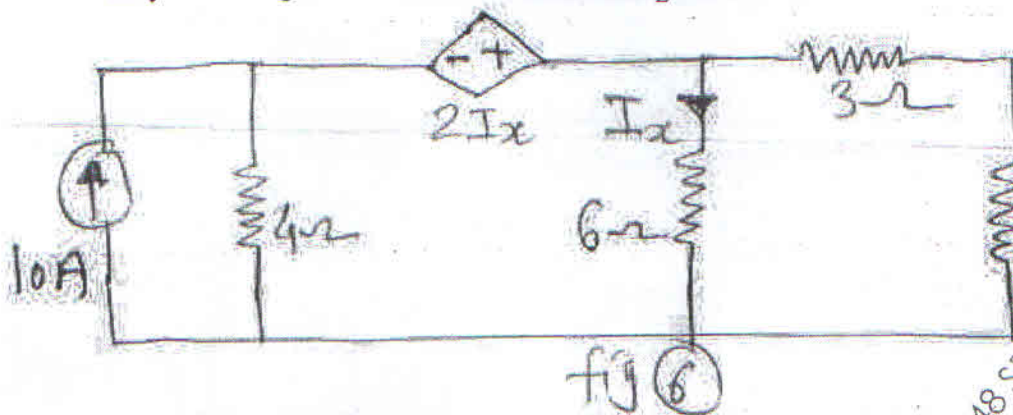3. (a) For the network shown in fig (6), calculate the maximum power that may be dissipated in the load resistor R_L . 10




- (b) A load impedance $Z_L = (30 + j60)\Omega$ is connected to a 50Ω transmission line of 2 cm length and operated at 2 GHz. Using Smith Chart, find the input impedance of transmission line under the assumption that phase velocity is 50% of speed of light. 10

4. (a) An impedance is given by- 10

$$Z(s) = \frac{8(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)(s^2 + 4)}$$


Realise the network in Foster-I and Cauer-I form

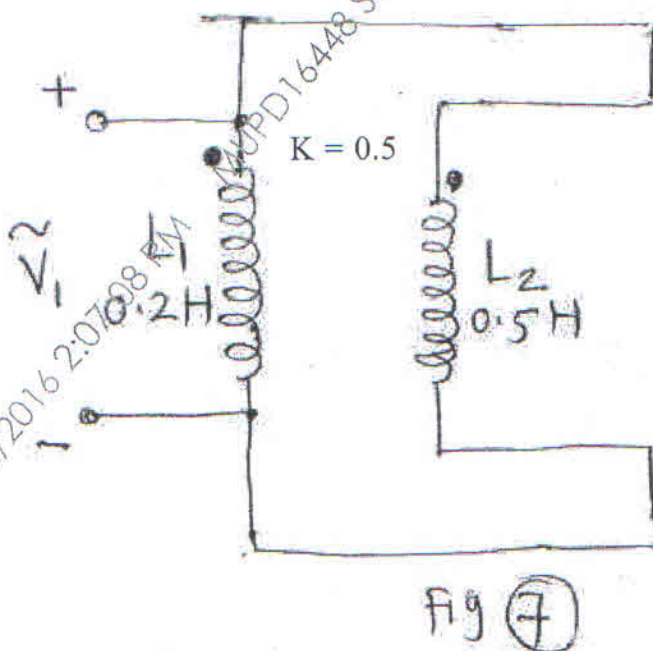- (b) In the coupled circuit of figure (7), find the input impedance as well as the net inductance. 10



[TURN OVER

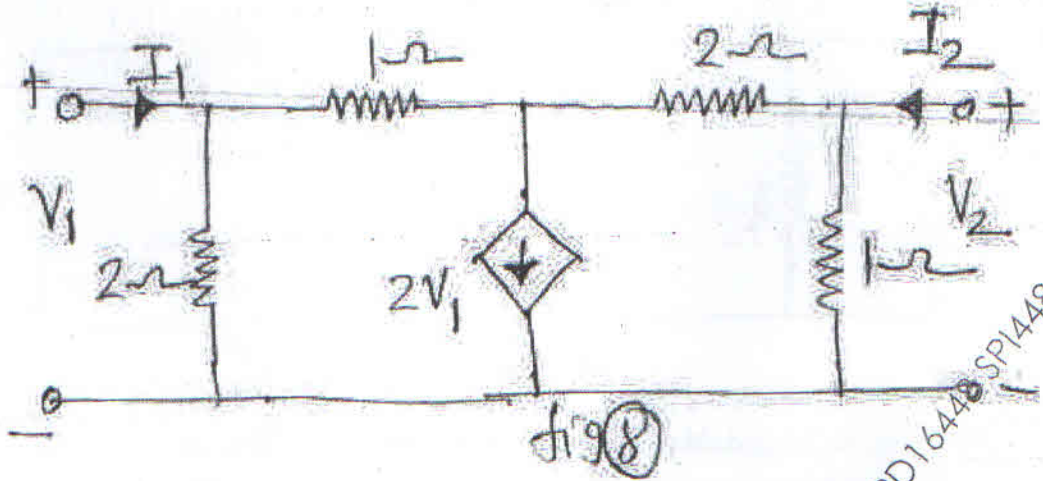5. (a) Find the open circuit impedance parameters of the circuit shown in fig. (8). Also find the Y parameters. 10



- (b) (i) State properties of LC driving point impedance functions. 5
(ii) Test whether the polynomial is Hurwitz 5

$$P(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4$$

6. (a) A co-axial line has the following parameters 10

$$R = 6 \Omega/\text{m}$$

$$L = 5.2 \times 10^{-8} \text{ H/m}$$

$$G = 6 \times 10^{-3} \text{ mho/m}$$

$$C = 2.136 \times 10^{-10} \text{ F/m}$$


$$f = 1 \text{ GHz}$$

$$Z_L = (100 + j 100) \Omega$$

Compute the following parameter using formulae

- Characteristics impedance
- Propagation constant
- Reflection coefficient at the load
- Transmission coefficient at the load

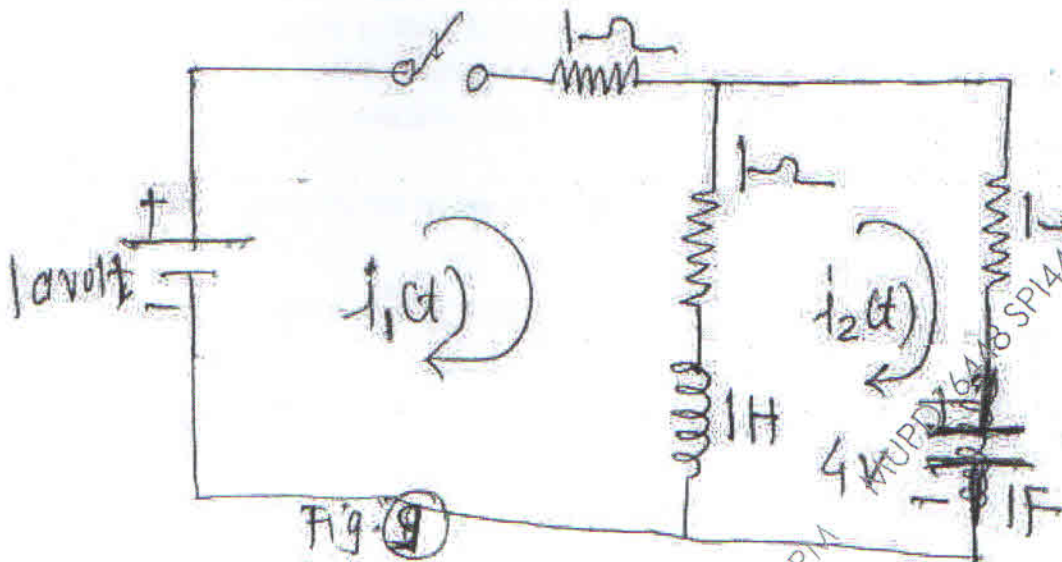- (b) In the network shown in fig (9), the switch is closed at $t = 0$. Find the current $i_1(t)$ and $i_2(t)$ when initial current through the inductor is zero and initial voltage is 4 volt. 10



SE EXTC SEM-III (CBSSGS) 16-12-2016
Electronic Instruments & Measurements
Q.P. Code : 545500

(3 Hours)

[Total Marks : 80

- N.B. :** (1) Attempt **four** questions, question no **1** is **compulsory**.
(2) Assume suitable data where ever required.
(3) Answers to the questions should be grouped together.
(4) Figure to the **right** of question indicates **full** marks.

1. Attempt any **four** :

20

- (a) Significance of three and half digit display
 - (b) Define accuracy, precision and sensitivity with suitable example
 - (c) Explain working of strain gauge and its application in load measurement
 - (d) List various sensors for pressure and temperature along with their ranges
 - (e) A galvanometer, with a 1 mA full scale deflection and an internal resistance of 500Ω , is to be used as voltmeter, find series resistance for 1V and 10 V ranges.
2. (a) Draw and explain working of capacitive transducer for level measurement. 10
(b) Draw neat block diagram of CRO and explain its functioning, comment on role of sweep in CRO. 10
3. (a) Draw and explain R-2R ladder network DAC for 3 bits input taking suitable example. 10
(b) Explain Kelvin's double bridge and its application in very low resistance measurement. 10
4. (a) Explain SAR OR Flash type ADC with the help of block diagram and comment on its speed. 10
(b) Explain LVDT and define its application in displacement measurement. 10
5. (a) Explain Heterodyne type waves analyser and its applications. 10
(b) Discuss DSO with the help of block diagram along with various modes of operation also explain its applications. 10
6. (a) Draw and discuss Hey Bridge and its application for measurement of inductance. 10
(b) Define power and energy and explain working of an energy meter. 10
-

Digital Electronics

Q.P. Code : 545401

(3 Hours)

[Total Marks : 80

N.B. : (1) Question No. 1 is compulsory.

(2) Attempt any 3 questions from Q.2 to Q.6.

(3) Figures to the right in the bracket indicate full marks.

(4) Assume suitable data if necessary.

1.
 - a) State basic theorems of Boolean algebra. 5
 - b) Compare Mealy and Moore machine 5
 - c) Define Noise Margin, Propagation delay, Power Dissipation 5
 - d) Design a full adder using half adders and logic Gates 5
2.
 - a) Prove that NAND and NOR Gates are universal Gates 10
 - b) Design a 2-bit comparator and implement using logic Gates 10
3.
 - a) Design a 4 bit Binary to Grey code converter. 10
 - b) Implement the given function using single 4:1 Multiplexer and few logic gates: $F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 10, 12, 13, 15)$ 10
4.
 - a) What is a universal shift register? Explain its various modes of operation 10
 - b) Write a VHDL program to design a 3:8 Decoder. 10
5.
 - a) Minimize the following expression using Quine McClusky Technique $F(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 9, 11)$ 10
 - b) Convert JK FF to T FF and JK FF to D FF 10
6.
 - a) Explain the working of 3-bit asynchronous counter with proper timing diagram. 10
 - b) Write a note on CPLDs. 10

(3 Hours)

[Total Marks : 80

N.B. : (1) Question No. 1 is compulsory.


(2) Attempt **any three** questions out of remaining **five** questions.

(3) Assume suitable data if required and mention the same in answer sheet.


1. Attempt **any five** questions

20

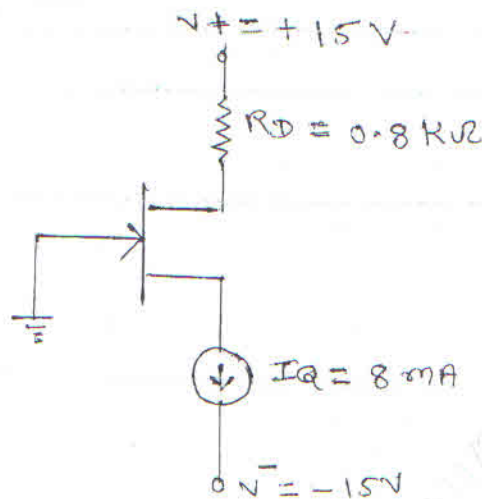(a) For the circuit given below, the transistor parameters are $V_p = -3.5\text{V}$, $I_{DSS} = 18\text{mA}$ and $\lambda = 0$. Calculate V_{GS} and V_{DS} .




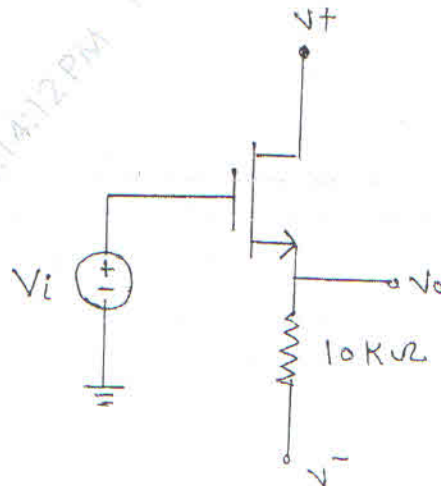(b) The small-signal parameters of the NMOS transistor in the source follower circuit shown in fig. below are $g_m = 5\text{mA/V}$ and $r_o = 100\text{ k}\Omega$. Determine the voltage gain and output resistance.




[TURN OVER]

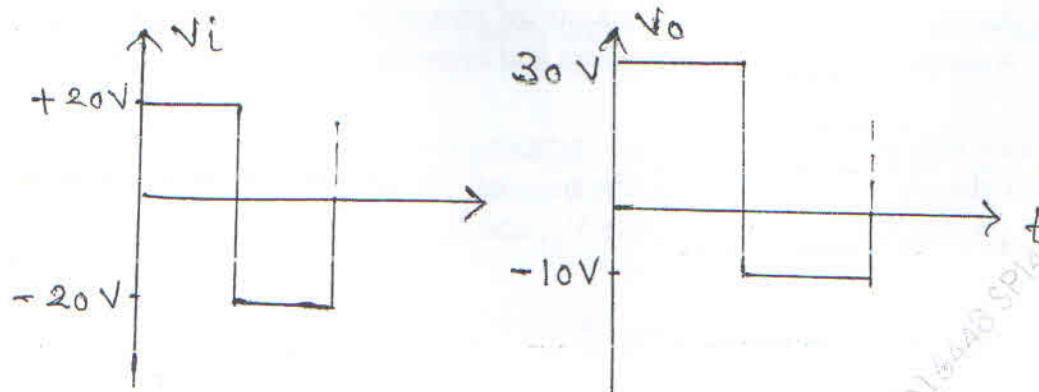- (c) Design a diode clamper to generate a steady-State output voltage V_o from the input voltage V_i in fig. Shown below if diode is Ideal.



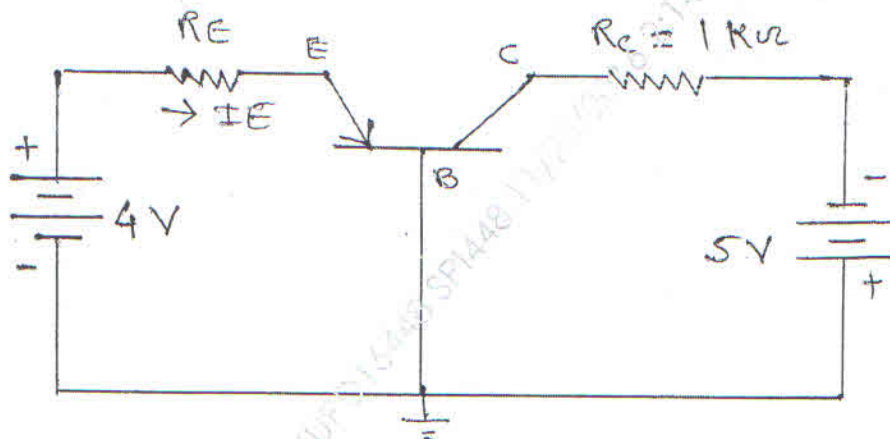- (d) For the circuit shown, determine R_E such that the emitter current is limited to $I_E = 1mA$, Also find I_B (Given $\alpha = 0.9920$)



- (e) Describe the channel length modulation effect and define the parameters λ .
- (f) Draw a neat circuit diagram of emitter follower configuration and its hybrid - π model.


[TURN OVER]

3

2 (a) Determine the following for the network given below

10

- Q- Point
- A_v , A_i , Z_i , Z_o .

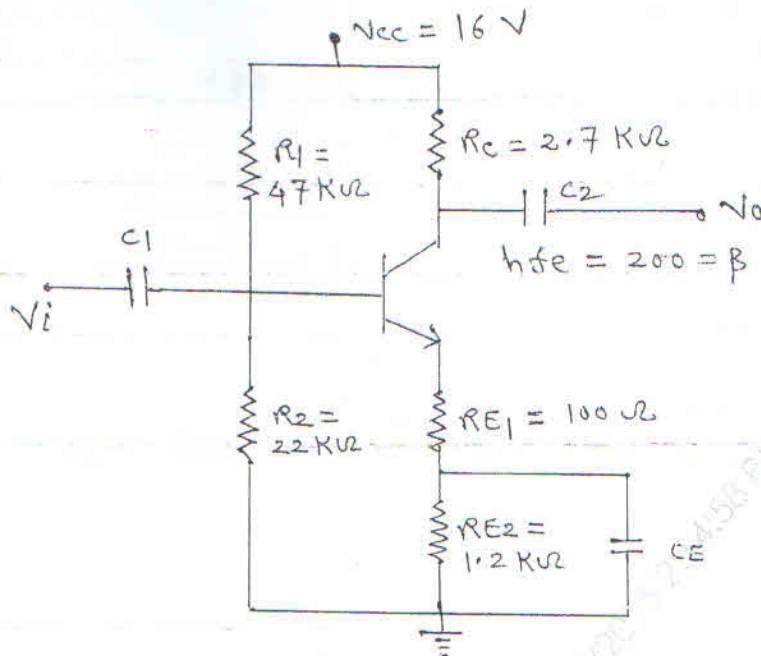


(b) Explain the working of Wein Bridge oscillator. Derive the expression for frequency of oscillation and condition of oscillation.

10



3 (a) Draw output waveform for clipper and clamper circuits shown.

10

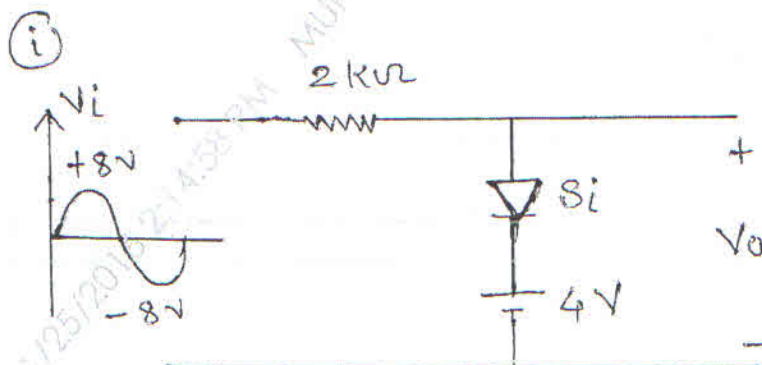


[TURN OVER]

(ii)

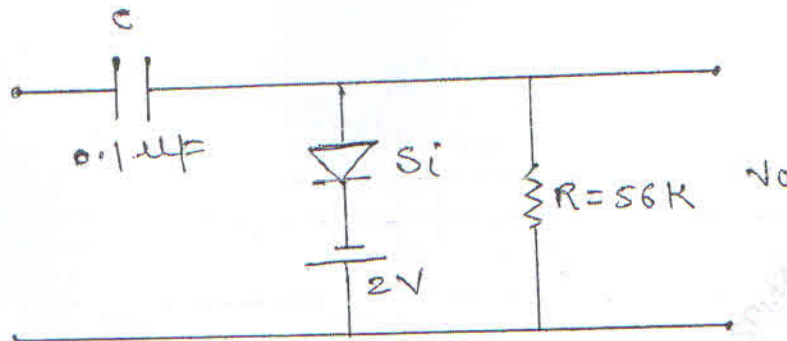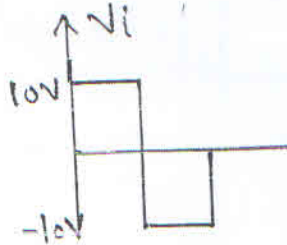

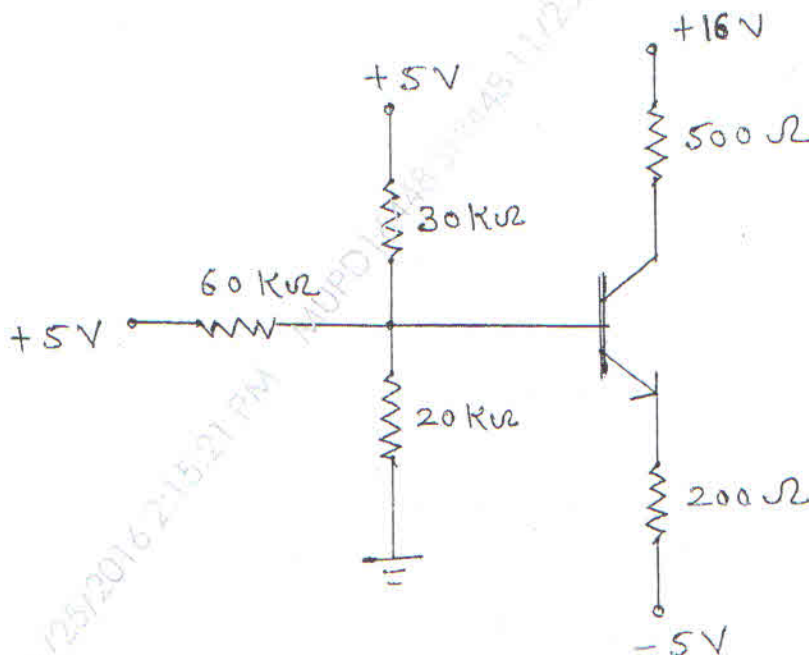
- (b) Explain construction and characteristics of n-channel Depletion MOSFET. 10
Draw transfer characteristics and drain characteristics.

- 4 (a) Find I_{CQ} and V_{CEQ} for the circuit shown in figure if $\beta = 100$ 10



5

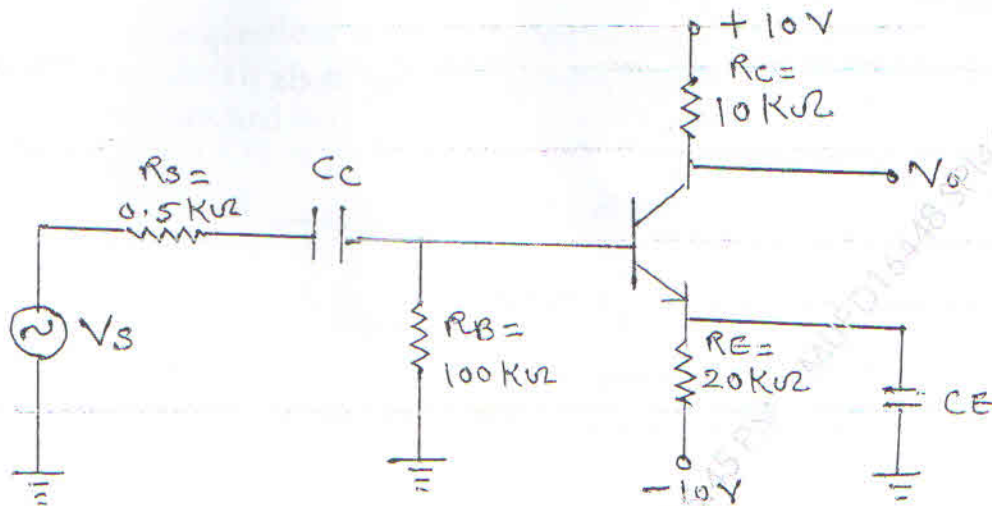
- (b) For the circuit in fig. let $\beta = 100$, $V_A = 100V$, $V_{BE(on)} = 0.7V$. Determine 10
- Small signal voltage gain
 - Input resistance seen by the signal source
 - output resistance



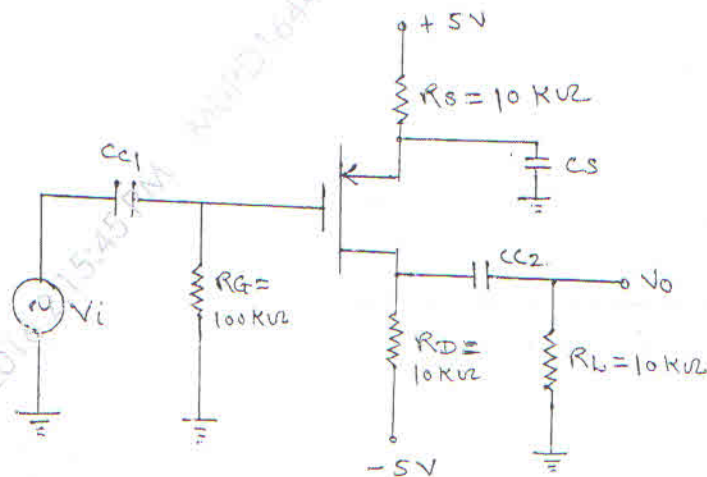5. (a) For the amplifier circuit shown below

10

- Determine the values of K_p such that $V_{SDQ} = 6V$
- Determine the resulting value of I_{DQ} and small signal voltage gain.



$$V_{TP} = -2V, \lambda = 0$$

[TURN OVER]

- (b) Draw circuit diagram of common source amplifier with voltage divider bias with unbypassed source resistance ' R_s ' using n-channel EMOSFET. Derive expression for voltage gain, input resistance and output resistance.

10

6. Write short note on any four :-

- (i) Energy band diagram of MOS capacitor
- (ii) Construction and operation of Schottky diode
- (iii) Crystal Oscillator
- (iv) Hybrid parameters
- (v) Stability factor of biasing circuit.

10

DURATION: 3 HRS.

MAX. MARKS:80

- 1) Question No. 1 is compulsory.
- 2) Attempt any **THREE** of the remaining.
- 3) **Figures** to the **right** indicate **full marks**.

Q 1.A) Determine the constants a, b, c, d, e if

$$f(z) = (ax^4 + bx^2y^2 + cy^4 + dx^2 - 2y^2) + i(4x^3y - exy^3 + 4xy) \text{ is analytic.} \quad (5)$$

B) Find half range Fourier sine series for $f(x) = x^2$, $0 < x < 3$. (5)

C) Find the directional derivative of $\phi(x, y, z) = xy^2 + yz^3$ at the point (2, -1, 1) in the direction of the vector $i + 2j + 2k$. (5)

D) Evaluate $\int_0^\infty e^{-2t} t^5 \cosh t \, dt$. (5)

Q.2) A) Prove that $J_{\frac{3}{2}}(x) = \sqrt{\frac{2}{\pi x}} \left(\frac{\sin x}{x} - \cos x \right)$ (6)

B) If $f(z) = u + iv$ is analytic and $u - v = e^x(\cos y - \sin y)$, find $f(z)$ in terms of z . (6)

C) Obtain Fourier series for $f(x) = x + \frac{\pi}{2} \quad -\pi < x < 0$
 $= \frac{\pi}{2} - x \quad 0 < x < \pi$

Hence deduce that $\frac{\pi^2}{8} = \frac{1}{1^2} + \frac{1}{3^2} + \frac{1}{5^2} + \dots$ (8)

Q.3) A) Show that $\vec{F} = (2xy + z^3)i + x^2j + 3xz^2k$, is a conservative field. Find its scalar potential and also find the work done by the force \vec{F} in moving a particle from (1, -2, 1) to (3, 1, 4). (6)

B) Show that the set of functions $\{\sin(2n+1)x\}$, $n = 0, 1, 2, \dots$ is orthogonal over $[0, \pi/2]$. Hence construct orthonormal set of functions. (6)

[TURN OVER]

C) Find (i) $L^{-1}\{\cot^{-1}(s+1)\}$

(ii) $L^{-1}\left(\frac{e^{-2s}}{s^2+8s+25}\right)$ (8)

Q.4) A) Prove that $\int J_3(x) dx = -\frac{2J_1(x)}{x} - J_2(x)$ (6)

B) Find inverse Laplace of $\frac{s}{(s^2+a^2)(s^2+b^2)}$ ($a \neq b$) using Convolution theorem. (6)

C) Expand $f(x) = x \sin x$ in the interval $0 \leq x \leq 2\pi$ as a Fourier series.

Hence, deduce that $\sum_{n=2}^{\infty} \frac{1}{n^2-1} = \frac{3}{4}$ (8)

Q.5) A) Using Gauss Divergence theorem evaluate $\iint_S \bar{N} \cdot \bar{F} dS$ where $\bar{F} = x^2\mathbf{i} + z\mathbf{j} + yz\mathbf{k}$

and S is the cube bounded by $x=0, x=1, y=0, y=1, z=0, z=1$ (6)

B) Prove that $J_2'(x) = \left(1 - \frac{4}{x^2}\right)J_1(x) + \frac{2}{x}J_0(x)$ (6)

C) Solve $(D^2+3D+2)y = 2(t^2 + t + 1)$, with $y(0)=2$ and $y'(0)=0$ (8)
by using Laplace transform

Q.6) A) Evaluate by Green's theorem for $\int_C (e^{-x} \sin y dx + e^{-x} \cos y dy)$ where C is the
the rectangle whose vertices are $(0,0), (\pi, 0), (\pi, \pi/2)$ and $(0, \pi/2)$ (6)

B) Show that under the transformation $w = \frac{z-i}{z+i}$, real axis in the z -plane is mapped onto the
circle $|w| = 1$ (6)

C) Find Fourier Sine integral representation for $f(x) = \frac{e^{-ax}}{x}$ (8)