

Q.P. Code : 4032

(OLD COURSE)

(3 Hours)

[Total Marks : 100

- N.B: (1) Question No. 1 is compulsory  
 (2) Attempt any four questions from the remaining six questions.  
 (3) Figures to the right indicate full marks.  
 (4) Use of statistical table is allowed.

1 (a) If,  $A = \begin{bmatrix} -1 & 0 & 0 \\ 2 & -3 & 0 \\ 1 & 4 & -2 \end{bmatrix}$  find the eigen values of  $A^2$ . 5

- (b) Find the solution of  $5 * x = 2$  5  
 (i) In the group of real numbers under the binary operation  
 $a * b = a + b - 1$   
 (ii) In the group of rational numbers different from -3 under the  
 binary operation  $a * b = a + b + \frac{ab}{3}$

(c) Determine the pole of the function : 5  
 $f(z) = \frac{z^2}{(z-1)^2(z+2)}$  and also find the residue at each pole.

(d) The probability distribution of a random variable x is given by 5

X :	-2	-1	0	1	2	3
P(X = x):	0.1	k	0.2	2k	0.3	k

Find the mean and variance.

2. (a) Find the Laurent's series for : 6  
 $f(z) = \frac{4z+3}{z(z-3)(z+2)}$  valid for  $2 < |z| < 3$

- (b) With usual notation find P of Binomial distribution if 6  
 $n = 6, \text{ and } P(X = 4) = P(X = 2)$

- (c) Show that the matrix  $A = \begin{bmatrix} 8 & -6 & 2 \\ -6 & 7 & -4 \\ 2 & -4 & 3 \end{bmatrix}$  is diagonalisable. Find the transforming matrix and the diagonal matrix. 8

is diagonalisable. Find the transforming matrix and the diagonal matrix.

3. (a) Ten school boys were given a test in statistics and their scores were recorded. They were given a months special coaching and a second test was given to them in the same subject at the end of the coaching period. Test if the marks given below give evidence to the fact that the students are benefitted by coaching. 6
- Marks in Test I : 70, 68, 56, 75, 80, 90, 68, 75, 56, 58  
 Marks in Test II : 68, 70, 52, 73, 75, 78, 80, 92, 54, 55

- (b) Find the characteristic equation of the matrix. 6

$$\begin{bmatrix} 2 & -1 & 1 \\ -1 & 2 & -1 \\ 1 & -1 & 2 \end{bmatrix} \text{ and verify that it is satisfied by } A \text{ and hence find } A^{-1}.$$

- (c) Let  $L = \{1, 2, 3, 6\}$  and  $R$  be the relation 'is divisible by' Prove that  $L$  is a lattice. 8

4. (a) Using normal distribution. Find the probability of getting 55 heads in the toss of 100 fair coins. 6

- (b) Evaluate  $\int_C \frac{dz}{z^3(z+1)}$ , where  $C$  is the circle  $|z| = 2$  6

- (c) The means of two samples of sizes 1000 and 2000 respectively are 67.50 and 68.0 inches. Can the samples be regarded as drawn from the same population of standard deviation 2.5 inches, at 0.27% level of significance. 8

5. (a) Fit a Poisson distribution to the following data. 6

No. of deaths	:	0	1	2	3	4
Frequencies	:	123	59	14	3	1

(b) If  $f : \{R-(2/5)\} \rightarrow \{R-(4/5)\}$  is a function defined by  $f(x) = \frac{4x+3}{5x-2}$ , 6  
 prove that  $f$  is a bijection and find  $f^{-1}$ .

(c) A random variable  $X$  has the following probability mass function. 8

$X$	:	-2	3	1
$P(X = x)$	:	1/3	1/2	1/6

Find (i) first four raw moments  
 (ii) first four central moments

6. (a) For  $x, y, \in Z$ ,  $xRy$  if and only if  $2x + 5y$  is divisible by 7. Is  $R$  an equivalence relation? 6

(b) If  $A = \begin{bmatrix} \pi & \pi/4 \\ 0 & \pi/2 \end{bmatrix}$ , find  $\cos A$  6

(c) The following table gives the number of accidents in a city during a week. Find whether the accidents are uniformly distributed over a week. 8

Day	:	Sun	Mon	Tue	Wed	Thu	Fri	Sat	Total
No.of accidents	:	13	15	9	11	12	10	14	84

7. (a) Evaluate  $\int_0^{2\pi} \frac{\cos 2\theta}{5 + 4\cos \theta} d\theta$  6

(b) Find the Binomial distribution if the mean is 4 and variance is 3. Find also its mode. 6

(c) Prove that  $Z_4$  is a ring under addition and multiplication modulo 4. 8

**(OLD COURSE) QP Code : 4034**

(3 Hours)

[ Total Marks : 100

- N. B. : (1) Question no 1 is compulsory.  
 (2) Solve any four from remaining six questions.  
 (3) Figures on right indicate maximum marks.

1. Answer any four of the following questions. 20
- (a) List the features of VHDL.
  - (b) Compare Synchronous counters and Asynchronous counters.
  - (c) Draw 4 bit ring counter using universal shift register IC 74194. Also draw its output waveforms w.r.t. clock.
  - (d) Draw a state diagram of Moore type sequence detector that detects the sequence, '010100'. Overlapping of sequence is allowed.
  - (e) Name various Programmable Logic Devices and explain the advantages of using those. 10
2. (a) Design a synchronous counter that counts following count in binary. 10  
 011 → 100 → 010 → 111 → 101 → 000 → 011
- (b) Write a VHDL code for 4 bit binary counter with clear, and clock. 10
3. (a) Reduce the following state table and draw the state diagram for the reduced table. 10

Present state	Next state		O/P (z)	
	x=0	x=1	x=0	x=1
S <sub>0</sub>	S <sub>4</sub>	S <sub>3</sub>	0	1
S <sub>1</sub>	S <sub>5</sub>	S <sub>3</sub>	0	0
S <sub>2</sub>	S <sub>4</sub>	S <sub>1</sub>	0	1
S <sub>3</sub>	S <sub>5</sub>	S <sub>1</sub>	0	0
S <sub>4</sub>	S <sub>2</sub>	S <sub>5</sub>	0	1

- (b) Design and explain the working of mod 50 counter using decade counter IC 7490. 10

[ TURN OVER

4. (a) Explain different modeling styles in VHDL with suitable examples. 10  
(b) Design a sequential state machine that receives bits at its input terminal 'S' serially in synchronism with the clock. It makes the output Z=1 when consecutive three 0's are received at the input. Otherwise Z remains low. 10
5. (a) Write a VHDL code for Half adder. Declare it as a component. Using this component, design a Full adder. 10  
(b) Write a VHDL code for 3:8 decoder with active low enable. 10
6. (a) Draw and explain the architecture of Xilinx XC 4000 FPGA family. 10  
(b) Design a mod 8 Up/ Down synchronous counter that counts in Up direction when mode input M=0 and in Down direction when M=1. Use D flip flops and gates. 10
7. Write short notes on (Any three) :- 20  
(a) SRAM architecture  
(b) Shift Register and its applications  
(c) State assignment rules in designing a state machine  
(d) Functional block of Xilinx 95xx family CPLD
-

(OLD COURSE)

QP Code : 4039


(3 Hours)

[ Total Marks :100

- N.B. : (1) Question No. 1 is compulsory.  
(2) Solve any four questions from remaining questions.  
(3) Assume suitable data if necessary.


1. (a) Design two stage JFET based CS Amplifier for  $AV \geq 500$ ,  $V_o = 3V$  use suitable biasing circuit. 15  
(b) From the designed circuit calculate  $R_i$ ,  $R_o$  and  $A_v$ . 5
2. (a) Which components affect high frequency response of JFET amplifier and hence derive equation of higher cut off frequency of JFET amplifier. 10  
(b) State the properties of crystal and hence explain different types of crystal oscillators, also state the different applications of it. 10
3. (a) For the given circuit find : 10

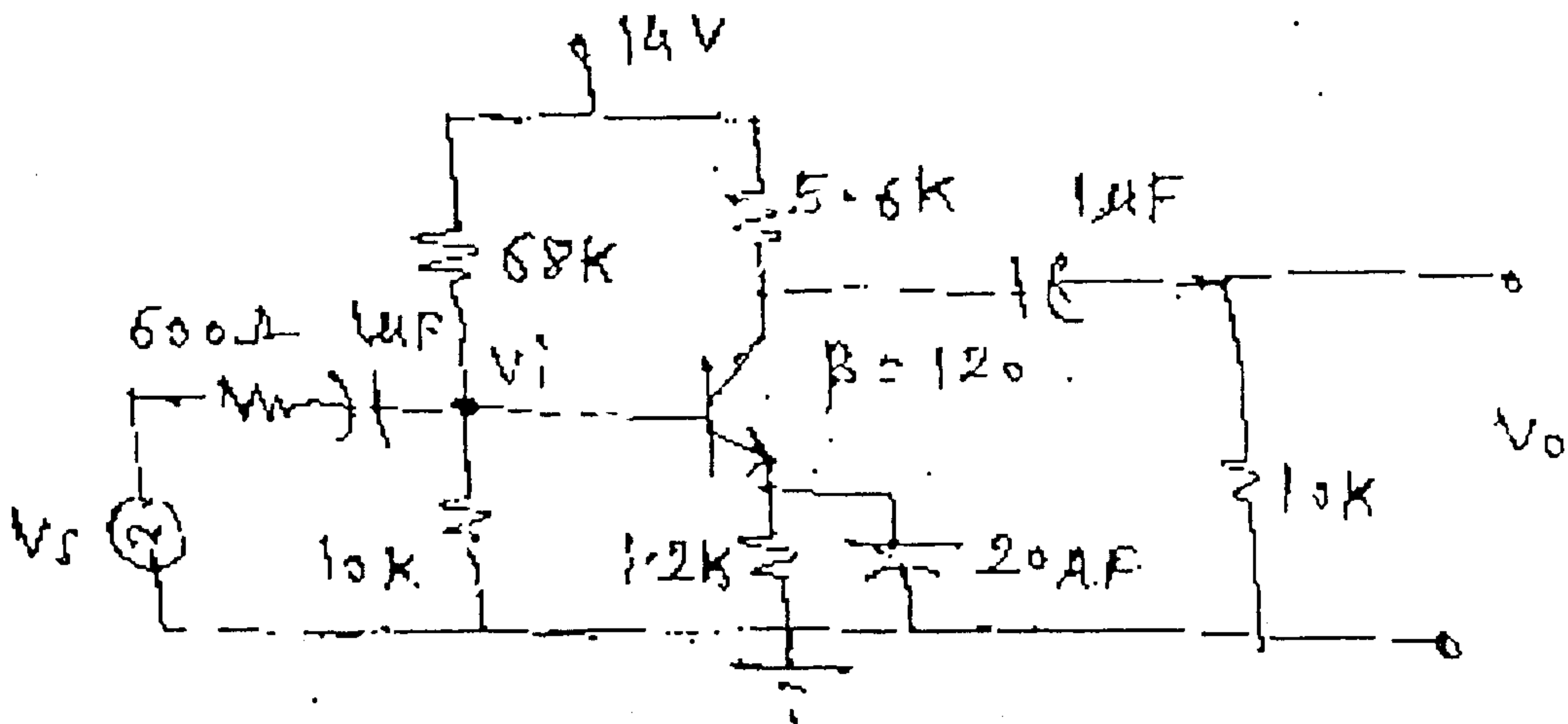- (i)  $r_e$       (ii)  $A_{vmid} \frac{V_o}{V_i}$       (iii) Lower cut off frequency



- (b) Design RC phase shift oscillator to generate frequency of 20KHz. 10
4. (a) What are the advantages of -ve feedback amplifiers, give the topologies of different -ve feedback amplifiers. 10  
(b) Design class B power amplifier to give output of 15W for  $8\Omega$  load. 10

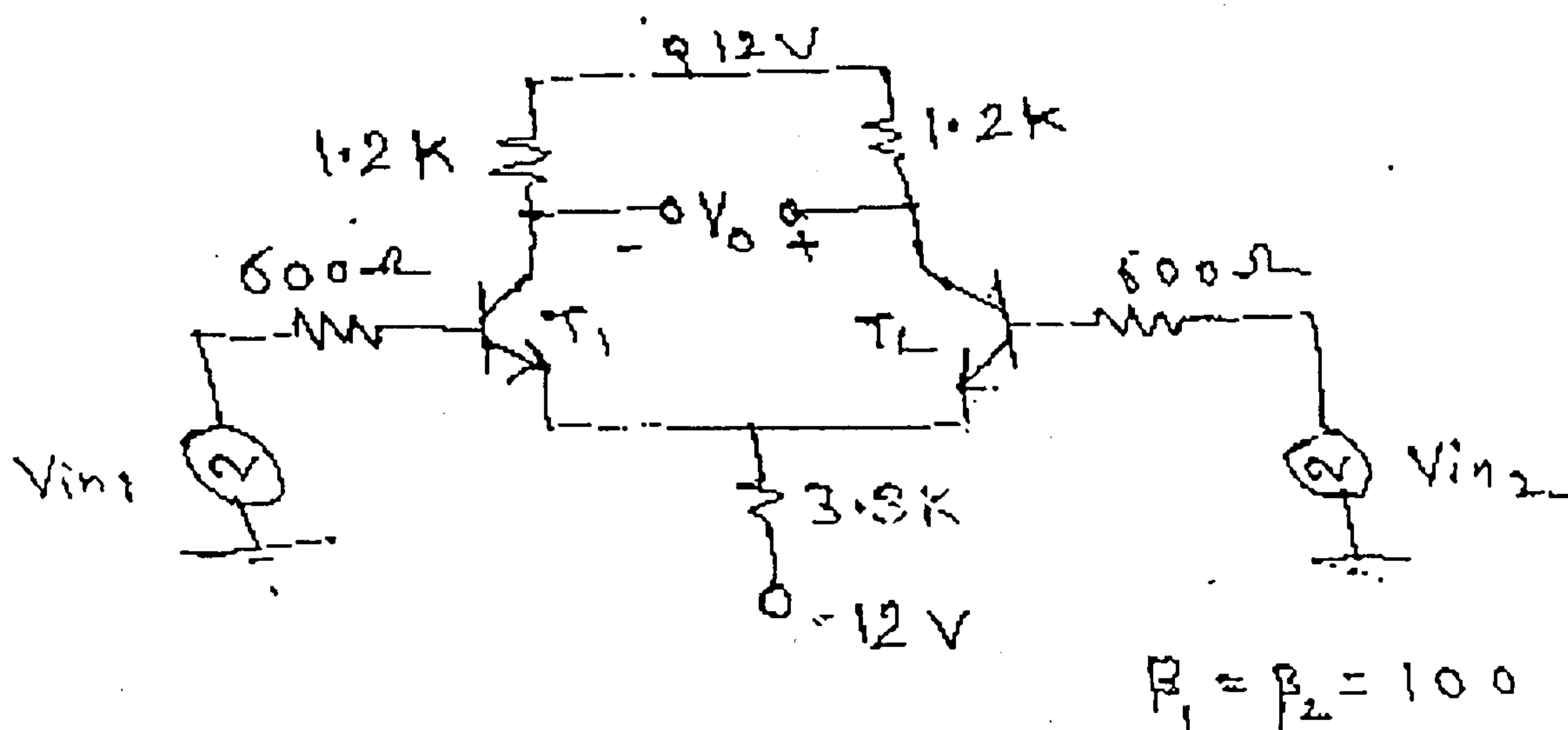5. (a) Compare power amplifier with voltage amplifier and derive equation of efficiency of direct coupled series fed class A power amplifier. 10  
 (b) What do you mean by CMRR, how it can be improved in differential amplifier. 10
6. (a) Derive equation of  $R_{iF}$ ,  $R_{oF}$  and  $A_F$  for voltage shunt type -ve feedback amplifier. 10  
 (b) For the given differential amplifier determine : 10  
 (i)  $I_{CQ}$  (ii)  $V_{CEQ}$  (iii)  $A_{CM}$  (iv)  $A_{DM}$  (v) CMRR.



7. Write short notes on any four : 20
- CASCODE Amplifier
  - Types of power Amplifiers
  - Differential Amplifiers
  - Characteristics of -ve feedback Amplifier
  - Clapp oscillator.

Transistor type	$P_{max}$ 25°C Watts	$I_{m,25}$ 25°C Amps	$V_{CE(sat)}$ Vdc	$V_{CE}$ Vdc	$V_{CE(sat)}$ (Duty) Vdc	$V_{CE(sat)}$ (Pulse) Vdc	$V_{CE}$ Vdc	$V_{CE}$ Vdc	$T_1$ max °C	D.C. min	current typ	gain max	Spread min	Signal typ.	$f_h$ max	$V_{CE}$ max	$D_{CW}$	Overdrive above 75°C WPC
2N 3085	115.5	15.0	1.1	100	80	70	80	7	200	20	80	70	15	50	120	1.8	1.5	0.7
1CN 055	80.0	5.0	1.0	60	60	55	60	5	200	25	50	100	25	75	125	1.5	1.6	0.4
1CN 148	30.0	4.0	1.0	50	40	-	-	8	150	30	80	110	33	80	115	1.2	4.0	0.1
1CN 100	8.0	0.7	0.8	70	60	65	-	8	200	60	90	200	50	90	280	0.9	35	0.05
1C 147A	.025	0.1	0.25	50	45	50	-	8	125	115	180	220	125	220	260	0.9	-	-
2N 805 (PNP)	0.225	0.5	0.25	85	30	-	-	-	100	35	-	65	-	45	-	-	-	-
1C 147 B	0.28	0.1	0.28	50	45	50	-	8	125	200	280	450	240	300	500	0.9	-	-

Transistor type	$V_{CE}$	$I_{m,25}$	$I_{m,100}$	$I_{m,150}$	$I_{m,200}$
1C 147 A	2.7Vdc	14μAmps	15 × 10 <sup>-4</sup>	0.6μAmps	-
2N 805 (PNP)	1.4Vdc	25μAmps	32 × 10 <sup>-4</sup>	-	-
1C 147 B	4.9Vdc	30μAmps	2 × 10 <sup>-4</sup>	0.4μAmps	-
1CN 100	800	-	-	-	-
1CN 148	150	-	-	-	-
1CN 055	120	-	-	-	-
2N 3085	0.0	-	-	-	-

1N 1157E MATH. CHARACTERISTICS

$V_{CE}$ Vdc	$I_{m,25}$ mA	$I_{m,100}$ mA	$I_{m,150}$ mA	$I_{m,200}$ mA	$I_{m,250}$ mA	$I_{m,300}$ mA	$I_{m,400}$ mA	$I_{m,500}$ mA	$I_{m,600}$ mA	$I_{m,700}$ mA	$I_{m,800}$ mA	$I_{m,900}$ mA	$I_{m,1000}$ mA
0.0	0.2	0.4	0.8	0.8	1.0	1.2	1.6	2.0	2.4	2.8	3.0	3.5	4.0
10	0.0	0.5	0.8	0.8	0.1	0.4	0.2	0.1	0.2	0.2	0.1	0.1	0.0
4.0	3.0	2.2	1.8	1.1	0.8	0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0

MECHANICAL SPEC

Type	$V_{CE(sat)}$ Vdc	$V_{CE(sat)}$ Vdc	$V_{CE(sat)}$ Vdc	$P_{max}$ Q 25°C	$T_1$ °C	$I_{m,25}$ mA	$I_{m,100}$ mA	$I_{m,150}$ mA	$I_{m,200}$ mA	$I_{m,250}$ mA	$I_{m,300}$ mA	$I_{m,400}$ mA	$I_{m,500}$ mA	$I_{m,600}$ mA	$I_{m,700}$ mA	$I_{m,800}$ mA	$I_{m,900}$ mA	$I_{m,1000}$ mA	Depth above 25°C	$I_{m,25}$	$I_{m,100}$
2N 3085	80	80	80	300 mW	170°C	2 mA	3000 μA	0	80 kΩ	2.5μWPC	0.5μAmps	-	-	-	-	-	-	-	0.5μAmps	0.5μAmps	0.5μAmps
1N 11 (Epsilon)	30	30	30	300 mW	200°C	7 mA	6500 μA	2.5	80 kΩ	-	-	-	-	-	-	-	-	-	0.5μAmps	0.5μAmps	0.5μAmps



S.F. (SEM IV) (OLD)

ETRX

ELECTRONIC & ELECTRICAL MEASURING  
INSTRUMENTS & MACHINE

DT. 12/06/15

(OLD COURSE)

QP Code : 4044

(3 Hours)

[ Total Marks : 100

- N. B. : (1) Question No. 1 is compulsory.  
(2) Solve any **four** from remaining.  
(3) Assume suitable data wherever required.

1. Answer any four :- 20
  - (a) State the requirements of good laboratory type signal generator.
  - (b) Explain the operation of a megger.
  - (c) Compare analog and digital phase meter.
  - (d) Explain multirange ohm meter with neat diagram.
  - (e) Explain the stepper motor characteristics.
  
2. (a) Draw neat diagram of front panel of dual trace oscilloscope and explain it in detail. 10  
(b) What are essentials of indicating instruments. Explain it in detail. 10
  
3. (a) Explain digital phase meter using Flip-flop. Write its advantages and disadvantages. 10  
(b) Explain the principle of operation of PMMC and moving Iron type of instruments. Compare the two basic types. 10
  
4. (a) Explain different methods of D to A converters. 10  
(b) What is z-modulation in CRO for what purpose it is used. Can the frequency and phase difference be measured using z-modulation. 10
  
5. (a) Explain the measurement of self inductance with maxwells bridge with vector diagram. Write advantages and disadvantages. 10  
(b) Explain with the block diagram basic elements of a laboratory type function generator. Which is the basic function generated. How the frequency is controlled & how the sine function is generated. 10
  
6. (a) Explain the various performance parameters of DVM. 10  
(b) Explain the need of starter for induction motor what are various types of starters used for IM. Explain any one in detail. 10
  
7. Write short notes on (any three) :- 20
  - (a) FET voltmeters
  - (b) Weston type frequency meter
  - (c) Derivation of torque equation for moving iron meter
  - (d) Power factor meter