

QP Code : 3313

(3 Hours)

[Total Marks : 80

- N.B. : (1) Questions No.1 is compulsory.  
 (2) Attempt any three questions from the remaining questions.  
 (3) Solve every question in an order.

1. (a) Prove convolution property of Fourier Transform. 20  
 (b) State and prove final value Theorem of Laplace Transform.  
 (c) Prove shifting property of Z transform.  
 (d) Determine energy and/or power of following signals.

$$(i) \quad x(n) = \left(\frac{3}{5}\right)^n u(n) - (4)^n u(-n-1)$$

$$(ii) \quad x(t) = 4e^{-2t} u(t)$$

2. (a) Obtain output  $y(t) = x(t) * h(t)$  using graphical convolution. 10

$$x(t) = 1+t \quad \text{for } -1 \leq t \leq 0 \\
 = 1-t \quad \text{for } 0 \leq t \leq 1$$

$$h(t) = 1 \quad \text{for } 0 \leq t \leq 2 \\
 = 0 \quad \text{elsewhere}$$

- (b) Obtain  $h(n)$  for all possible ROC conditions. Also plot the ROC comment on causality and stability at the system. 10


$$H(z) = \frac{4z(z^2 - 8z + 9)}{(z - \frac{1}{3})(z - 3)(z + 4)}$$

3. (a) A C.T. LTI system has 8

$$\frac{d^2y(t)}{dt^2} + \frac{5dy(t)}{dt} + 6y(t) = \frac{7dx(t)}{dt} - 3x(t)$$

- (i) Determine Transfer function.  
 (ii) Obtain impulse response.  
 (iii) Obtain unit Ramp response.

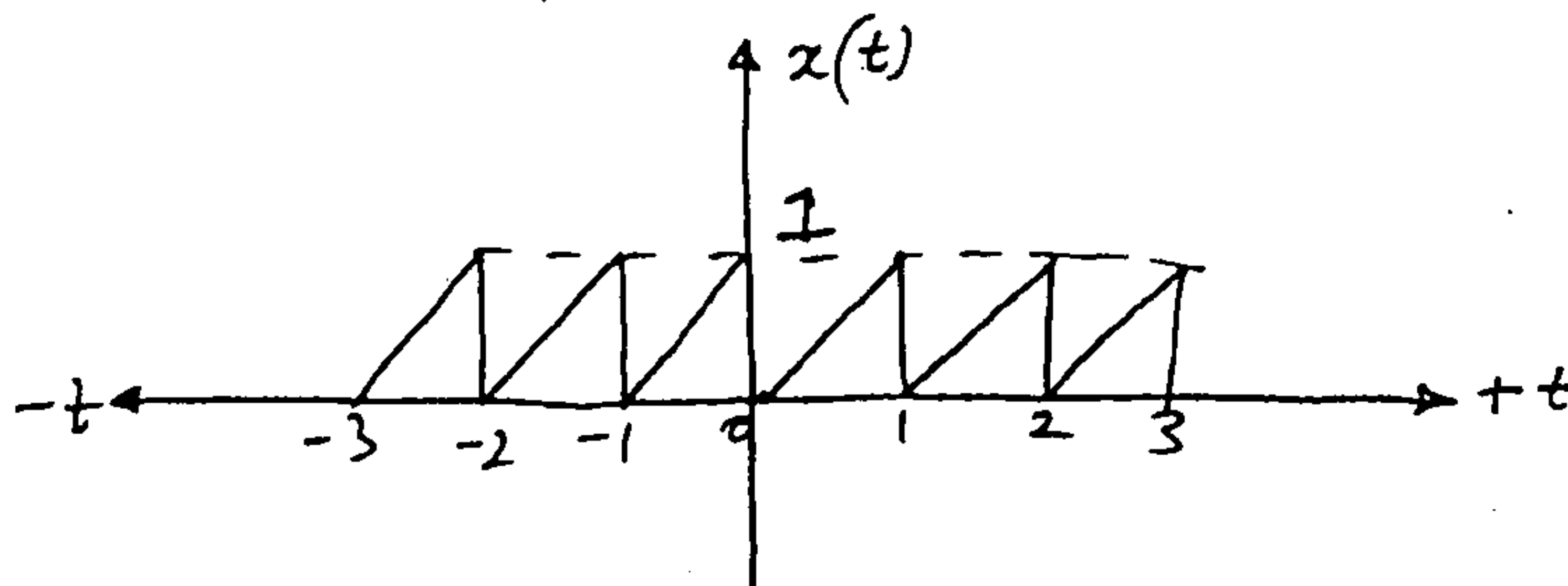- (b) Plot the magnitude and phase spectrum of the periodic signal. Shown below. 8



TURN OVER

- (c) Obtain initial and final value 4

$$\text{if } X(z) = \frac{3z^2}{4z^2 - 5z + 1}$$

4. (a) If two subsystem are connected in cascade 8

$$h_1(n) = (0.9)^n u(n) - 0.5(0.9)^{n-1} u(n-1)$$

$$h_2(n) = (0.5)^n u(n) - (0.5)^{n-1} u(n-1)$$

Determine overall impulse response of the interconnected system.

- (b) Obtain z transform of the following signal using properties of z transform. 6

$$x(n) = \left(\frac{3}{4}\right)^{n-1} \sin\left(\frac{\pi}{6}n\right) u(n)$$


- (c) Prove Parsevals theorem of Fourier series. 6

5. (a) Obtain circular convolution of 5

$$x_1(n) = [3 \ 2 \ 1 \ 4]$$

$$x_2(n) = [5 \ 7 \ -8 \ 2]$$

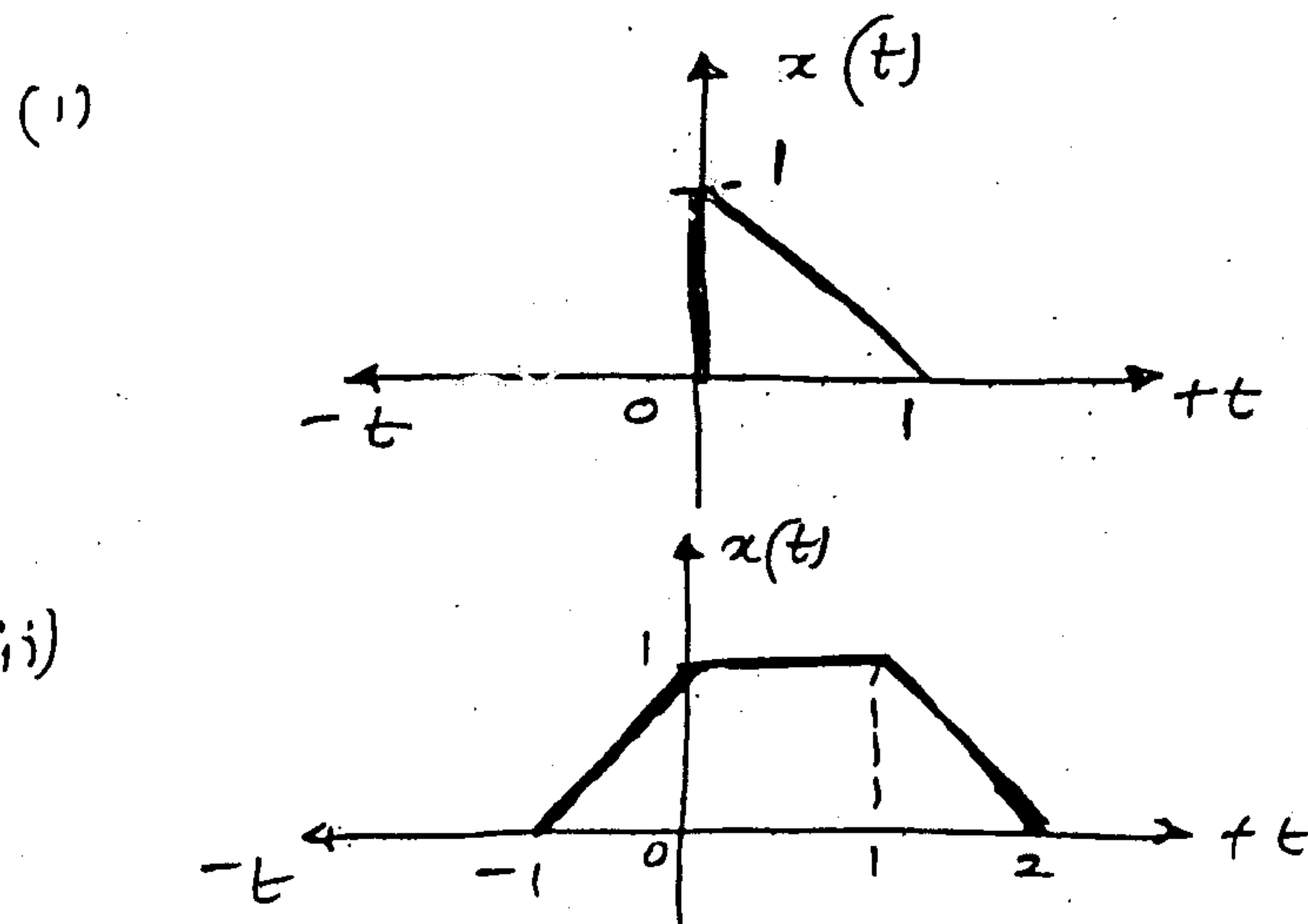- (b) Obtain Laplace Transform of following waveforms using its properties. 5



- (c) Obtain zero input response, zero state response and total response of a D. T. L. T. I. system. 10


$$y(n) + 7y(n-1) + 12y(n-2) = 4x(n) - 11x(n-1)$$

If  $y(-1) = 1$   $y(-2) = 2$   $x(-1) = 0$ .


If input  $x(n) = u(n) = \text{unit step signal}$

TURN OVER

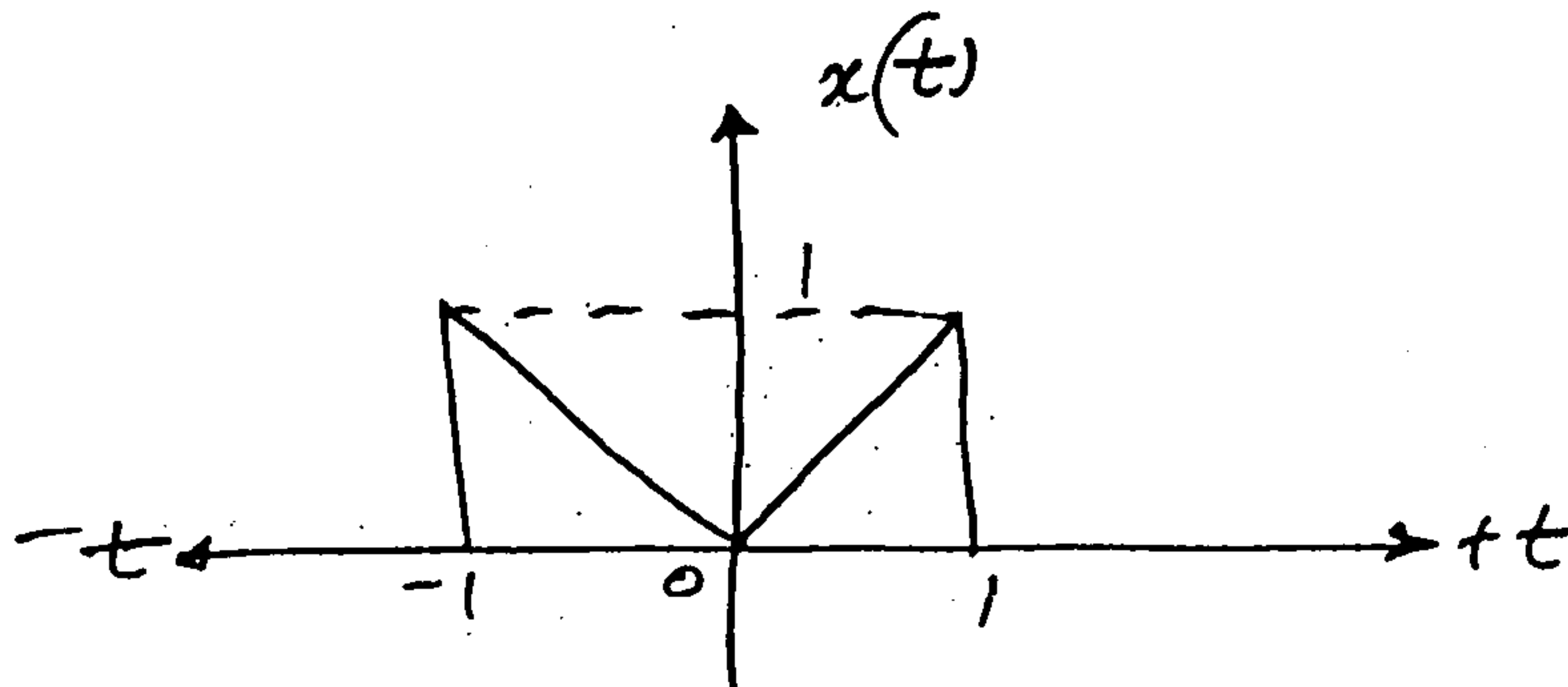6. (a) Obtain Fourier transform of the following signal. 6



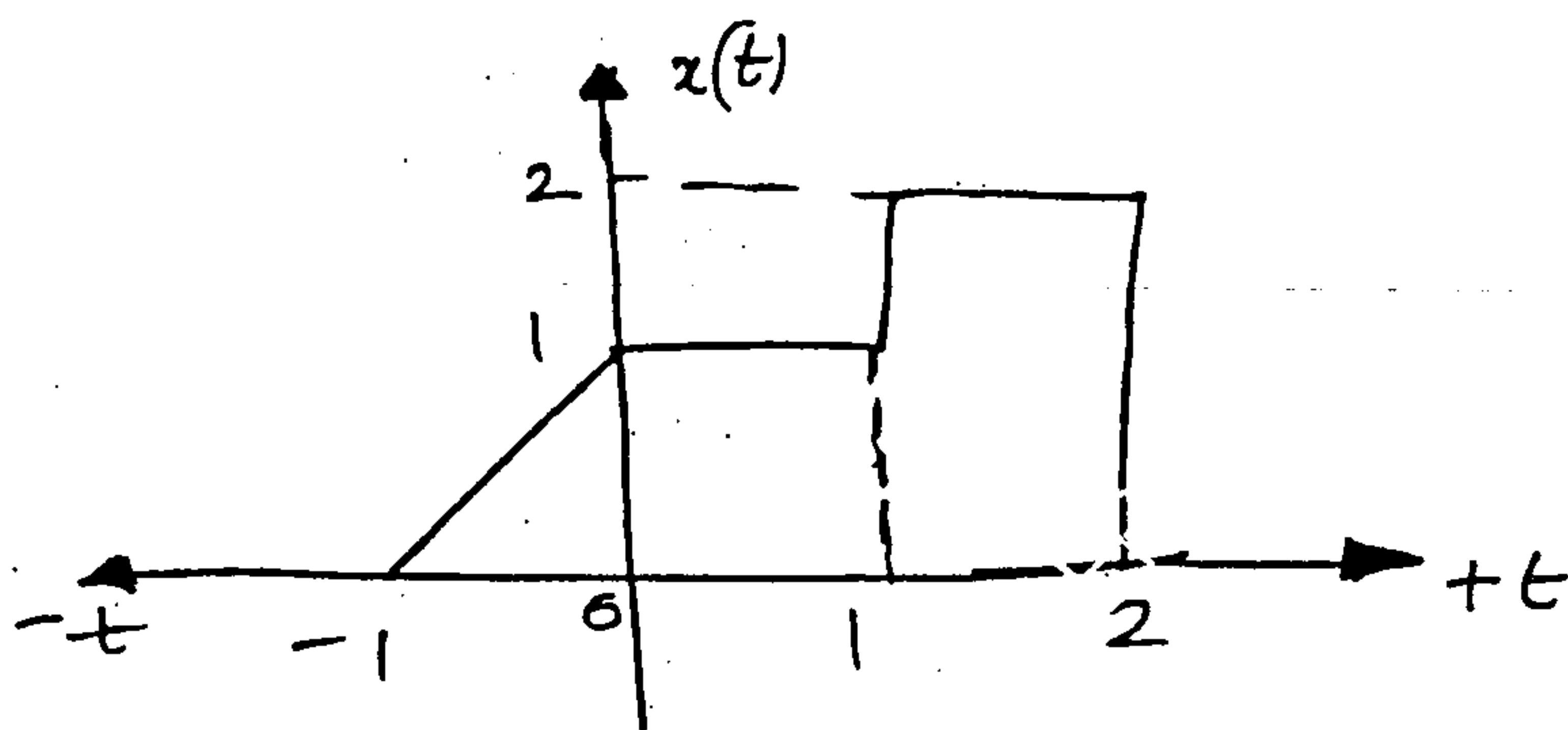- (b) Plot even and odd parts of following signals. 6



- (c) Obtain  $h(t)$  for causal and stable system If 8

$$H(s) = \frac{s^2 - 3s + 11}{(s-i)(s+2)(s+3)}$$

Plot the ROC and pole's and zero's of the system.

N.B. (1) Question No. 1 is compulsory.

(2) Solve any **three** questions from **remaining** questions.

(3) Assume **suitable** data if **necessary**.

1. Solve any **four** :-

(a) What is the need of Input offset voltage compensation and how it can be achieved. 5

(b) Design RC phase shift oscillator to produce sinusoidal output of 5KHz. 5

(c) Design schmitt strigger circuit to achiev upper and lower threshold voltage as 1.5 volts. 5

(d) Explain Resolution, Accuracy and settling time with respect to DAC. 5

(e) Design a Flasher circuit using IC 555, in which lamp should remain on for 4 sec and off for 2 sec. 5


2. (a) Derive closed loop parameters for Inverting opamp. 10

(b) Design a second order KRC low pass filter with a cut off frequency  $f_o = 2\text{KHz}$  and  $Q = 5$ . 10

3. (a) Design a triangular wave generator to get the ouput frequency of 1.5 KHz and  $V_{o(p-p)} = 7.5\text{V}$  using IC 741. 10

(b) Explain counter type ADC with neat diagram. 10

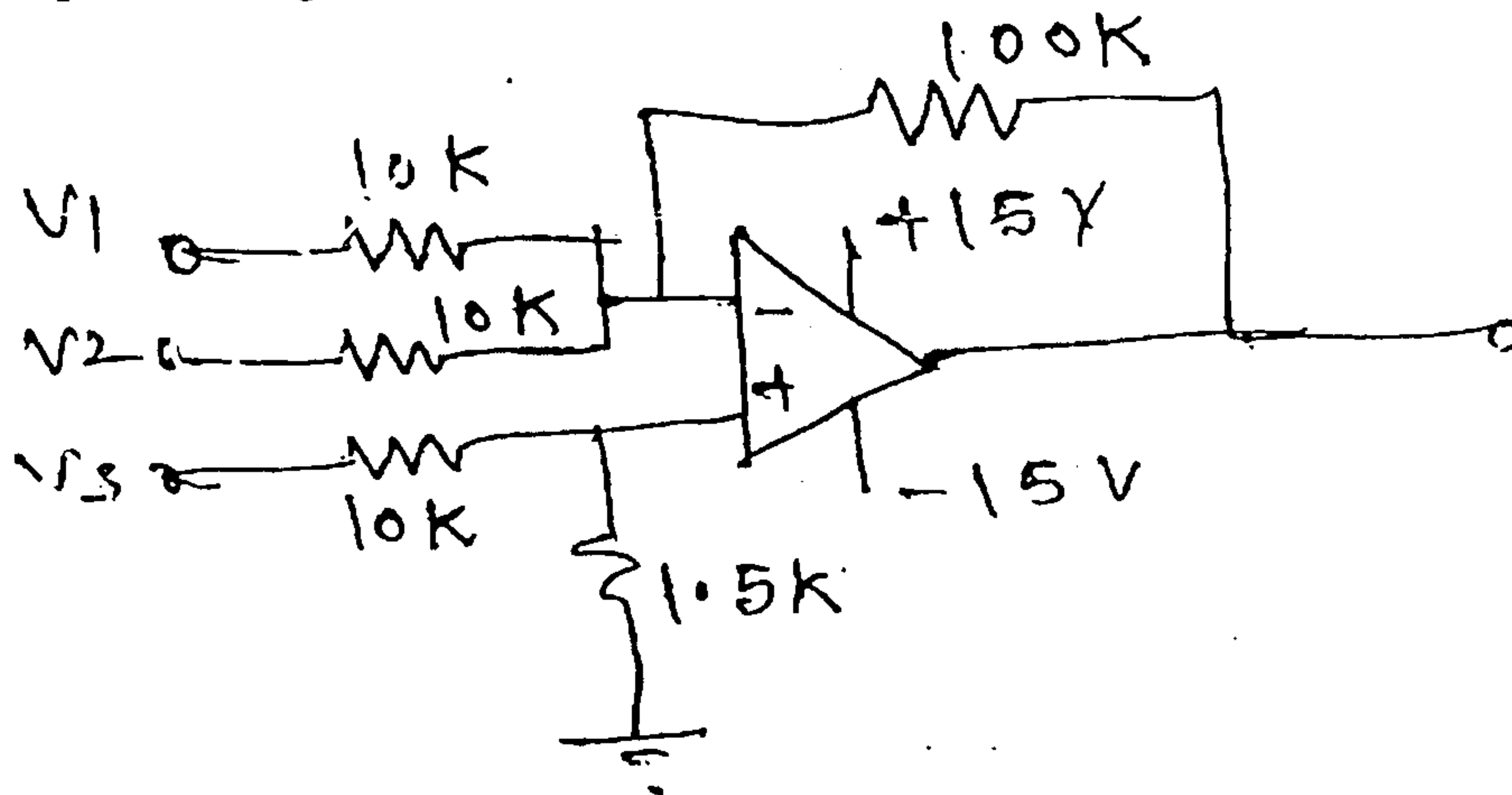4. (a) Calculate output voltage for the given amplifier. 10



$$V_1 = 1.5\text{V}$$

$$V_2 = 3\text{V}$$

$$V_3 = 4\text{V}$$

- (b) (i) Prove that opamp can be used as current to voltage converter. 4
- (ii) Compare normal rectifier with precision rectifier. 3
- (iii) Define different parameters of PLL. 3
5. (a) Explain different comparators, state different applications and suggest 10  
modifications for practical comparator.
- (b) What are different possible IC 723 based voltage regulators. Design voltage 10  
regulator to achieve  $V_o = 12V$  and  $I_o = 1$  Amp.
6. (a) Explain function of each block of PLL. 10
- (b) Design voltage Regulator using IC LM317 for the given specifications. 10  
 $V_o = 12 \pm 3$  volts and  $I_L = 100mA$ .
-